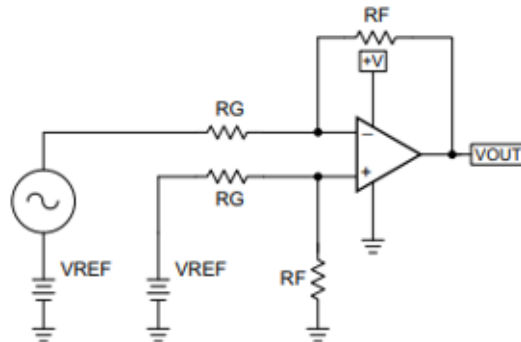



LINEAR INTEGRATED CIRCUITS QUESTION BANK

UNIT-1 part 2


- 1) List out reasons for single supply op amp device
- 2) What is DC offset voltage ? How it effects output?
- 3) What is the role V_{REF} in this circuit ?



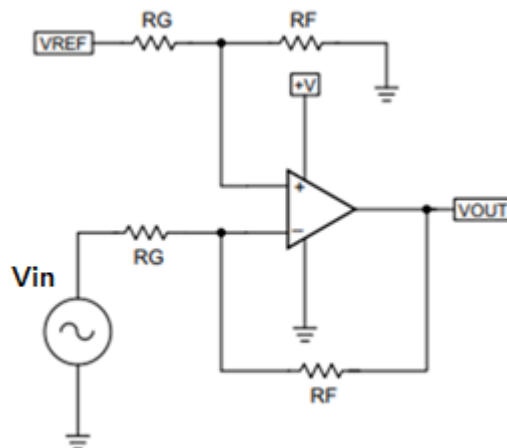
- 4) Write output voltage equation for the below circuit.



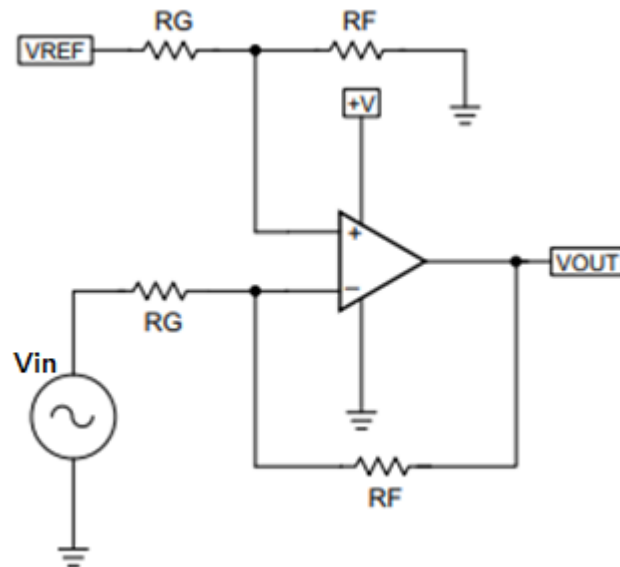- 5) What is the value of output voltage when $V_{REF} = V_{OUT}$? Refer above circuit
- 6) Write output voltage equation for the below circuit for three conditions
 - a. When $V_{REF} = V_{IN}$
 - b. When $V_{REF} = 0$
 - c. When $V_{REF} = 0$ and V_{IN} is positive



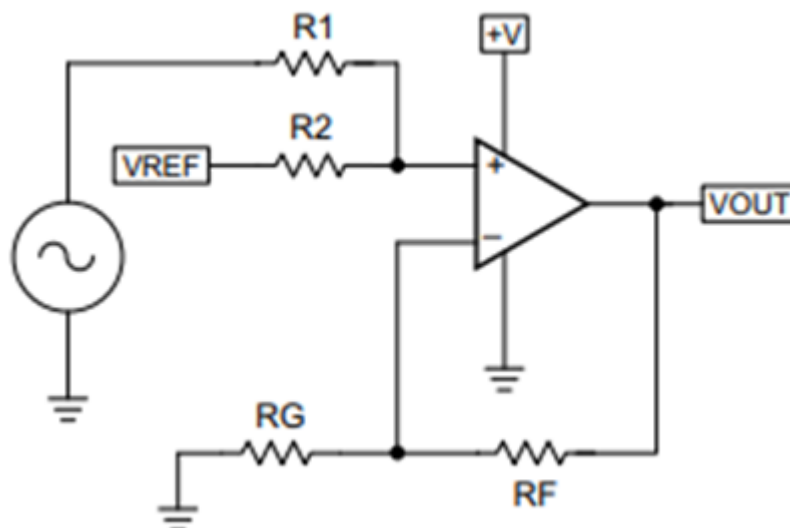- 7) Why above circuit will not work for positive input voltage?
- 8) In a typical representation of op amp in simultaneous equation form, what m represents and what b represents?
- 9) Calculate m and b for amplifier specifications; input range 0.1V to 0.4V and output range 1V to 5V
- 10) Write equation for m and b for the below circuit.



- 11) Write circuit diagram of op amp amplifier for following specification; $V_{out} = 1.5V$ at $V_{in} = 0.2V$ and $V_{out} = 4.5V$ at $V_{in} = 0.6V$

