

LINEAR INTEGRATED CIRCUITS

Dr Shashidhar Tantry

Electronics and Communication Engineering


Current feedback amplifier

- *Current feedback* refers to any closed-loop configuration in which the error signal used for feedback is in the form of a current. A current feedback op amp responds to an error current at one of its input terminals, rather than an error voltage, and produces a corresponding output voltage
- The transfer function of a *transimpedance amplifier* is expressed as a voltage output with respect to a current input
- the open-loop "gain", v_O/i_{IN} , is expressed in ohms


Summary of points in current feedback op amps

- Non inverting and Inverting gain circuits use the same formula for the gain that is $-R_F/R_G$ and $1+R_F/R_G$
- Use R_F as recommended by the data sheet, R_G can be as per the gain
- Use noninverting circuit, otherwise it will load source
- Never put capacitance across feedback resistor
- If only DC gain required, preferably use voltage feedback
- Current feedback op amps are choice for high speed and high current requirements
- For filters, voltage feedback op amp is preferred
- Current feedback op amps are best for high speed and high current circuits

Unit 3 Current feedback amplifier model

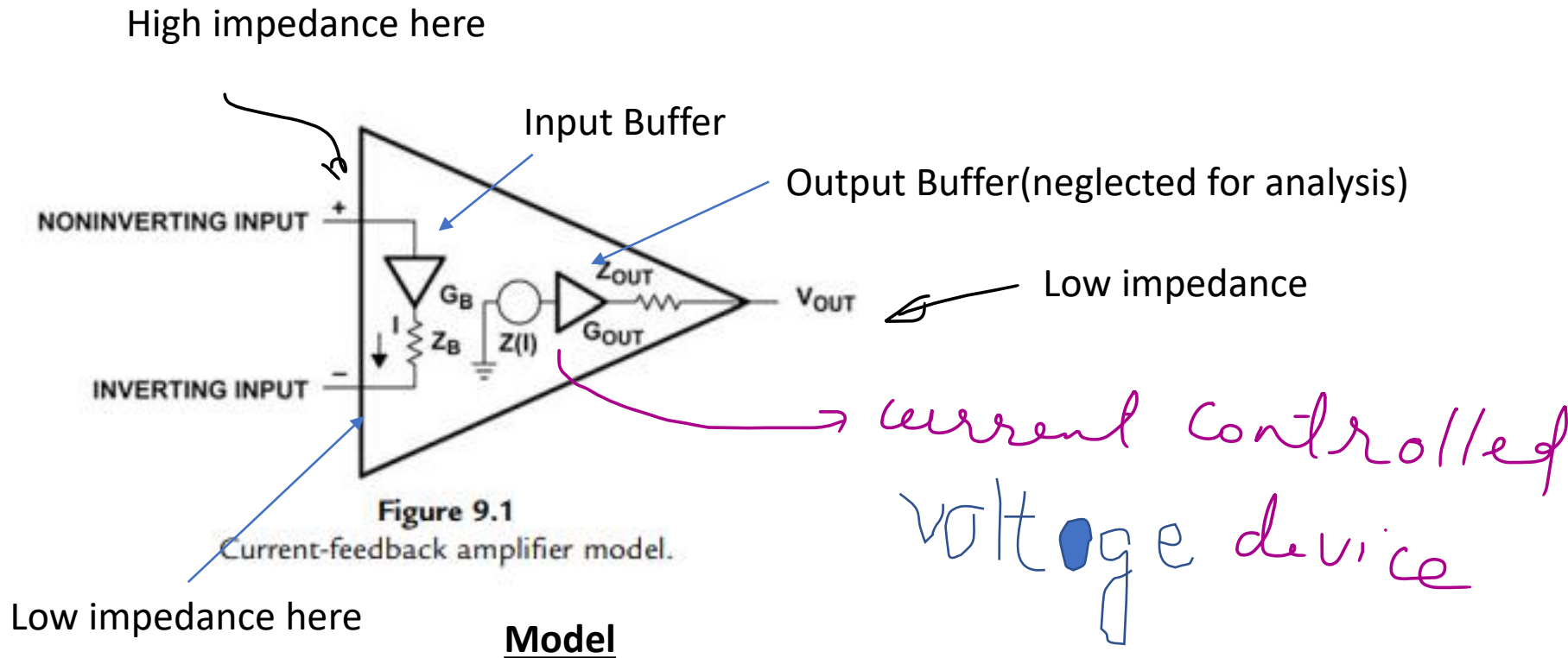


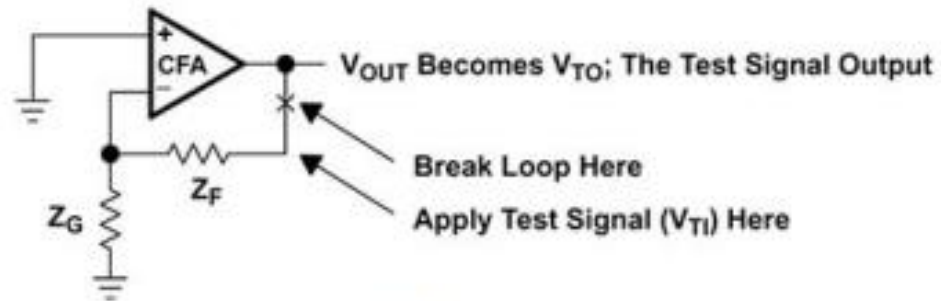Unit 3 Development of stability equations



Loop gain

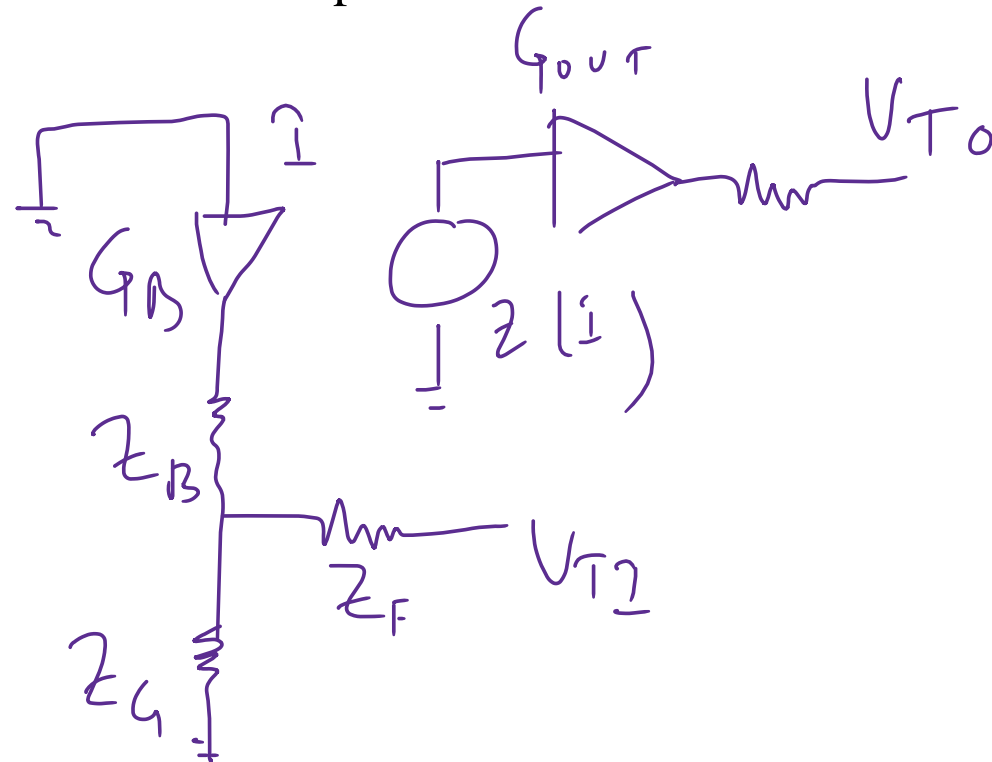- Stability measurement done by loop gain
 - Feedback circuit is seen at negative input terminal
- Break the loop, apply test signal and measure output



Unit 3 Development of stability equations

- Break the loop, apply test signal and measure output
- Z is the transimpedance of the op amp which is nothing but gain in terms of impedance

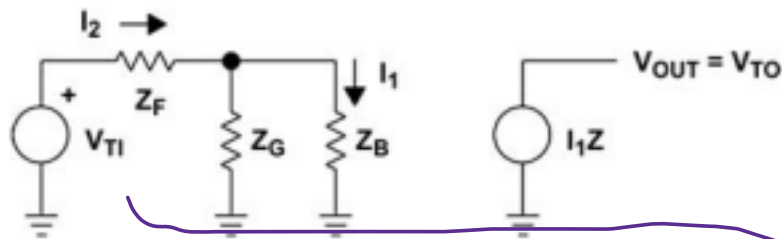


Figure 9.3
Stability analysis circuit.

$$V_{TO} = I_1 Z$$

$$V_{T1} = I_2 (Z_F + Z_G \parallel Z_B)$$

Loop gain

Use
current

divider theorem

$$\rightarrow I_2 (Z_G \parallel Z_B) = I_1 Z_B$$

$$\rightarrow I_2 = I_1 (Z_G + Z_B) / Z_G$$

— (2)

Unit 3 Development of stability equations

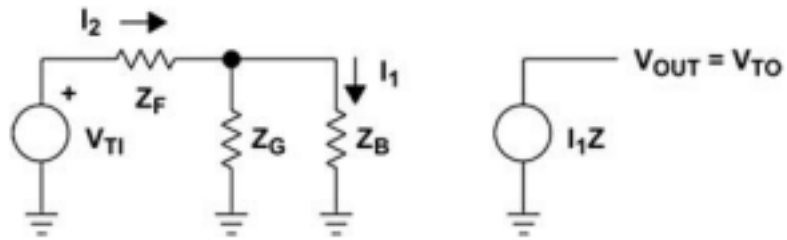


Figure 9.3
Stability analysis circuit.

$$V_{TO} = I_1 Z \quad \text{--- (4)}$$

From (3) & (4)

from (1) & (2)

$$V_{T1} = I_1 (Z_F + Z_G \parallel Z_B) \left(1 + \frac{Z_B}{Z_G} \right)$$


or

$$V_{T1} = I_1 Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right) \quad \text{--- (3)}$$

$$A\beta = \frac{V_{TO}}{V_{T1}} = \frac{Z}{\left(Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right) \right)}$$

This is Loop gain

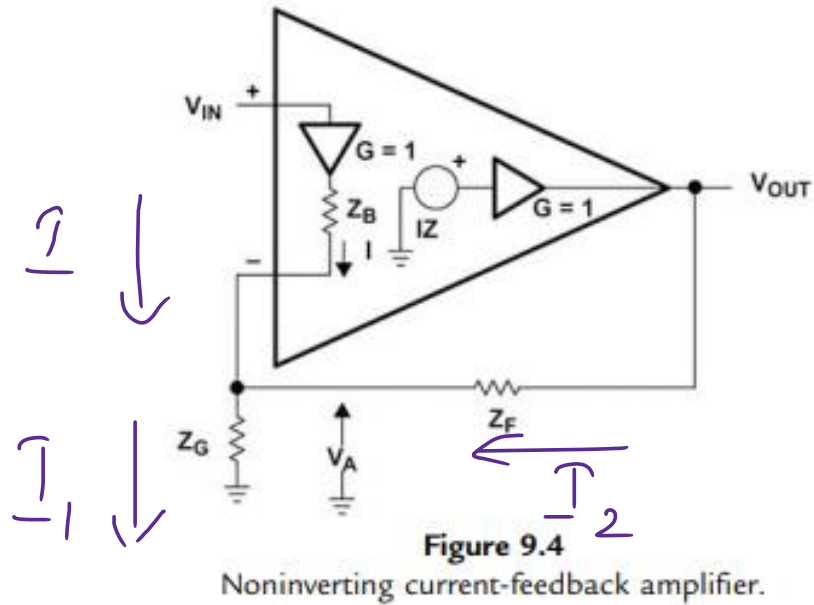Unit 3 Noninverting current feedback amplifier



Circuit is nothing but non inverting amplifier

$$V_A = V_{IN} - IZ_B$$

$$V_{OUT} = IZ$$

$$I = I_1 - I_2$$

$$I_1 = V_A / Z_G$$

$$I_2 = (V_{OUT} - V_A) / Z_F$$

$$I = (V_A / Z_G) - (V_{OUT} - V_A) / Z_F$$

Unit 3 Noninverting current feedback amplifier

From (1) (2) & (3)

$$\frac{V_{OUT}}{V_{IN}} = \frac{\frac{Z \left(1 + \frac{Z_F}{Z_G}\right)}{Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G}\right)}}{1 + \frac{Z}{Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G}\right)}}$$

$Z_\phi \approx 0$

$$\frac{V_{OUT}}{V_{IN}} = \frac{Z \left(1 + \frac{Z_F}{Z_G}\right)}{Z_F \left(1 + \frac{Z}{Z_F}\right)} = \frac{1 + \frac{Z_F}{Z_G}}{1 + \frac{Z_F}{Z}}$$

Unit 3 Noninverting current feedback amplifier

$$\frac{V_{OUT}}{V_{IN}} = \frac{\frac{Z \left(1 + \frac{Z_F}{Z_G} \right)}{Z_F}}{1 + \frac{Z}{Z_F}} = \frac{1 + \frac{Z_F}{Z_G}}{1 + \frac{Z_F}{Z}}$$

when $Z = \text{high}$

$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{Z_F}{Z_G}$$

Identical to Voltage Feedback amplifier

Unit 3 Inverting current feedback amplifier

$$I + I_2 = I_1$$

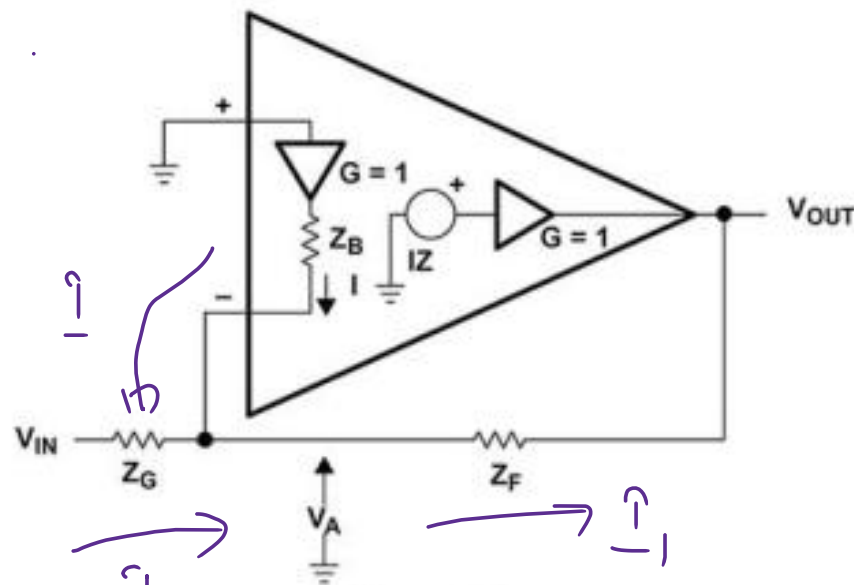


Figure 9.5

Inverting current-feedback amplifier.

$$I + (V_{IN} - V_A)/Z_G = (V_A - V_{OUT})/Z_F \quad \text{--- (1)}$$

$$-V_A = IZ_B \quad \text{--- (2)}$$

$$V_{OUT} = IZ \quad \text{--- (3)}$$

Circuit is nothing but inverting amplifier

Unit 3 Inverting current feedback amplifier

From ① ② & ③

$$\frac{V_{OUT}}{V_{IN}} = - \frac{\frac{Z}{Z_G \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right)}}{1 + \frac{Z}{Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right)}}$$

when $Z_B \approx 0$

$$\frac{V_{OUT}}{V_{IN}} = - \frac{\frac{1}{Z_G}}{\frac{1}{Z} + \frac{1}{Z_F}}$$

Unit 3 Inverting current feedback amplifier

$$\frac{V_{OUT}}{V_{IN}} = -\frac{\frac{Z}{Z_G \left(1 + \frac{Z_B}{Z_F \parallel Z_G}\right)}}{1 + \frac{Z}{Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G}\right)}}$$

z = high

$$\frac{V_{OUT}}{V_{IN}} = -\frac{Z_F}{Z_G}$$

Identical to Voltage Feedback amplifier

Unit 3 Stability analysis

$$A\beta = \frac{V_{TO}}{V_{TI}} = \frac{Z}{\left(Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right) \right)}$$

Stability equation (loop gain)

$$20 \text{ LOG}|A\beta| = 20 \text{ LOG}|Z| - 20 \text{ LOG} \left| Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right) \right|$$
$$\phi = \text{TANGENT}^{-1}(A\beta)$$

Gain and Phase equations for loop gain

Typical values

$$Z = \frac{1 \text{ M}\Omega}{(1 + \tau_1 S)(1 + \tau_2 S)}$$
$$Z_B = 70 \Omega$$
$$Z_G = Z_F = 1 \text{ k}\Omega$$

Unit 3 Stability analysis

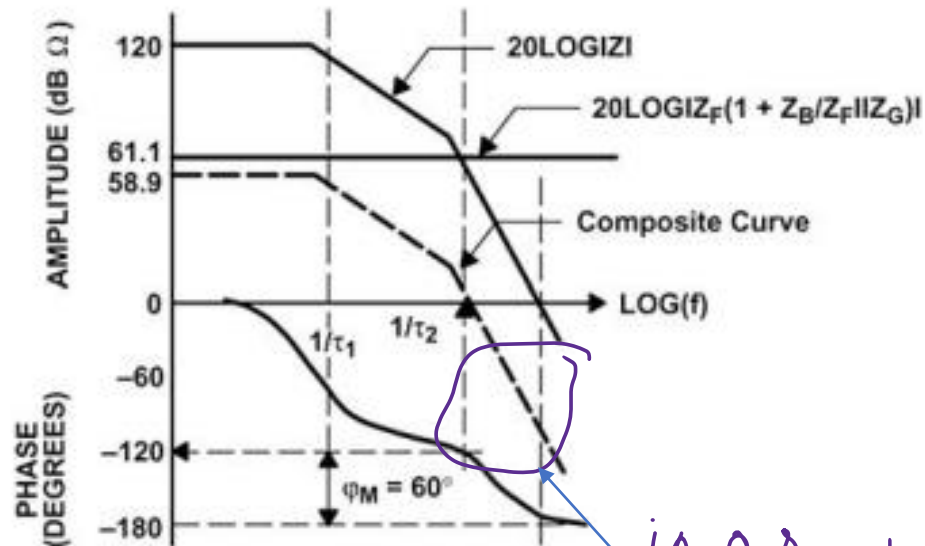


Figure 9.6
Bode plot of stability equation.

- Open loop Gain is measured in terms of Z which trans-impedance
- Loop gain too measured in terms of impedance
- Assumed open loop gain to have two poles
- Loop gain reduces gain. As a result phase margin improves

Unit 3 Stability analysis

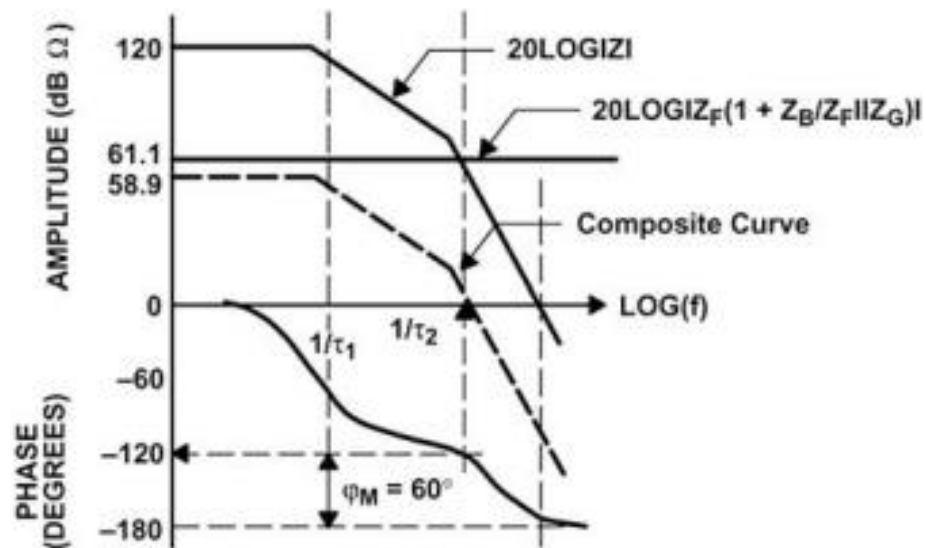


Figure 9.6
Bode plot of stability equation.

Summary of points

- R_F is usually recommended by the manufacturer
- R_F selection based on stability and bandwidth requirement

$$A\beta = \frac{V_{TO}}{V_{TI}} = \frac{Z}{\left(Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G}\right)\right)}$$

$$A\beta = \frac{Z}{Z_F + Z_B \left(1 + \frac{R_F}{R_G}\right)}$$

Stability equation Different form

When $Z_B = 0$ and $Z_F = R_F$



$$A\beta = Z/R_F$$

Unit 3 Selection of feedback resistor

First method : Key points

- R_F defines stability of the amplifier
- It is important to select R_F properly
- R_F value range given by the manufacturer
- If different value to be used, results of loop gain are extrapolated assuming linear relation

Loop gain 1 value

Loop gain 2 value

$$\frac{Z}{Z_{F1} + Z_B \left(1 + \frac{Z_{F1}}{Z_{G1}} \right)} = \frac{Z}{Z_{FN} + Z_B \left(1 + \frac{Z_{FN}}{Z_{GN}} \right)}$$
$$Z_{FN} = Z_{F1} + Z_B \left(\left(1 + \frac{Z_{F1}}{Z_{G1}} \right) - \left(1 + \frac{Z_{FN}}{Z_{GN}} \right) \right)$$

New value of feedback resistor

Unit 3 Selection of feedback resistor

Second method

We can also use graphical method to select R_F value

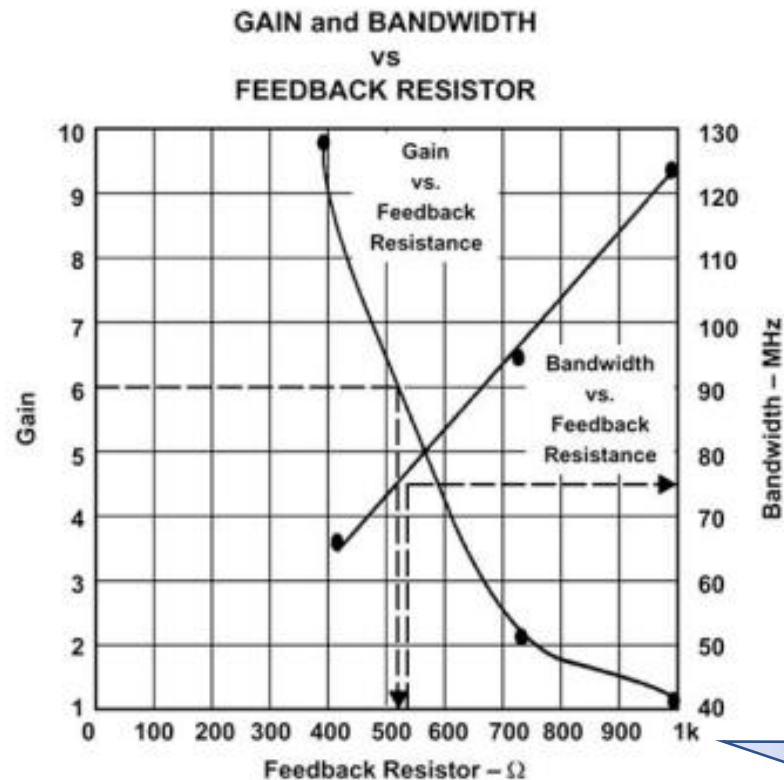


Figure 9.7

Plot of current-feedback amplifier R_F , G , and BW.

For a given gain, calculate R_F and from R_F calculate Bandwidth of the amplifier

Table represents different gain R_F and Bandwidth values


Table 9.1: Data Set for Curves in Fig. 9.7

Gain (A_{CL})	R_F (Ω)	Bandwidth (MHz)
+1	1000	125
+2	681	95
+10	383	65

Graph taken from the data sheet of CFA


Unit 3 Stability and input capacitance

Stray capacitance gets introduced across input resistor
Hence Z_G becomes reactive

$$Z_G = \frac{R_G}{1 + R_G C_G s}$$


Loop gain is given by,

$$A\beta = \frac{Z}{Z_B + \frac{Z_F}{Z_G^2 + Z_B Z_G}}$$


$$Z_B = R_B \quad Z_G = R_G$$


From 1 and 2, loop gain is given by,

$$A\beta = \frac{Z}{R_F \left(1 + \frac{R_B}{R_F \parallel R_G} \right) (1 + R_B \parallel R_F \parallel R_G C_G s)}$$

Loop gain added with one pole

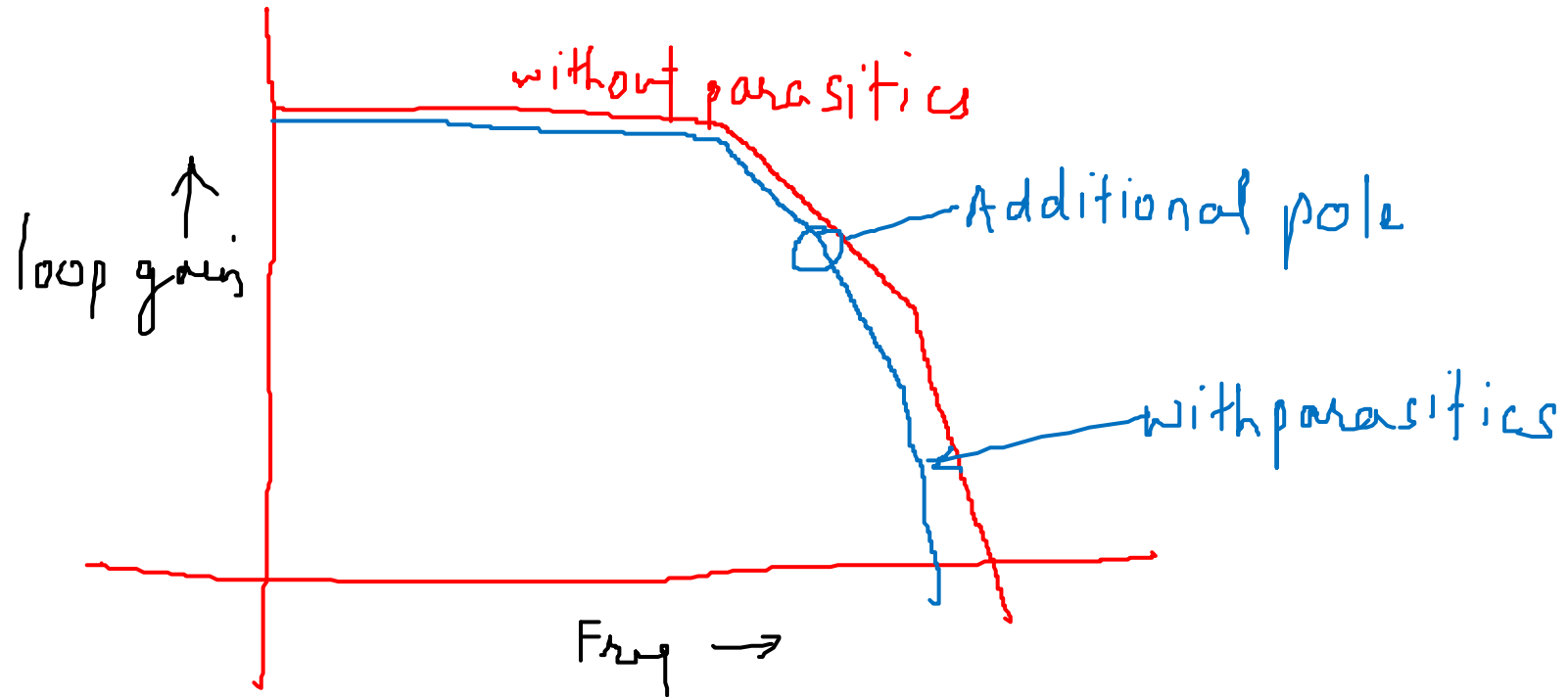Unit 3 Stability and feedback capacitance



Unit 3 Stability and feedback capacitance

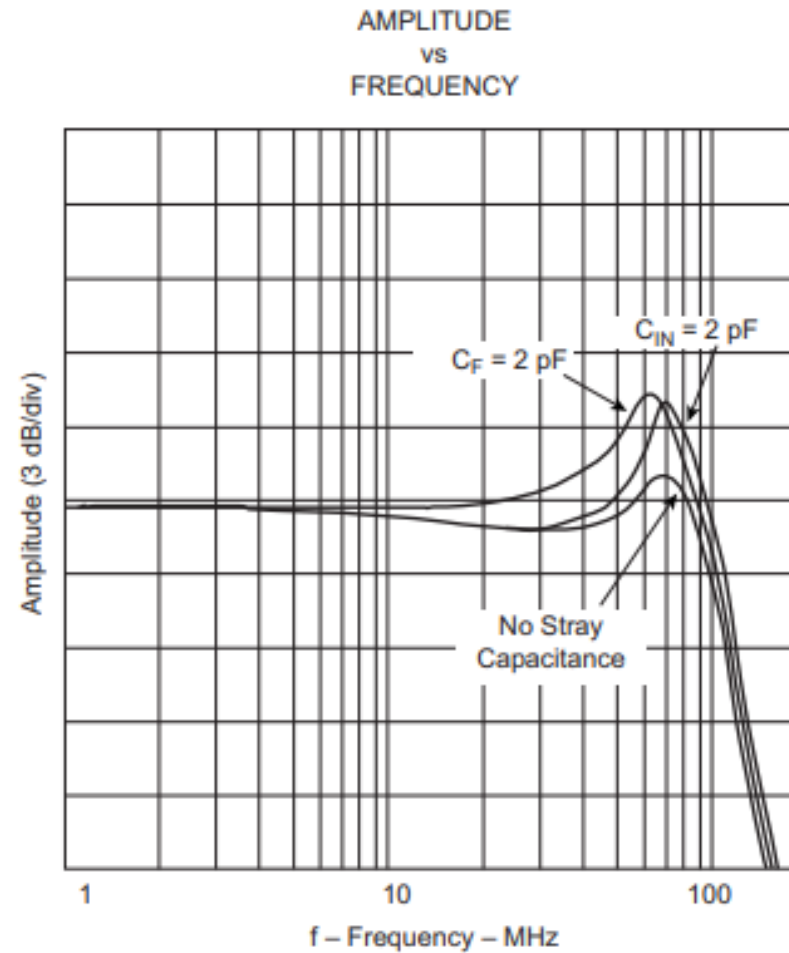



Figure 9.8

Effects of stray capacitance on current-feedback amplifiers.

Unit 3 Stability and feedback capacitance

Stray capacitance gets introduced across feedback resistor Hence Z_F becomes reactive

$$Z_F = \frac{R_F}{1 + R_F C_{FS}}$$



From 1 and 2, loop gain is given by,

Loop gain is given by,

$$A\beta = \frac{V_{TO}}{V_{TI}} = \frac{Z}{\left(Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right) \right)}$$

$$A\beta = \frac{Z(1 + R_F C_{FS})}{R_F \left(1 + \frac{R_B}{R_F \parallel R_G} \right) (1 + R_B \parallel R_F \parallel R_G C_{FS})}$$

Loop gain added with one pole and one zero,

$$Z_B = R_B \quad Z_G = R_G$$


Unit 3 Stability and feedback capacitance

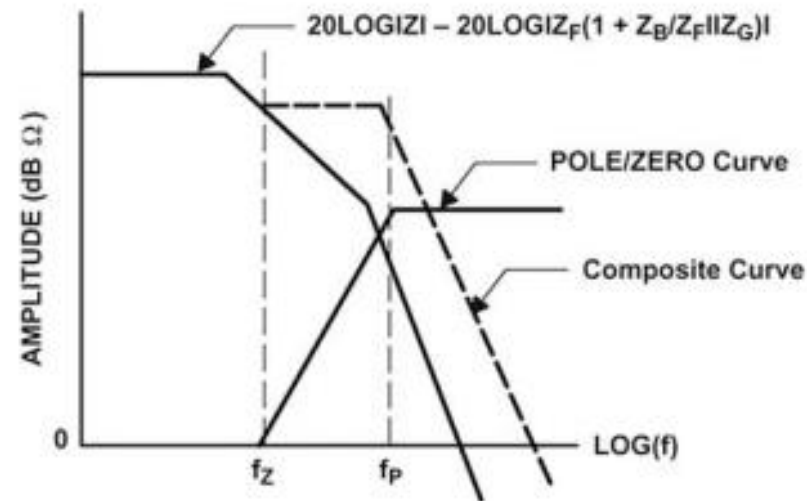


Figure 9.9

Gain plot with and without addition of poles and zeros

Unit 3 Stability with input capacitance and feedback capacitance

Z_F becomes reactive and Z_G also becomes reactive


Loop gain equation becomes,

$$A\beta = \frac{Z(1 + R_F C_F s)}{R_F \left(1 + \frac{R_B}{R_F \parallel R_G}\right) (R_B \parallel R_F \parallel R_G (C_F + C_G)s + 1)}$$


- when pole = zero
- when $R_F \gg R_G \& R_B$
 $R_F C_F = C_G (R_G \parallel R_B)$

when $R_B \ll R_G$

$$R_F C_F = R_B C_G$$

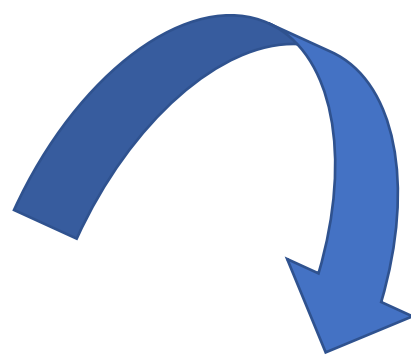


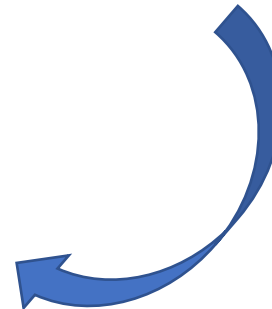To make circuit to
cancel pole and zero,
we need to keep



Unit 3 Comparison between VFA and CFA - Precision

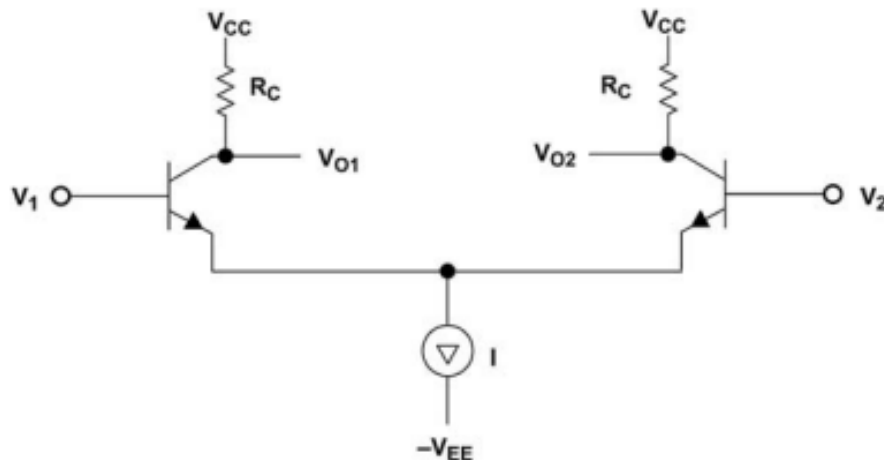- Traditional op amps are voltage feedback type whereas current feedback amps are recent
- VFA input comes from differential pair




Differential pair are perfectly matched

- V_{BE} are matched
- Q_1 and Q_2 are matched
- Transistor current gains are matched
- Matched for layout equality
- Thermal balancing
- Trimming

Unit 3 Comparison between VFA and CFA - Precision

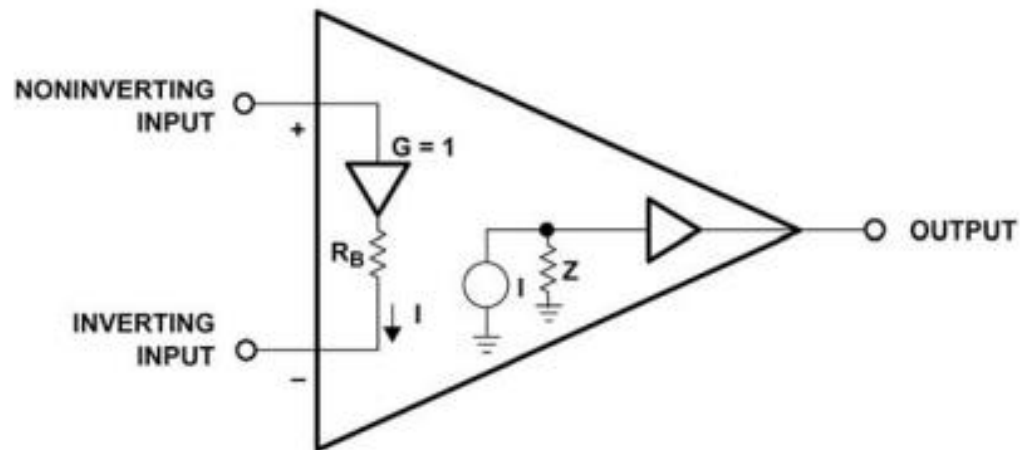- CFA inputs are at different impedance levels



CFA

- Input impedance for inverting and non inverting are different
- Common mode rejection is not good
- Overall precision is bad compared to VFA

Unit 3 Comparison between VFA and CFA - Bandwidth

- VFA bandwidth not good


$$A\beta = \frac{aR_G}{R_F + R_G}$$

$$A\beta = \frac{a}{\frac{R_F + R_G}{R_G}} = \frac{a}{G_{CLI}}$$

$$A\beta = \frac{a}{\frac{R_F + R_G}{R_G}} = \frac{a}{G_{CLI} + 1}$$

VFA

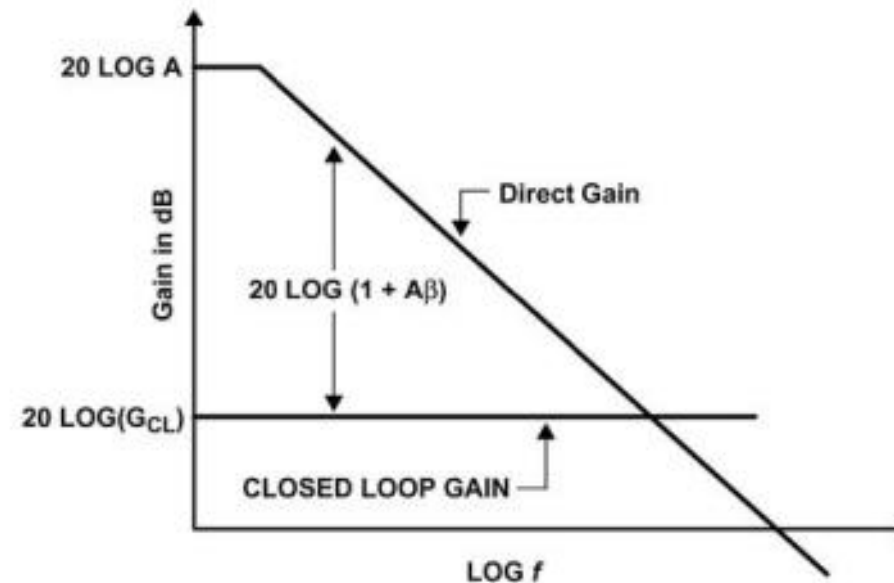- Loop gain decreases for an increase in bandwidth
- Error is directly related to the bandwidth



Unit 3 Comparison between VFA and CFA - Bandwidth


- CFA bandwidth good

$$A\beta = \frac{Z}{R_F \left(1 + \frac{R_B}{R_F \parallel R_G} \right)}$$

$$A\beta = \frac{Z}{R_F}$$

CFA

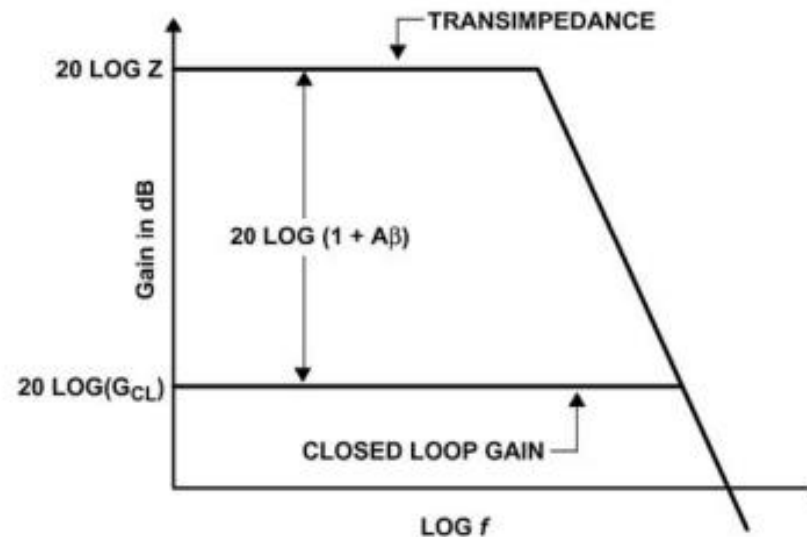- No low frequency pole
- Loop gain does not depend on closed loop gain



Unit 3 Comparison between VFA and CFA - Stability

- **VFA stability**

$$A\beta = \frac{aR_G}{R_F + R_G}$$

Stability depends on a , R_G and R_F

Stray capacitance does not change stability significantly


- **CFA stability**

$$A\beta = \frac{Z}{R_F}$$

Stability depends on R_F

Stray capacitance play role in stability significantly

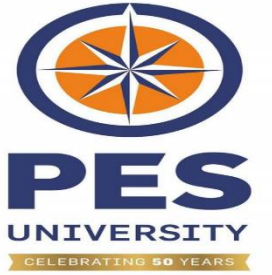Unit 3 Comparison between VFA and CFA - Impedance



- **VFA impedance**

Input impedance is high and matched at both terminals
Even in CMOS input impedance is high

- **CFA impedance**

Not high compared to VFA
Two input impedances are not matched
Because of low input impedance at inverting terminal

Unit 3 Comparison Table on equations

Table 10.1: Tabulation of Pertinent Voltage-Feedback Amplifier and Current-Feedback Amplifier Equations

Circuit Configuration	Current-Feedback Amplifier	Voltage-Feedback Amplifier
Noninverting		
Forward or direct gain	$\frac{Z \left(1 + \frac{Z_F}{Z_G} \right)}{Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right)}$	a
Ideal loop gain	$\frac{Z}{Z_F} \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right)$	$\frac{aZ_F}{(Z_G + Z_F)}$
Actual closed-loop gain	$\frac{Z_F \left(1 + \frac{Z_B}{Z_G} \right)}{Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right)}$	$\frac{a}{1 + \frac{aZ_G}{Z_F \parallel Z_G}}$
Closed-loop gain	$1 + \frac{\frac{Z}{Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right)}}{1 + Z_F/Z_G}$	$1 + Z_F/Z_G$
Inverting		
Forward or direct gain	$\frac{Z}{Z_G \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right)}$	$\frac{aZ_F}{(Z_F + Z_G)}$
Ideal loop gain	$\frac{Z}{Z_F} \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right)$	$\frac{aZ_G}{(Z_G + Z_F)}$
Actual closed-loop gain	$\frac{-Z_G \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right)}{1 + \frac{Z}{Z_F \left(1 + \frac{Z_B}{Z_F \parallel Z_G} \right)}}$	$\frac{-aZ_F}{\frac{Z_F + Z_G}{1 + \frac{aZ_G}{Z_F \parallel Z_G}}}$
Closed-loop gain	$-Z_F/Z_G$	$-Z_F/Z_G$

Unit 3 Fully Differential op amp

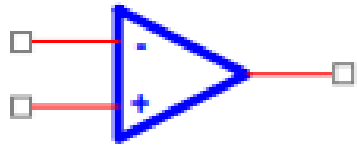


Figure 11.1

Single-ended op amp schematic symbol.

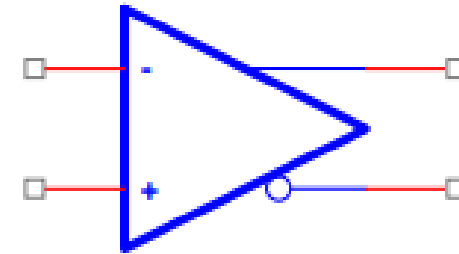
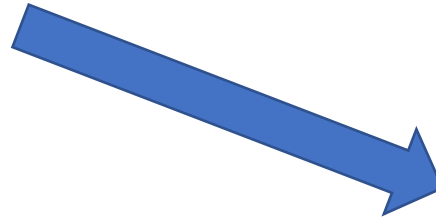


Figure 11.2

Fully differential op amp schematic symbol.

- Differential input (Two inputs), single output (One output)
- 2 inputs and 1 output

- Differential input (Two inputs), differential output (Two outputs)
- 2 inputs and 2 outputs

Unit 3 Fully Differential op amp

Why use integrated fully-differential amplifiers?

- Increased immunity to external noise
- Increased output voltage swing for a given voltage rail
- Ideal for low-voltage systems
- Integrated circuit is easier to use
- Reduced even-order harmonics

Unit 3 Fully Differential op amp


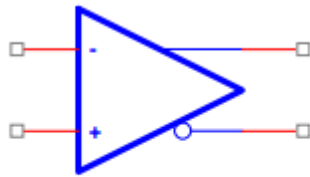


Figure 11.2
Fully differential op amp schematic symbol.

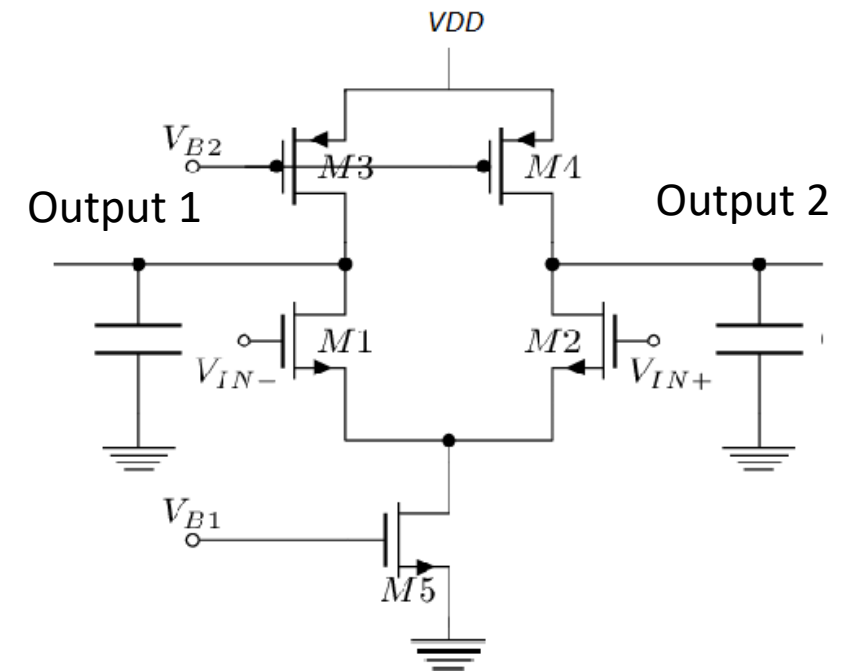

- Differential input(Two inputs),
differential output(One output)

- Typical circuit inside fully
differential amplifier

Unit 4 Fully Differential op amp

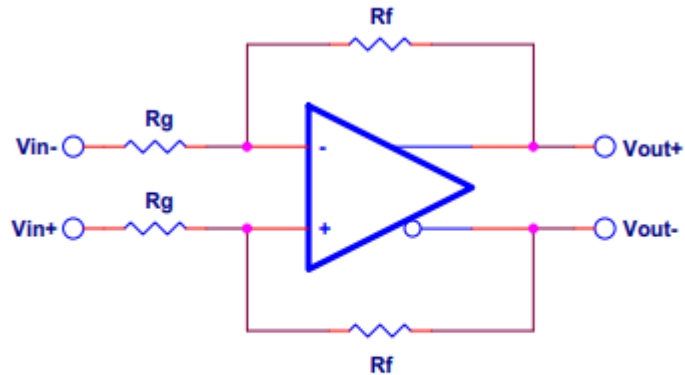


Figure 11.4

Closing the loop on a fully differential op amp.



- Two closed loop feedbacks are required for feedback circuit
- Loop is from inverting input to non inverting output and non inverting input to inverting output
- Assume 180 degree phase difference between two inputs and two outputs
- Both loops to be matched
- Here, each loop is a inverting type

Ideal fully differential
op amp gain is

$$\frac{V_O}{V_I} = \frac{R_F}{R_G}$$

Unit 3 Fully Differential op amp

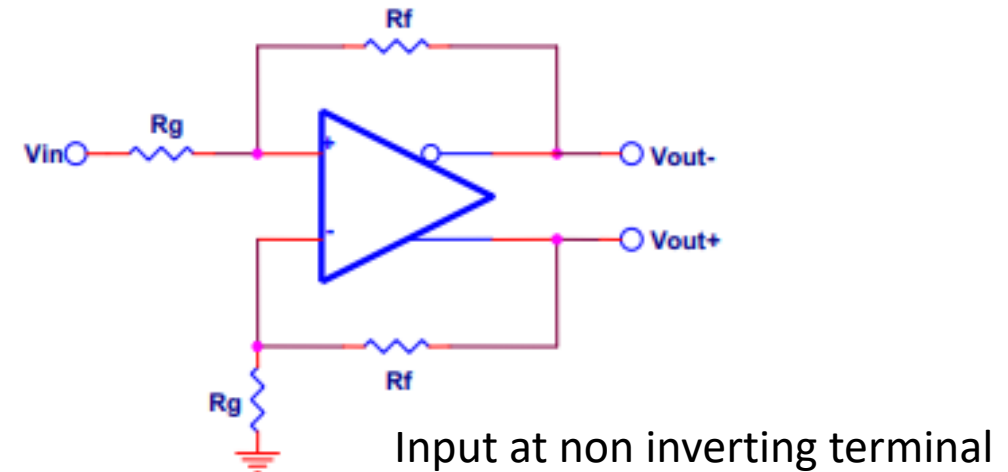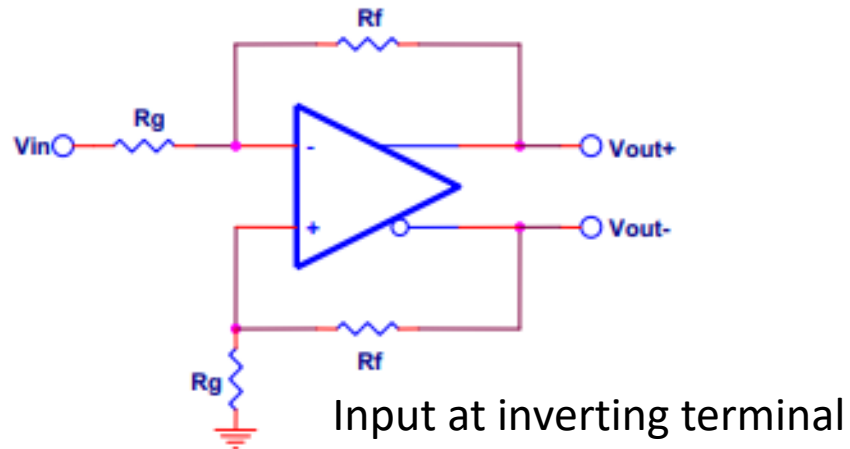- **Single Ended to Differential Conversion**
- *In some applications, it is necessary to have two output, which can be derived from single input*



- Gain of single ended to differential is

$$\frac{V_O}{V_I} = \frac{R_F}{R_G}$$

- In many cases, fully differential output is expressed as $(V_{out+} - V_{out-})$

Unit 3 Fully Differential op amp

- Single Ended to Differential Conversion
 - Gain plot when R_F is equal to R_G that is when gain is one.

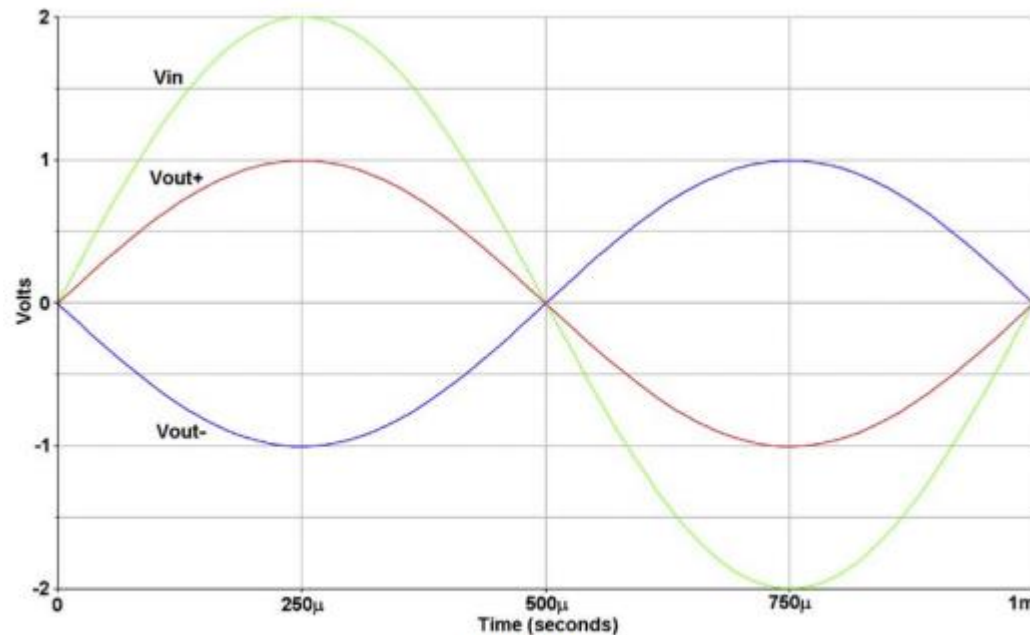


Figure 11.6
Relationship between V_{IN} , V_{OUT+} , and V_{OUT-} .

- Value of differential gain is always equal to one which is
- $V_{IN} = V_{OUT+} - V_{OUT-}$

Unit 3 Fully Differential op amp

- Concept of V_{OCM}
 - A new pin is added called V_{OCM}
 - V_{OCM} is called voltage output common mode
 - This sets output common mode voltage, output voltage swings with reference to this voltage
 - This is specific to TI chips

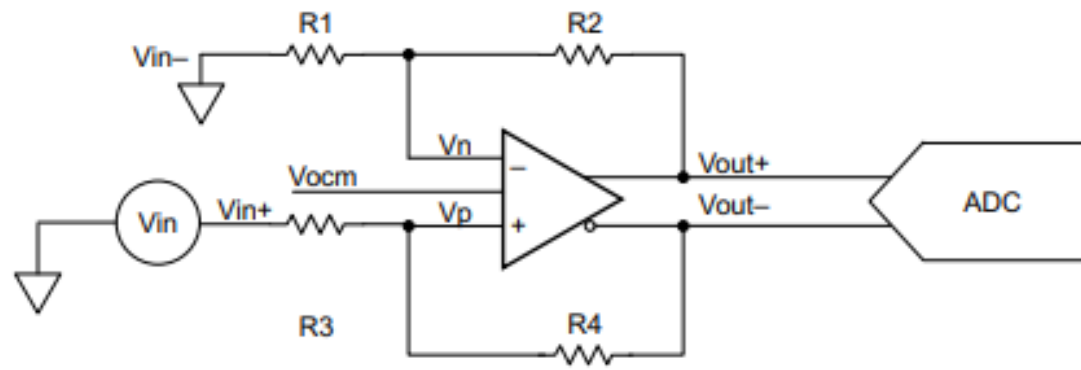


Figure 11.7
Electrical model of V_{ocm} .

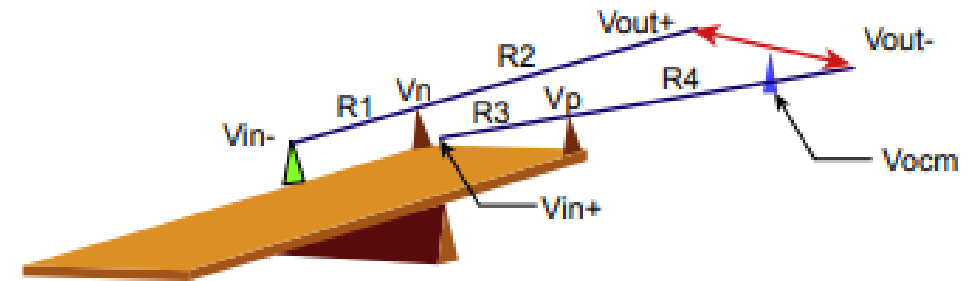


Figure 11.8
Mechanical model of V_{ocm} .

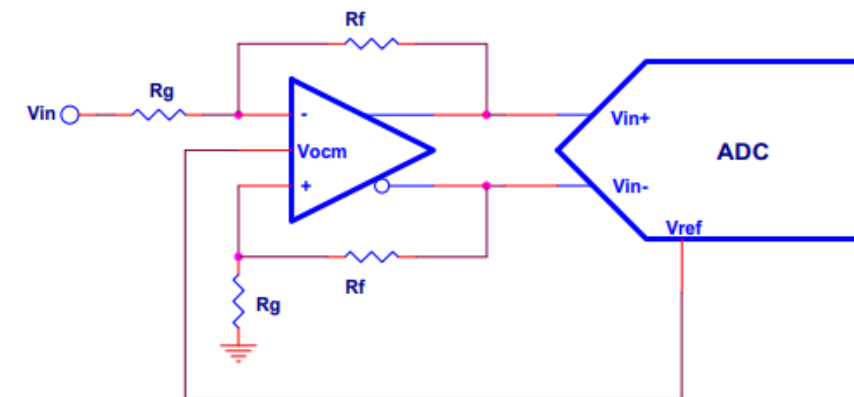


Figure 11.10
Using a fully differential op amp to drive an analog-to-digital converter

Unit 3 Fully Differential op amp

- Instrumentation amplifier

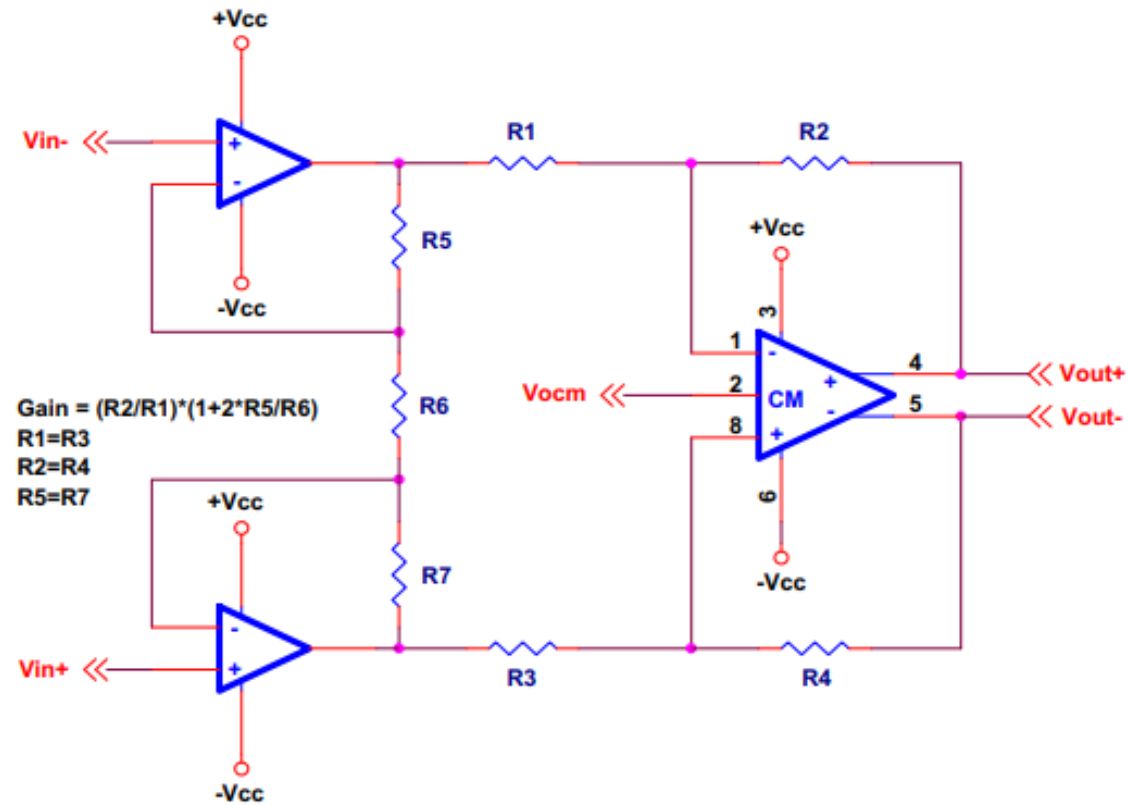


Figure 11.11
Instrumentation amplifier.

Instrumentation amplifier with V_{OCM} concept at second stage

Unit 3 Fully Differential op amp

- Differential low pass filter

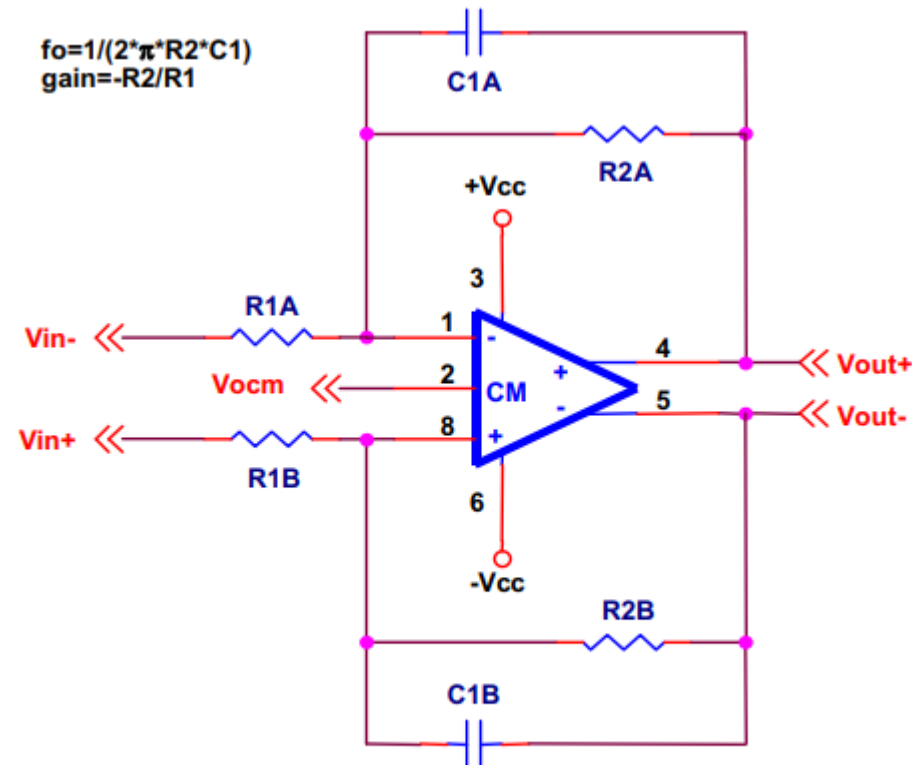


Figure 11.12
Single-pole differential low-pass filter.

Unit 3 Fully Differential op amp

- Differential high pass filter


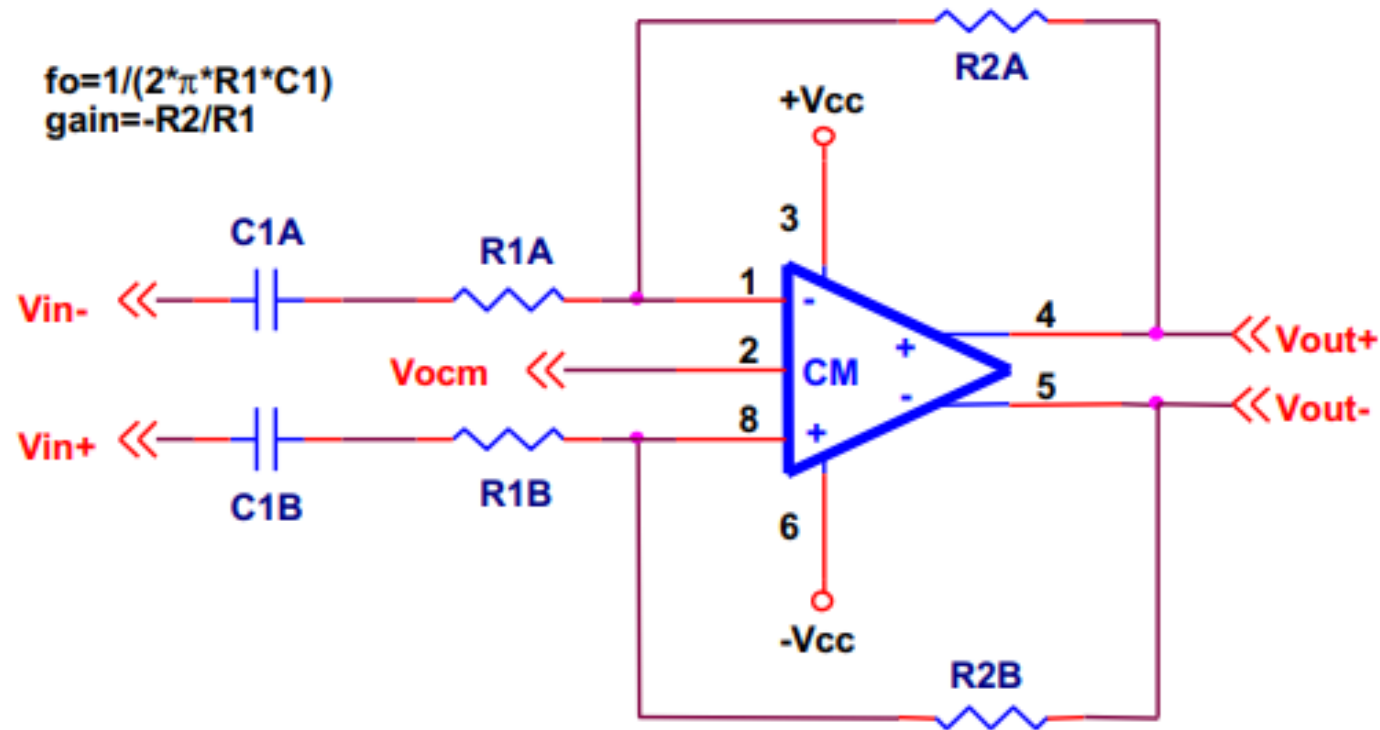



Figure 11.13
Single-pole differential high-pass filter.

Unit 3 Op Amp Noise Theory

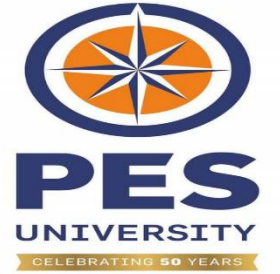

- Noise is a purely random signal
- Instantaneous value can not be predicted at any point of time
- Noise is created either internally or externally
- Instantaneous values are either positive voltage or negative voltage
- These can be plotted as Gaussian probability function
- Noise types Thermal noise and shot noise follow Gaussian function

Unit 3 Op Amp Noise Theory

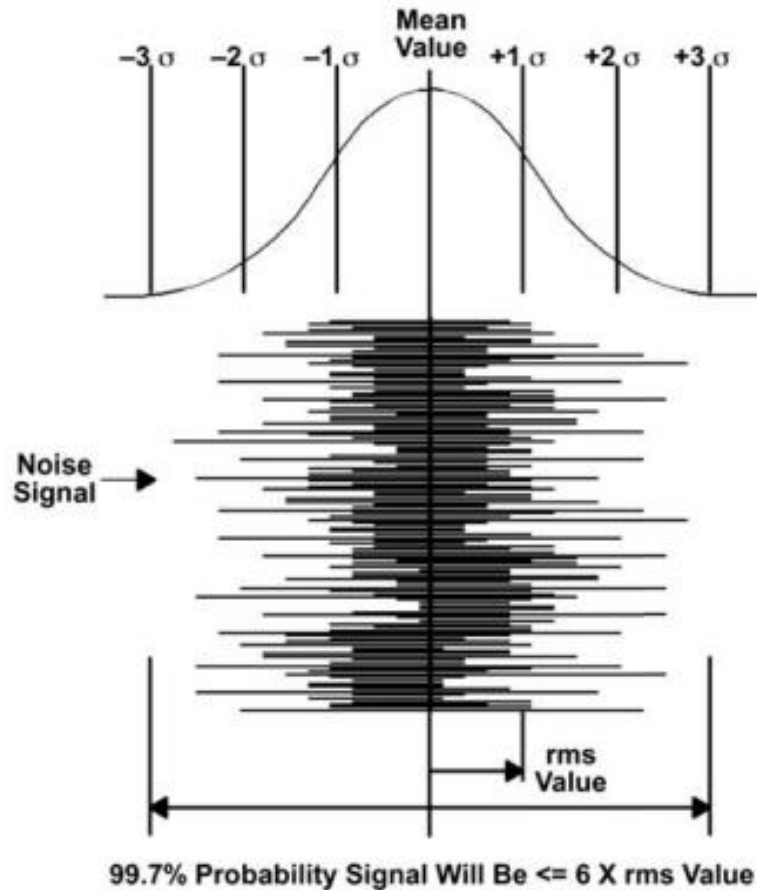


- σ is the standard deviation and it is root mean square value of noise current or voltage

$$X_n = \left(\frac{1}{T} \int_0^T x_n^2(t) dt \right)^{1/2}$$

noise voltage or current $x_n(t)$

Noise floor is the level of noise when there is no input given

Unit 3 Op Amp Noise Theory

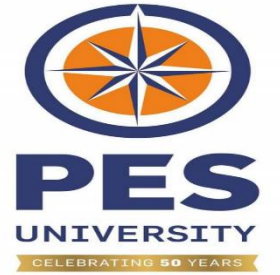

- Signal to Noise Ratio

$$\frac{S_{(f)}}{N_{(f)}} = \frac{\text{rms signal voltage}}{\text{rms noise voltage}}$$

- When there are multiple noise sources, total noise will be

$$E_{\text{Total rms}} = \sqrt{e_{1 \text{ rms}}^2 + e_{2 \text{ rms}}^2 + \cdots e_{n \text{ rms}}^2}$$

- **Example 1**
- If two noise sources are 2V rms, total value will be

$$E_{\text{Total rms}} = \sqrt{2^2 + 2^2} = \sqrt{8} = 2.83 \text{ V}_{\text{rms}}$$

- **Example 2**
- If one noise source is 10V and another 1V rms, total value will be

$$E_{\text{Total rms}} = \sqrt{10^2 + 1^2} = \sqrt{108} = 10.05 \text{ V}_{\text{rms}}$$

- Higher noise source dominates

Unit 3 Op Amp Noise Theory

- **Noise Units**

Normally expressed as rms volts(amps) per root hertz


$$V / \sqrt{\text{Hz}} \text{ or } A / \sqrt{\text{Hz}}$$

- Usually noise measured over a frequency band

For example:

- An op amp with a noise specification of $2.5 \text{ nV} / \sqrt{\text{Hz}}$ is used over an audio frequency range of 20 Hz–20 kHz, with a gain of 40 dB. The output voltage is 0 dB V (1 V).

Unit 3 Op Amp Noise Theory

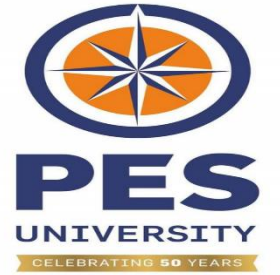

- To begin with, calculate the *root Hz* part: $\sqrt{20000 - 20} = 141.35$.
- Multiplying this by the noise spec: $2.5 \times 141.35 = 353.38 \text{ nV}$, which is the equivalent input noise (E_{IN}). The output noise equals the input noise multiplied by the gain, which is 100 (40 dB).


$$\text{Output noise} = \text{Gain} * \text{Input noise}$$

The signal-to-noise ratio can be now calculated:

$$353.38 \text{ nV} \times 100 = 35.3 \text{ } \mu\text{V}$$

$$\text{Signal-to-noise(dB)} = 20 \times \log(1 \text{ V} \div 35.3 \text{ } \mu\text{V}) = 20 \times \log(28329) = 89 \text{ dB}$$

Unit 3 Op Amp Noise Theory

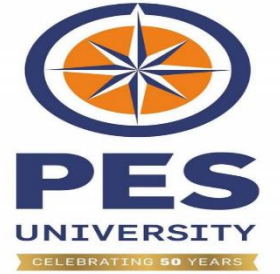


There are five types of noise in op amps and associated circuitry:

1. shot noise,
2. thermal noise,
3. flicker noise,
4. burst noise, and
5. avalanche noise.

Shot Noise

- Also called as **quantum** noise
- Caused by random movement of charge carriers in a conductor
- Few random electrons get energy and move randomly
- These noise independent of temperature
- These are always associated with current flow
- This noise is flat when plotted for spectral density
- They represent imperfections in a metal

Shot Noise

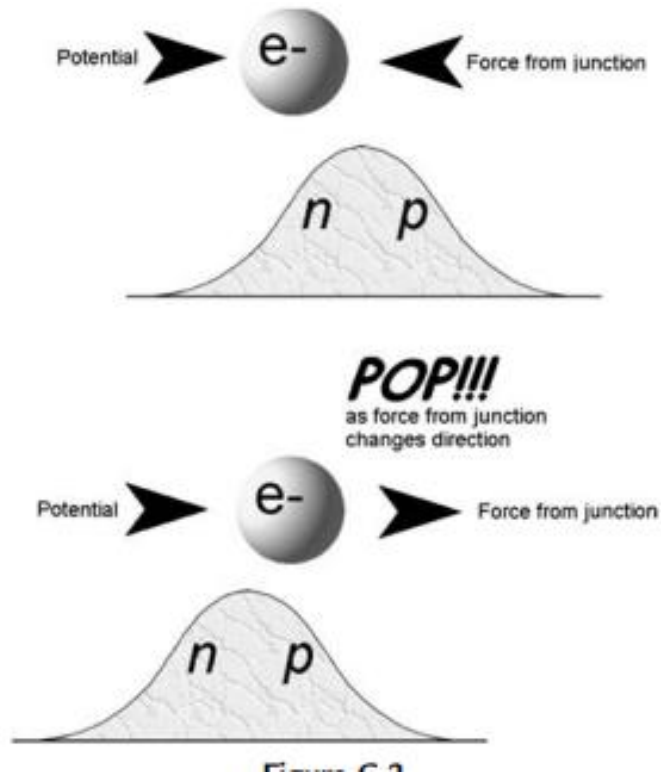

The rms shot noise current is equal to:

$$I_{sh} = \sqrt{(2qI_{dc} + 4qI_o)B}$$


where q = electron charge (1.6×10^{-19} C), I_{dc} = average forward dc current in A, I_o = reverse saturation current in A, and B = Bandwidth in Hz.

The rms shot noise voltage is equal to:

$$E_{sh} = kT \sqrt{\frac{2B}{qI_{dc}}}$$

where k is Boltzmann's constant (1.38×10^{-23} J/K); q is electron charge (1.6×10^{-19} C); T is temperature in K; I_{dc} is average dc current in A; and B is bandwidth in Hz.

Unit 3 Op Amp Noise Theory

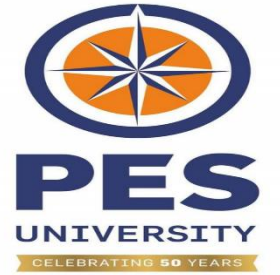

EXAMPLE 7.5. Find the signal-to-noise ratio for diode current over a 1-MHz bandwidth if (a) $I_D = 1 \mu\text{A}$ and (b) $I_D = 1 \text{ nA}$.

Solution.

$$(a) \quad I_n = \sqrt{2qI_D f_H} = \sqrt{2 \times 1.62 \times 10^{-19} \times 10^{-6} \times 10^6} = 0.57 \text{ nA (rms)}. \text{ Thus, SNR} = 20 \log_{10}[(1 \mu\text{A})/(0.57 \text{ nA})] = 64.9 \text{ dB}.$$

Thermal Noise

- Also called as Johnson's noise
- It is due to thermal agitation of electrons
- It has uniform spectral density

At frequencies below 100 MHz, thermal noise can be calculated using Nyquist's relation:

$$E_{th} = \sqrt{4kTRB}$$

$$I_{th} = \sqrt{\frac{4kTB}{R}}$$

where E_{th} is thermal noise voltage in volts rms; I_{th} is thermal noise current in amps rms; k is Boltzmann's constant (1.38×10^{-23}); T is absolute temperature in Kelvin; R is resistance in ohms; and B is noise bandwidth in Hertz ($f_{max} - f_{min}$).

EXAMPLE 7.4. Consider a 10-k Ω resistor at room temperature. Find (a) its voltage and (b) current spectral densities, and (c) its rms noise voltage over the audio range.


Solution.

$$(a) \quad e_R = \sqrt{4kTR} = \sqrt{1.65 \times 10^{-20} \times 10^4} = 12.8 \text{ nV}/\sqrt{\text{Hz}}$$

$$(b) \quad i_R = e_R/R = 1.28 \text{ pA}/\sqrt{\text{Hz}}$$

$$(c) \quad E_R = e_R \sqrt{f_H - f_L} = 12.8 \times 10^{-9} \times \sqrt{20 \times 10^3 - 20} = 1.81 \text{ } \mu\text{V}$$

Thermal Noise

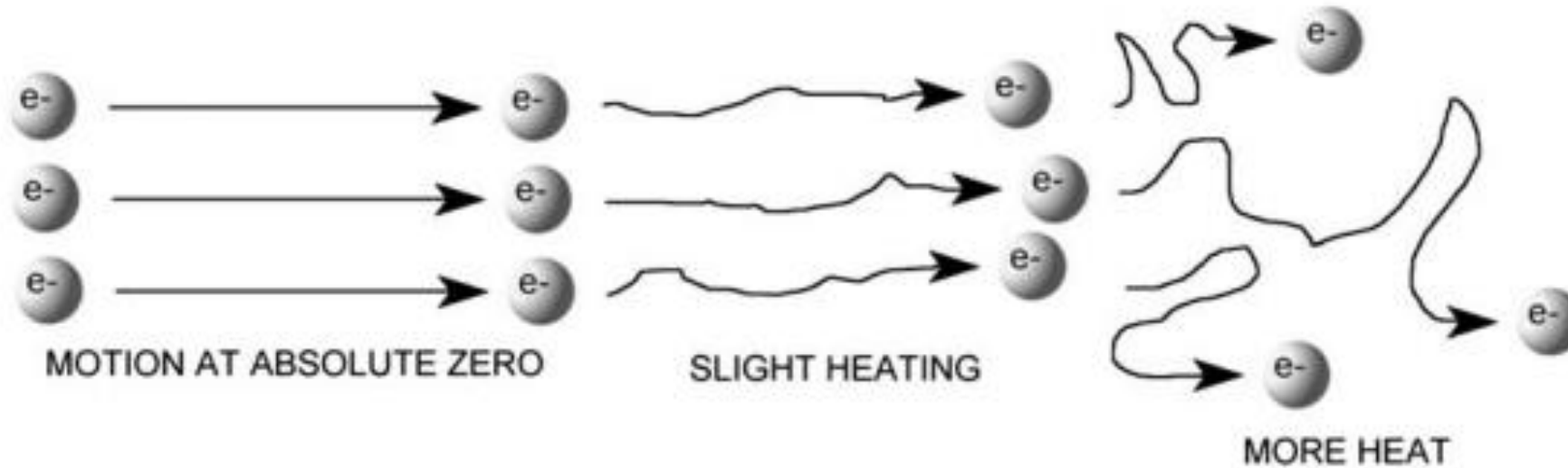

Lowering temperature reduces thermal noise

Flicker Noise

- Also called as 1/f noise
- It is present in all active and passive elements
- It is in crystal structure this can be reduced by better structure
- This noise Increases with decrease in frequency
- It is associated with DC currents

$$E_n = K_e \sqrt{\left(\ln \frac{f_{\max}}{f_{\min}} \right)} \quad I_n = K_i \sqrt{\left(\ln \frac{f_{\max}}{f_{\min}} \right)}$$

where K_e and K_i are proportionality constants (volts or amps) representing E_n and I_n at 1 Hz; and f_{\max} and f_{\min} are the maximum and minimum frequencies in Hz.

Burst Noise


- Also called as popcorn noise
- It is characterised by high frequency pulses
- It's amplitude is several times the thermal noise
- Can be heard at frequency in around 100hertz in a speaker

White Noise

White noise is characterized by a uniform spectral density, or $e_n = e_{nw}$ and $i_n = i_{nw}$, where e_{nw} and i_{nw} are suitable constants. It is so called by analogy with white light, which consists of all visible frequencies in equal amounts. When played through a loudspeaker, it produces a waterfall sound.

Avalanche Noise

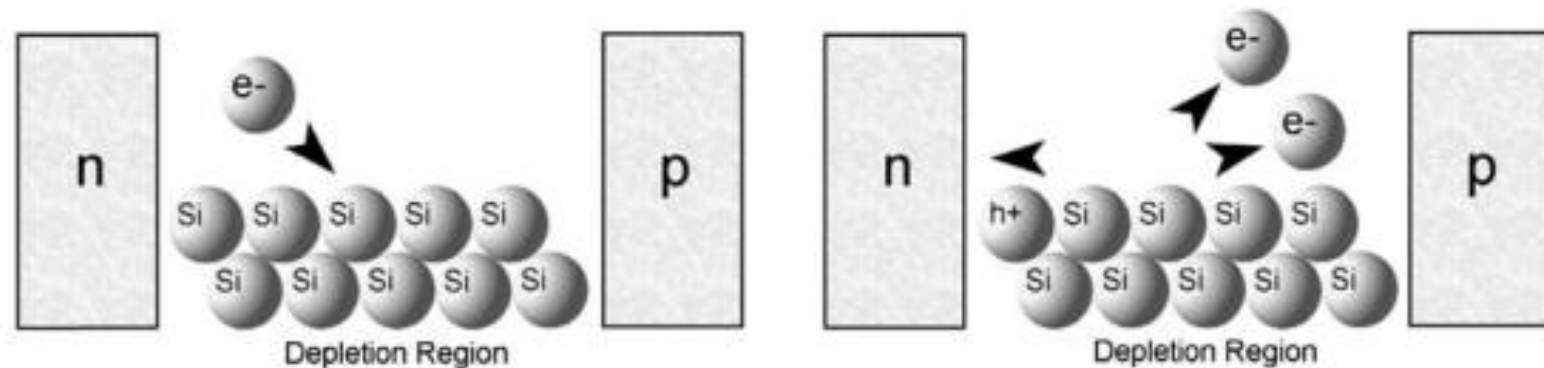- Occurs at p n junction area
- Occurs when strong reverse field is applied to the junction
- Electrons will get kinetic energy and move, resulting in a current




Noise Colours

- Colours describe type of noise and its frequency dependency

Table C.1: Noise Colors.


Color	Frequency Content
Purple	f^2
Blue	f
White	1
Pink	$\frac{1}{f}$
Red/brown	$\frac{1}{f^2}$

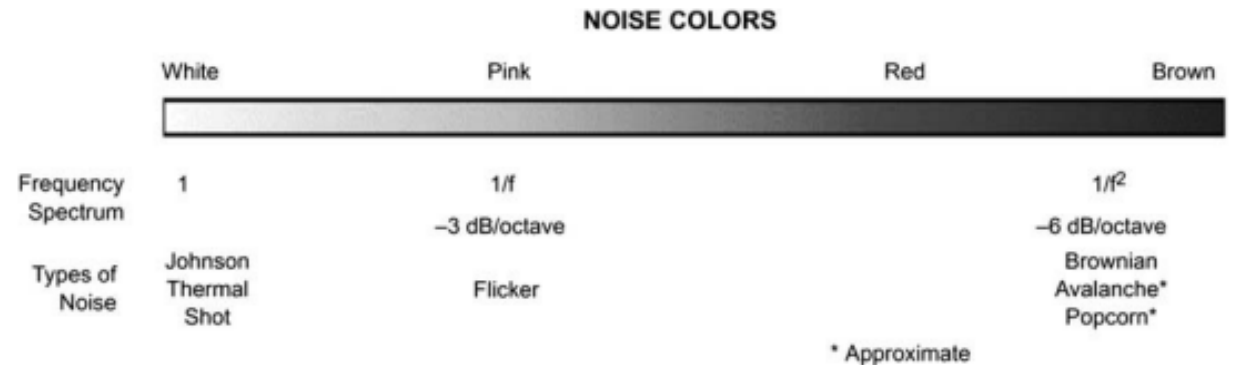

Unit 3 Op Amp Noise Theory

Op amp Noise

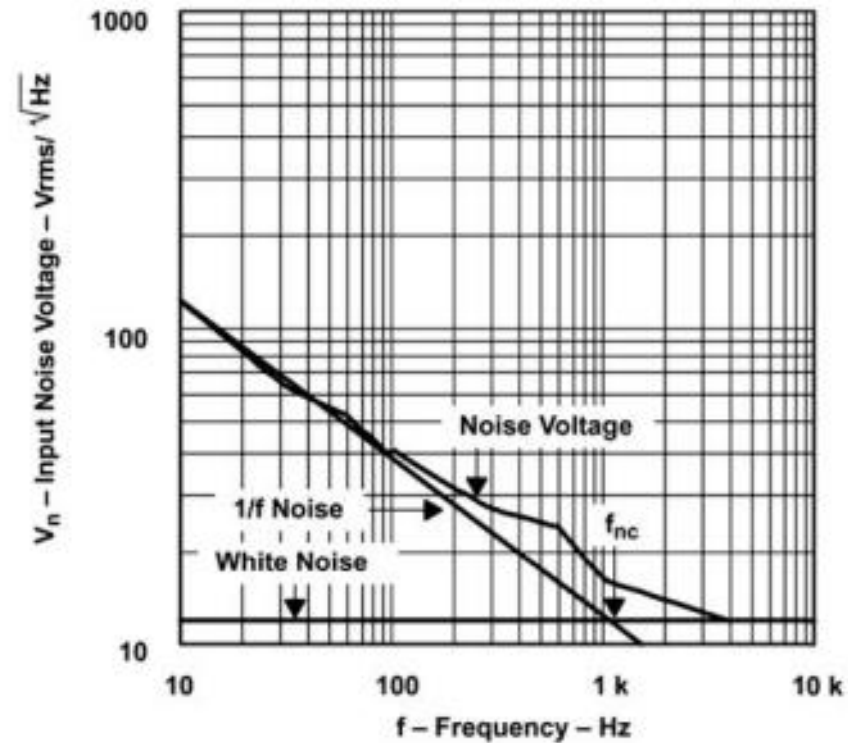
- Op amp noise described in a graph
- At low frequency, it is $1/f$ noise
- At high frequency, it is white noise



Unit 3 Op Amp Noise Theory


Op amp Noise

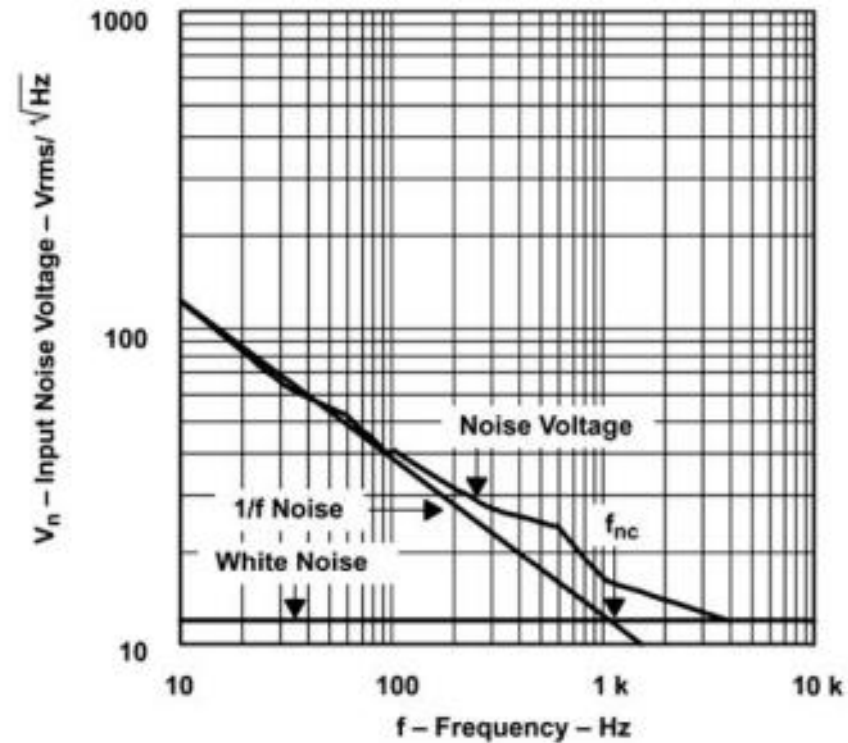- The point where $1/f$ noise is same as white noise is called **noise corner frequency**



Unit 3 Op Amp Noise Theory

Op amp noise model

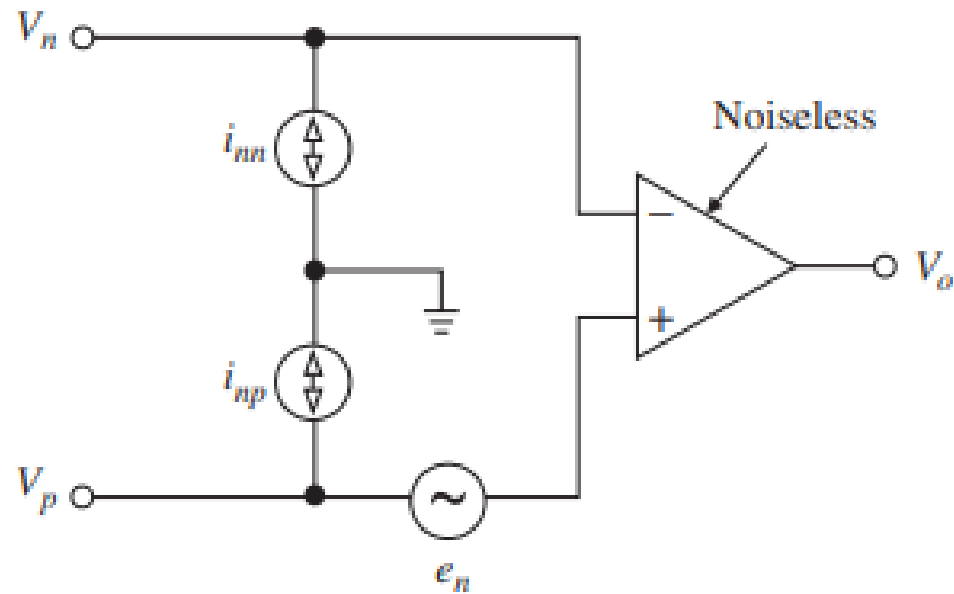

Reference:

Op Amp for Everyone : Bruce Carter and Ron Mancini Fifth
Edition 2017

Design with operational amplifiers and analogue integrated circuits
by Sergio Franco



THANK YOU

Dr Shashidhar Tantry

Electronics & Communication
Engineering

stantry@pes.edu