

# LINEAR INTEGRATED CIRCUITS

---

**Dr Shashidhar Tantry**

Electronics and Communication Engineering


## Unit 2 Simultaneous equations with $m < 1$

- Linear op amp transfer function is limited to equation of straight line  $y = +/-mx +/- b$

**Table 5.1: The Gain and Offset Matrix**

		$b < 0$	$b = 0$	$b > 0$
Noninverting	$m > 1$	Case 2 (Section 4.4.2)	Noninverting gain (Section 2.3)	Case 1 (Section 4.4.1)
	$m = 1$	Section 5.4	Noninverting buffer (Section 5.7)	
	$m < 1$		Section 5.2	Section 5.3
	$m = 0$	Negative reference or regulator (Chapter 21)	Ground	Positive reference or regulator (Chapter 20)
Inverting	$m < -1$	Section 5.7	Section 5.5	Section 5.6
	$m \geq -1$	Case 4 (Section 4.4.4)	Inverting gain (Section 2.4)	Case 3 (Section 4.4.3)

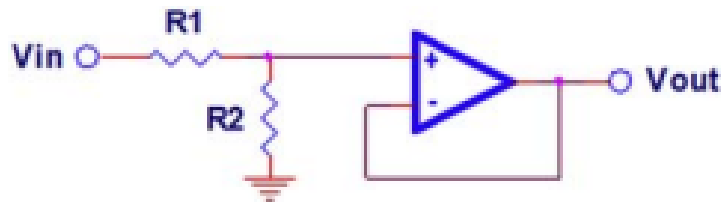
## Unit 2 Non inverting attenuator with zero offset, positive offset and negative offset



$$V_{out} = m \times V_{in}$$

$$m = \frac{R_2}{R_1 + R_2}$$

**Zero offset**

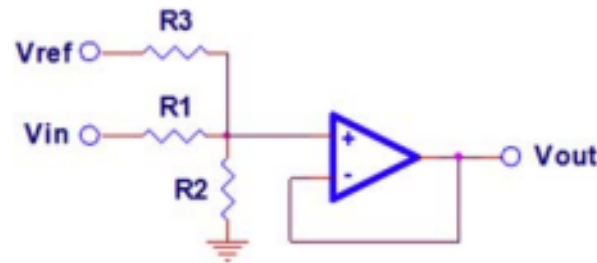


$$V_{out} = m \times V_{in} + b$$

$$m = \frac{1/R_1}{1/R_1 + 1/R_2 + 1/R_3}$$


$$b = V_{ref} \times \frac{1/R_3}{1/R_1 + 1/R_2 + 1/R_3}$$

**Positive offset**

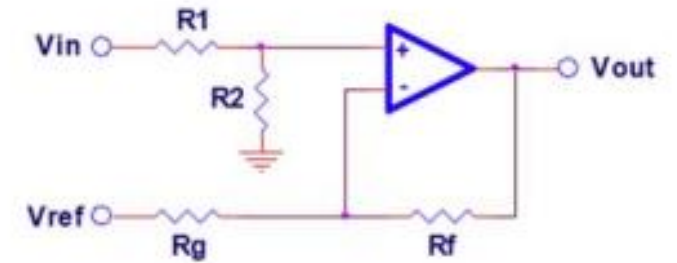


**Negative offset**
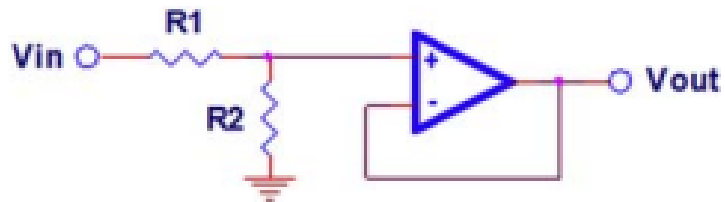
## Unit 2 Non inverting attenuator with zero offset, positive offset and negative offset




$$V_{out} = m \times V_{in}$$
$$m = \frac{R_2}{R_1 + R_2}$$

**Zero offset**

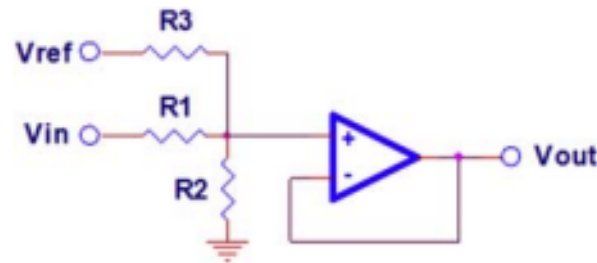

$$V_{out} = m \times V_{in} + b$$
$$m = \frac{1/R_1}{1/R_1 + 1/R_2 + 1/R_3}$$
$$b = V_{ref} \times \frac{1/R_3}{1/R_1 + 1/R_2 + 1/R_3}$$


**Positive offset**

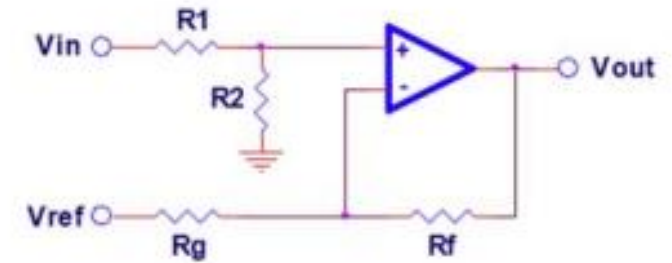


$$V_{out} = m \times V_{in} - b$$
$$m = \left( \frac{R_2}{R_1 + R_2} \right) \times \left( 1 + \frac{R_f}{R_g} \right)$$
$$b = V_{ref} \times \frac{R_f}{R_g}$$

**Negative offset**
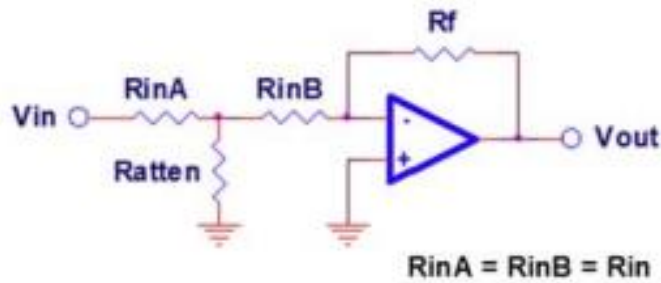
## Unit 2 Inverting attenuator with zero offset, positive offset and negative offset



Zero offset

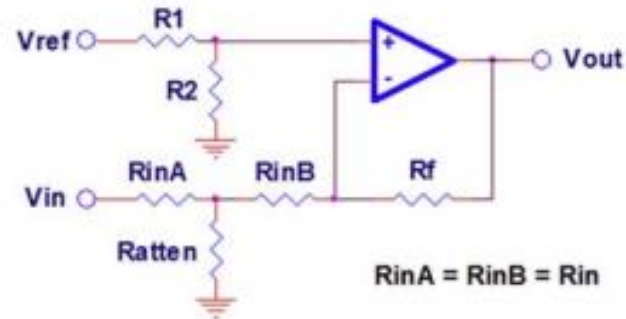


$$V_{out} = -m \times V_{in} + b$$

$$m = \frac{R_f \times R_{atten}}{R_{in} \times (R_{in} + 2 \times R_{atten})}$$


$$b = V_{ref} \times \left( \frac{R_2}{R_1 + R_2} \right) \times \left( 1 + \frac{R_f}{R_{in} + R_{in} \parallel R_{atten}} \right)$$

Positive offset

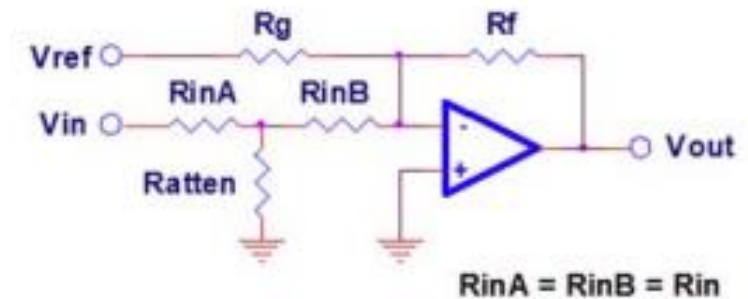

Negative offset

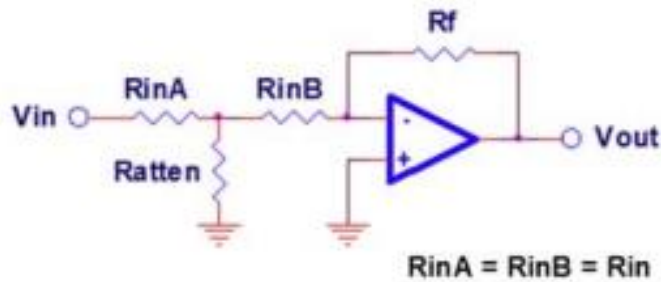
## Unit 2 Inverting attenuator with zero offset, positive offset and negative offset



$$V_{out} = -m \times V_{in}$$

$$m = \frac{R_f \times R_{atten}}{R_{in} \times (R_{in} + 2 \times R_{atten})}$$

**Zero offset**

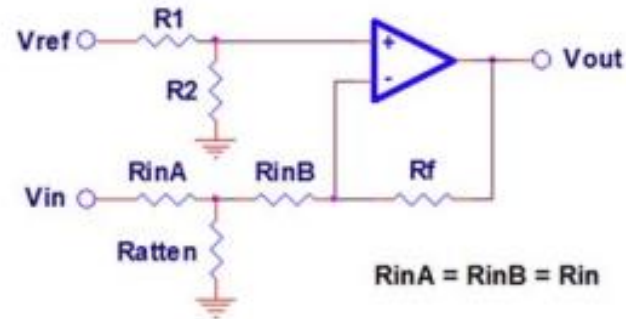


$$V_{out} = -m \times V_{in} + b$$

$$m = \frac{R_f \times R_{atten}}{R_{in} \times (R_{in} + 2 \times R_{atten})}$$

$$b = V_{ref} \times \left( \frac{R_2}{R_1 + R_2} \right) \times \left( 1 + \frac{R_f}{R_{in} + R_{in} \parallel R_{atten}} \right)$$

**Positive offset**

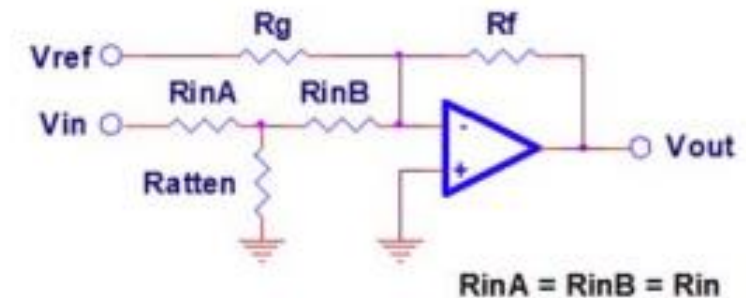

$$V_{out} = -m \times V_{in} - b$$


$$m = \frac{R_f \times R_{atten}}{R_{in} \times (R_{in} + 2 \times R_{atten})}$$

$$b = V_{ref} \times \frac{R_f}{R_g}$$

**Negative offset**


## Unit 2 Development of non ideal op amp equations

---

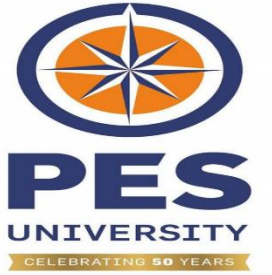

- Concept of DC errors and AC errors
- Inaccuracies can be minimized using negative feedback
- Stability is usually an criteria when operating frequency is high
- Internally compensated and externally compensated to improve stability

## Unit 2 Development of non ideal op amp equations

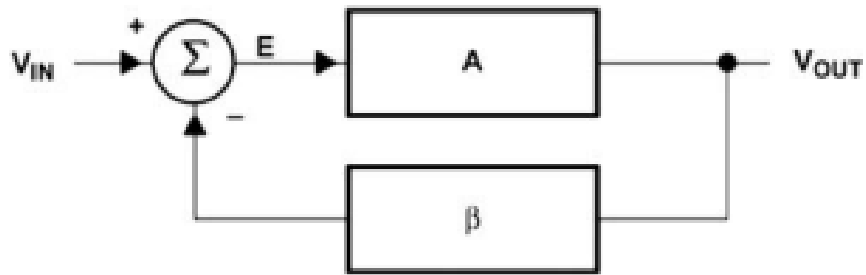


**Figure 7.1**  
Feedback system block diagram.
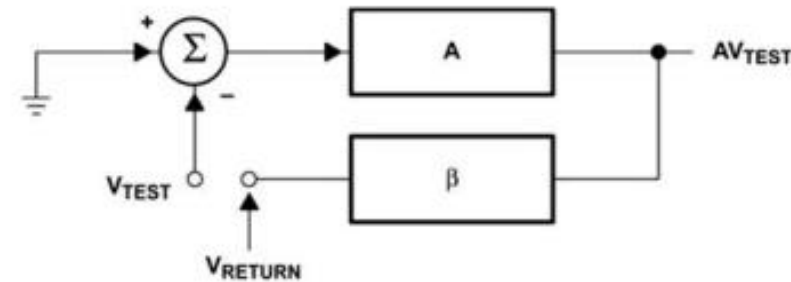
$$\frac{V_{OUT}}{V_{IN}} = \frac{A}{1 + A\beta}$$

When loop gain is large,

$$\frac{V_{OUT}}{V_{IN}} = \frac{1}{\beta}$$



$$\frac{V_{RETURN}}{V_{TEST}} = A\beta$$

**Figure 7.2**  
Feedback loop broken to calculate loop gain.

Error indicator, proportional to signal and inversely proportional to loop gain

$$E = \frac{V_{IN}}{1 + A\beta}$$



## Unit 2 Development of non ideal op amp equations Non Inverting amp

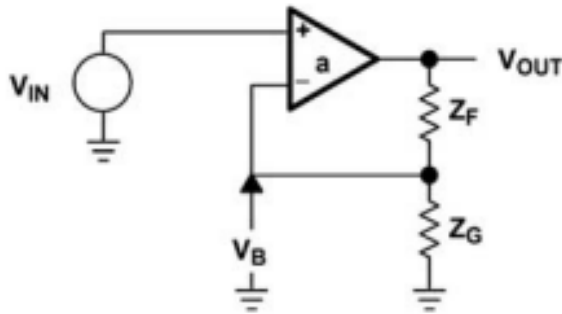


Figure 7.3  
Noninverting op amp.

amplifier transfer equation.

$$V_{OUT} = a(V_{IN} \pm V_B) \quad \text{----- 1}$$

$V_B$  calculated based on resistor divider from  $V_{OUT}$

$$V_B = \frac{V_{OUT} Z_G}{Z_F + Z_G} \text{ for } I_B = 0 \quad \text{----- 2}$$

From 1 and 2,

$$V_{OUT} = aV_{IN} - \frac{aZ_G V_{OUT}}{Z_G + Z_F}$$

After simplification,


$$\frac{V_{OUT}}{V_{IN}} = \frac{a}{1 + \frac{aZ_G}{Z_G + Z_F}}$$

In the form of closed loop function,

$$\frac{V_{OUT}}{V_{IN}} = \frac{A}{1 + A\beta}$$

loop gain  $\rightarrow A\beta = \frac{aZ_G}{Z_G + Z_F}$

## Unit 2 Development of non ideal op amp equations Non Inverting amp

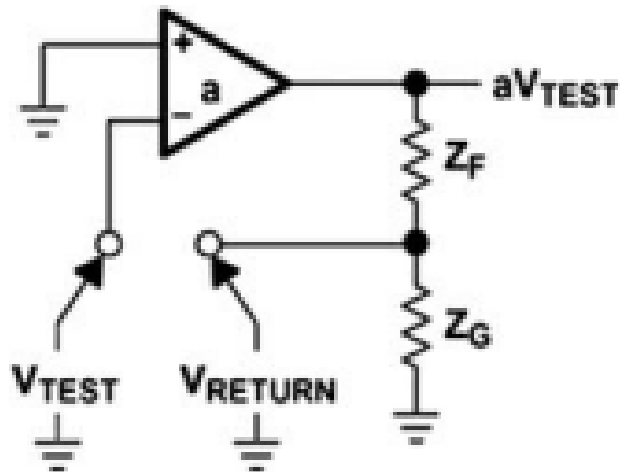


**Figure 7.4**

Open-loop noninverting op amp.

$$V_{\text{RETURN}} = \frac{aV_{\text{TEST}}Z_G}{Z_F + Z_G}$$
$$\frac{V_{\text{RETURN}}}{V_{\text{TEST}}} = A\beta = \frac{aZ_G}{Z_F + Z_G}$$

For measurement, break the loop, apply test signal at one end and measure voltage at the other end

## Unit 2 Development of non ideal op amp equations Inverting amp

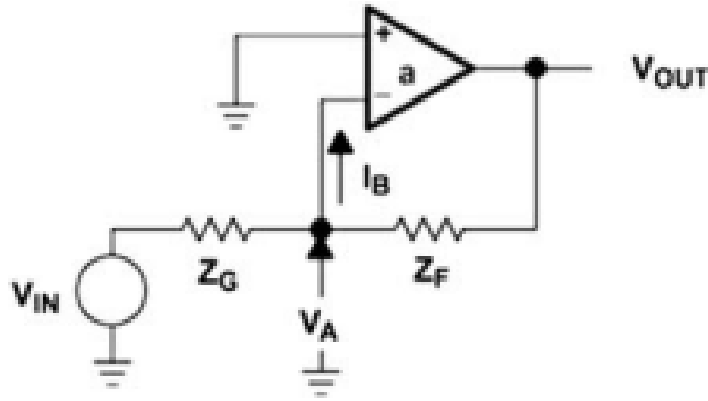

**Figure 7.5**  
Inverting op amp.

$$V_{OUT} = -aV_A$$

$$V_A = \frac{V_{IN}Z_F}{Z_G + Z_F} + \frac{V_{OUT}Z_G}{Z_G + Z_F} \text{ for } I_B = 0$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{\frac{-aZ_F}{Z_G + Z_F}}{1 + \frac{aZ_G}{Z_G + Z_F}}$$

open loop gain

loop gain

- Open loop gain is different compared to non inverting amp
- Loop gain is same compared to non inverting amp

## Unit 2 Development of non ideal op amp equations Inverting amp

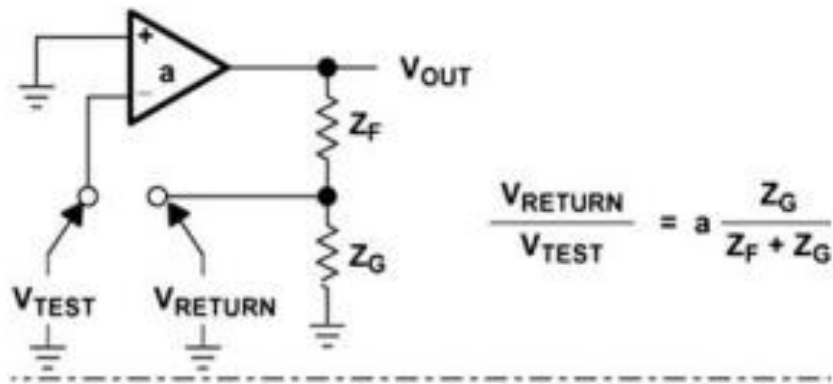



Figure 7.6

Inverting op amp: feedback loop broken for loop gain calculation.

$$\frac{V_{RETURN}}{V_{TEST}} = \frac{aZ_G}{Z_G + Z_F} = A\beta$$

For measurement, break the loop, apply test signal at one end and measure voltage at the other end

## Unit 2 Development of non ideal op amp equations Differential amp

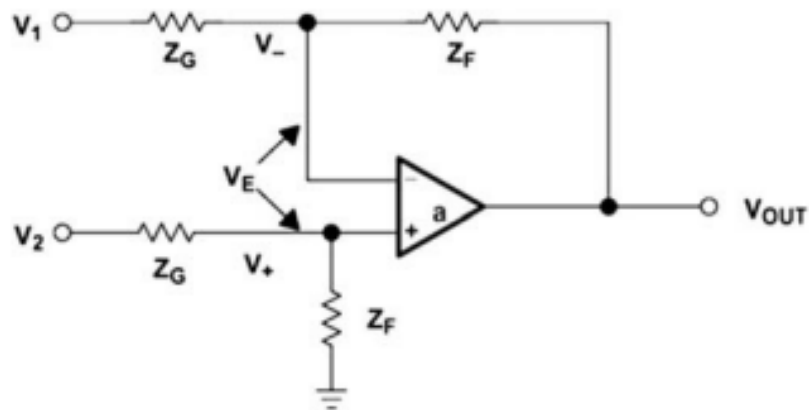

**Figure 7.7**  
Differential amplifier circuit.

$$V_+ = V_2 \frac{Z_F}{Z_F + Z_G}$$

$$V_- = V_1 \frac{Z_F}{Z_F + Z_G} - V_{OUT} \frac{Z_G}{Z_F + Z_G}$$

: transfer equation.

$$V_{OUT} = aV_E = V_+ \pm V_-$$

$$V_{OUT} = a \left[ \frac{V_2 Z_F}{Z_F + Z_G} - \frac{V_1 Z_F}{Z_F + Z_G} - \frac{V_{OUT} Z_G}{Z_F + Z_G} \right]$$

## Unit 2 Development of non ideal op amp equations Differential amp

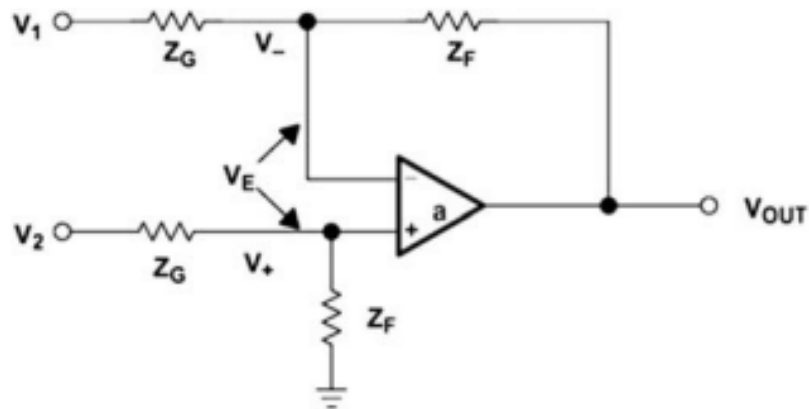


Figure 7.7  
Differential amplifier circuit.


open loop gain

$$\frac{V_{OUT}}{V_2 - V_1} = \frac{\frac{aZ_F}{Z_F + Z_G}}{1 + \frac{aZ_G}{Z_F + Z_G}}$$

loop gain

- Loop gain is same compared to non inverting amp and inverting amp

## Unit 2 Practical aspects

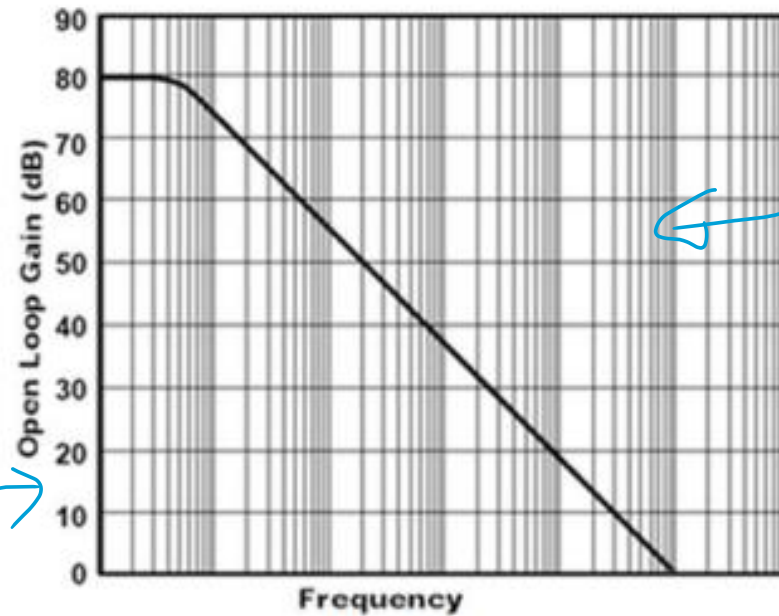

**Figure 7.8**  
Bode response of a typical op amp.

Operating  
Region

Not an operating  
region

## Unit 2 Practical aspects

noninverting op amp:

$$\frac{V_{OUT}}{V_{IN}} = \frac{a}{1 + \frac{aZ_G}{Z_G + Z_F}}$$

When open loop gain is high

when  $a \gg 1$ ,  $\frac{V_{OUT}}{V_{IN}} = 1 + \frac{Z_F}{Z_G}$

inverting op amp stage:

$$\frac{V_{OUT}}{V_{IN}} = \frac{\frac{-aZ_F}{Z_G + Z_F}}{1 + \frac{aZ_G}{Z_G + Z_F}}$$

When open loop gain is high

when  $a \gg 1$ ,  $\frac{V_{OUT}}{V_{IN}} = -\frac{Z_F}{Z_G}$



## Unit 2 Practical aspects

Table 7.1: Real Inverting Op Amp Stage Gains for  $a = 80$  dB

a	$R_G$	$R_F$	Attempted	Actual	Error (%)
10,000	100,000	100,000	-1	-0.9998	-0.0200
10,000	10,000	100,000	-10	-9.9890	-0.1099
10,000	1000	100,000	-100	-99.0001	-0.9999
10,000	100	100,000	-1000	-909.0083	-9.0992
10,000	10	100,000	-10,000	-4999.7500	-50.0025
10,000	1	100,000	-100,000	-9090.8264	-90.9092
10,000	1	1.00E + 12	-1E + 12	-9999.9999	-100

Table 7.2: Real Noninverting Op Amp Stage Gains for  $a = 80$  dB

a	$R_G$	$R_F$	Attempted	Actual	Error (%)
10,000	100,000	100,000	2	1.9996	-0.0200
10,000	10,000	100,000	11	10.9879	-0.1099
10,000	1000	100,000	101	99.9901	-0.9999
10,000	100	100,000	1001	909.9173	-9.0992
10,000	10	100,000	10,001	5000.2500	-50.0025
10,000	1	100,000	100,001	9090.9174	-90.9092
10,000	1	1.00E + 12	1E + 12	9999.9999	-100

Error is more for higher gain

## Unit 2 Practical aspects

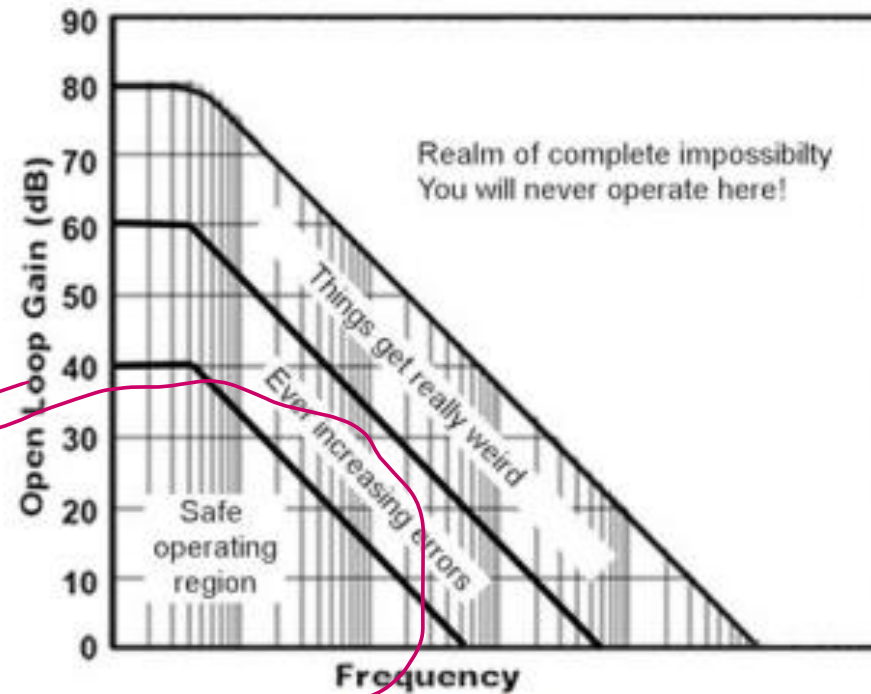


Figure 7.9


Bode response representation of safe operating region.

operating  
region

### Background

- Oscillations are considered as boundary between stability and non stability
- Poor stability circuit exhibits ringing and overshoot
- Phase margin is one measure for stability
- Compensation provides patch between stability and performance
- Compensation network is by RC network

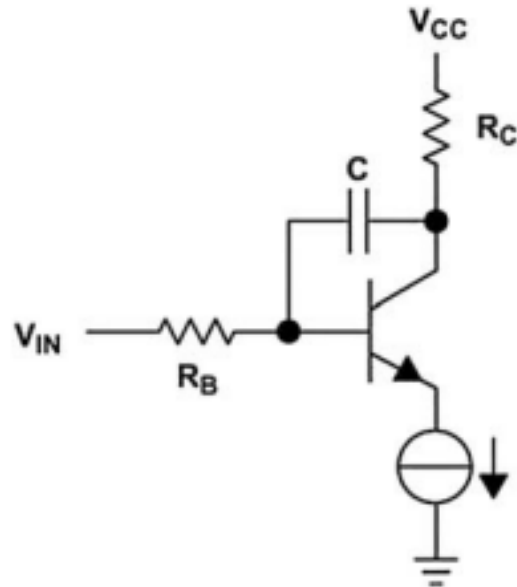
## Unit 2 Voltage feedback op amp compensation Internal compensation



A capacitor C connected between input and output for compensation, called internal compensation capacitor

Phase  
margin  
72°

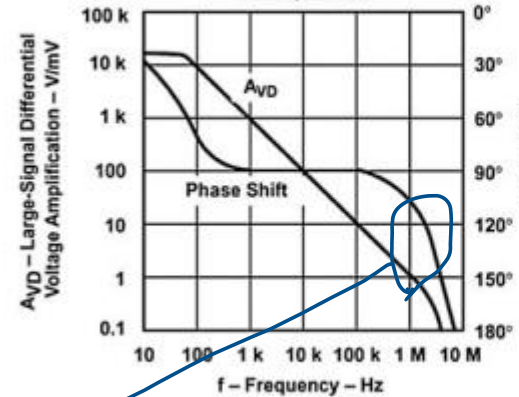
LARGE-SIGNAL DIFFERENTIAL VOLTAGE AMPLIFICATION AND PHASE SHIFT VS FREQUENCY



$V_{CC} \pm 15 \text{ V}$   $R_L = 10 \text{ k}\Omega$   
 $C_L = 25 \text{ pF}$   $T_A = 25^\circ\text{C}$

Plot of internally compensated op amp

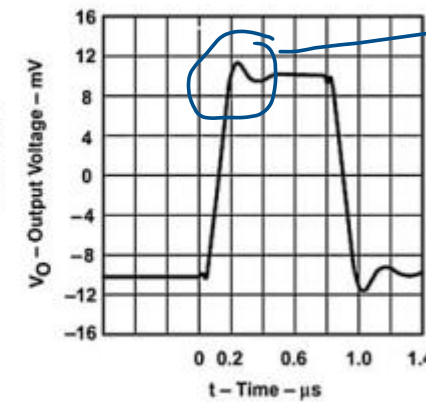VOLTAGE-FOLLOWER SMALL-SIGNAL PULSE RESPONSE



$V_{CC} \pm 15 \text{ V}$   $R_L = 10 \text{ k}\Omega$   
 $C_L = 100 \text{ pF}$   $T_A = 25^\circ\text{C}$

loading capacitor  
changes  
phase margin

overshoot  
10%

## Unit 2 Voltage feedback op amp compensation Internal compensation

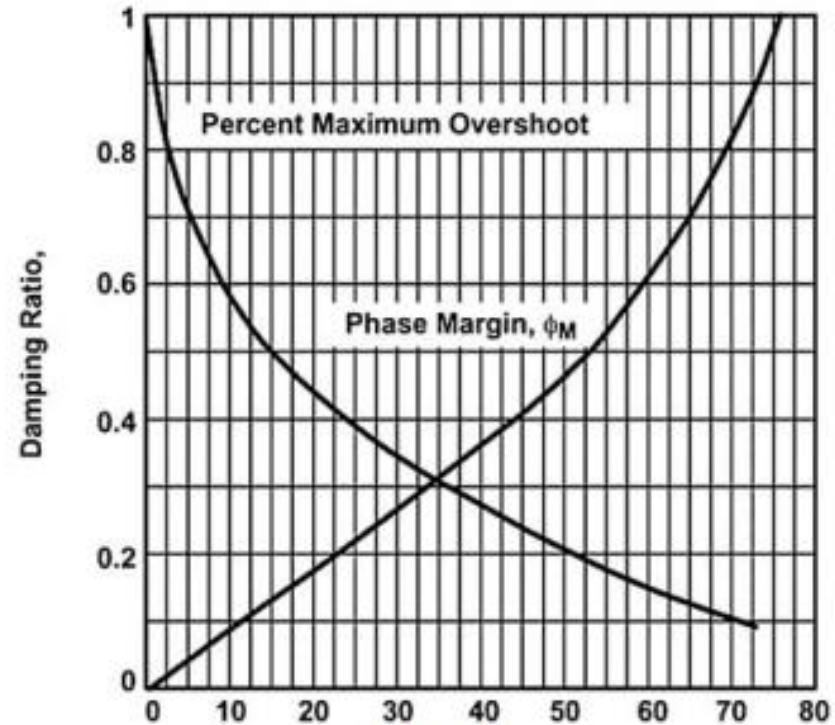
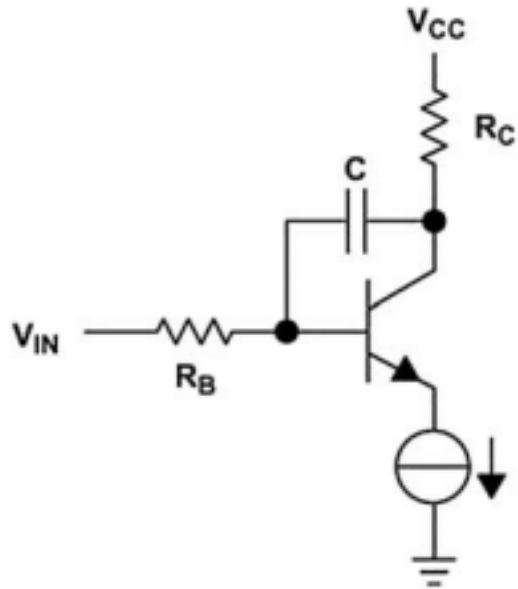



Figure 8.3

Phase margin and percent overshoot versus damping ratio.

Plot of internally compensated op amp, measure of phase margin with damping ratio and overshoot (Data sheet for TL03X)

## Unit 2 Importance of external compensation


---

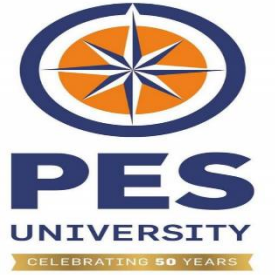


- High frequency noise reduction
- Improve phase margin
- Reduce overshoot
- Compensation can be tailored to the circuit requirement
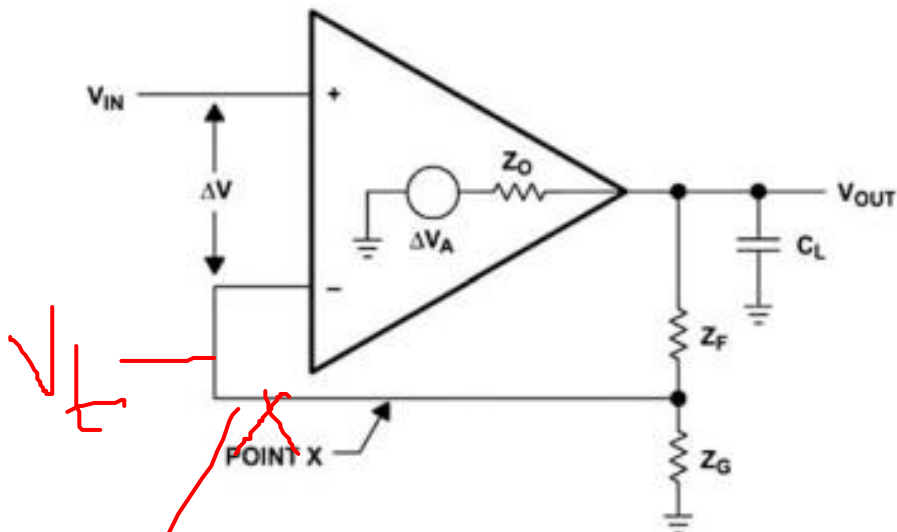
## Unit 2 Dominant pole compensation

- Output capacitor added
- Combination of output capacitor and output impedance forms dominant pole




Loop broken for loop gain calculations

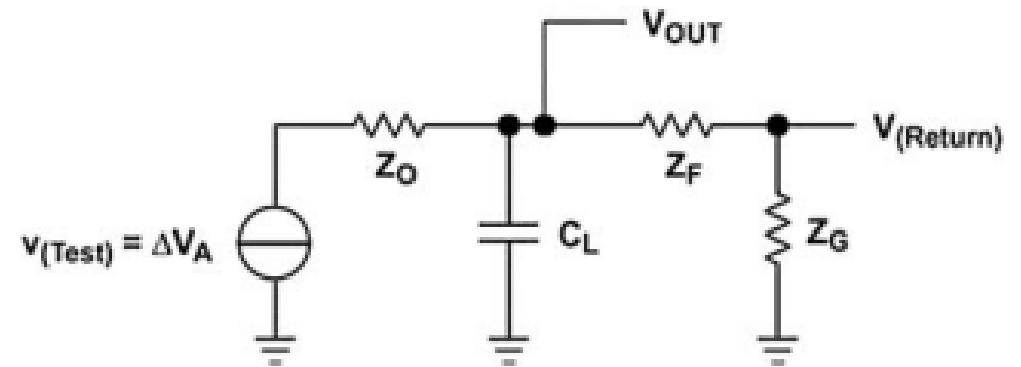

Equivalent circuit after loop break

## Unit 2 Dominant pole compensation

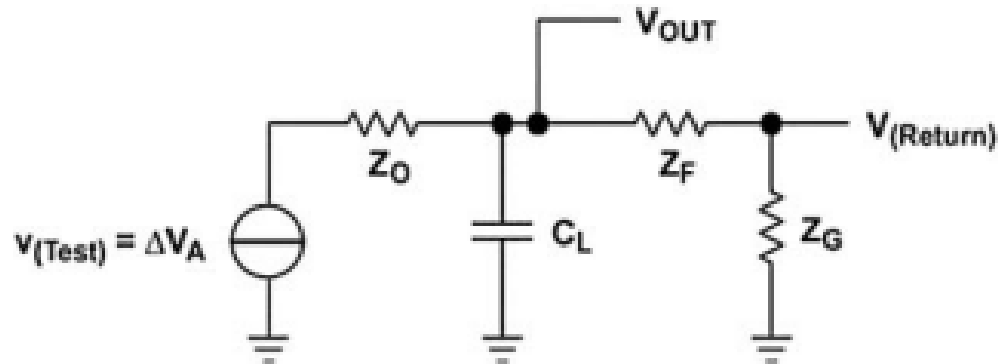


Apply Thevenin's theorem to separate  $Z_O$  and  $C_L$

$$V_{TH} = \frac{\Delta V_a}{Z_O C_L s + 1}$$

$$Z_{TH} = \frac{Z_O}{Z_O C_L s + 1}$$

Calculate  $V_{return}$  voltage
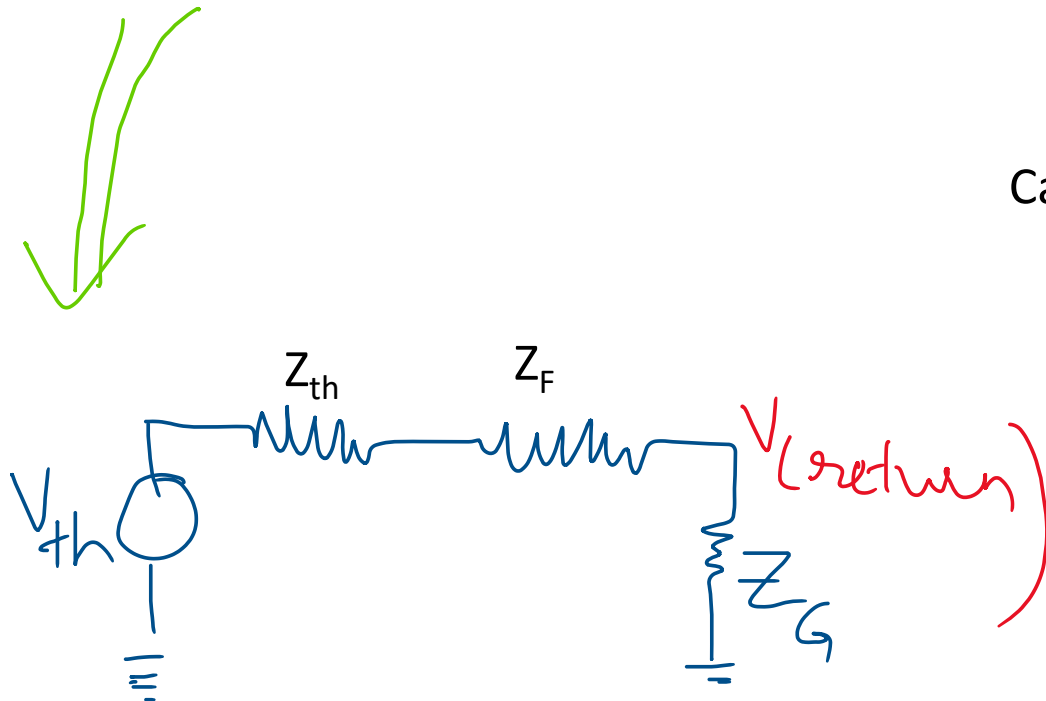
$$V_{RETURN} = \frac{V_{TH} Z_G}{Z_G + Z_F + Z_{TH}} = \frac{\Delta V_a}{Z_O C_L s + 1} \left( \frac{Z_G}{Z_F + Z_G + \frac{Z_O}{Z_O C_L s + 1}} \right)$$






## Unit 2 Dominant pole compensation

$$V_{\text{RETURN}} = \frac{V_{\text{TH}} Z_G}{Z_G + Z_F + Z_{\text{TH}}} = \frac{\Delta V_a}{Z_O C_L s + 1} \left( \frac{Z_G}{Z_F + Z_G + \frac{Z_O}{Z_O C_L s + 1}} \right)$$

Here  $\Delta V_a = a V_{\text{test}}$

*Rearranging*

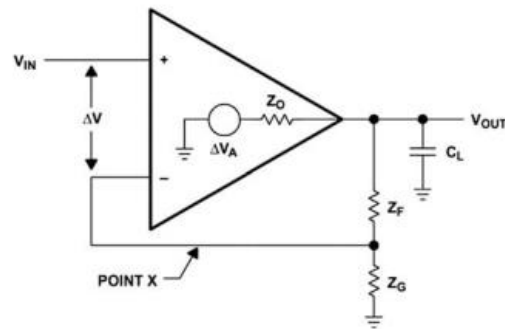


$$\frac{V_{\text{RETURN}}}{V_{\text{TEST}}} = A\beta = \frac{\frac{aZ_G}{Z_F + Z_G + Z_O}}{\frac{(Z_F + Z_G)Z_O C_L s}{Z_F + Z_G + Z_O} + 1}$$

When  $(Z_F + Z_O) \gg Z_O$

$$A\beta = \frac{aZ_G}{Z_F + Z_G} \left( \frac{1}{Z_O C_L s + 1} \right)$$

## Unit 2 Dominant pole compensation

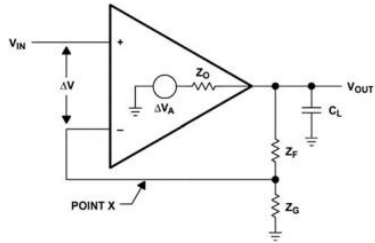

$$\frac{V_{\text{RETURN}}}{V_{\text{TEST}}} = A\beta = \frac{\frac{aZ_G}{Z_F + Z_G + Z_O}}{\frac{(Z_F + Z_G)Z_OC_Ls}{Z_F + Z_G + Z_O} + 1}$$

In case op-amp  
a second order system




$$a = \frac{K}{(s + \tau_1)(s + \tau_2)}$$

Loop gain is equal to


$$A\beta = \frac{K}{(s + \tau_1)(s + \tau_2)} \frac{Z_G}{Z_F + Z_G} \frac{1}{Z_OC_Ls + 1}$$

If is a three pole  
System

## Unit 2 Dominant pole compensation

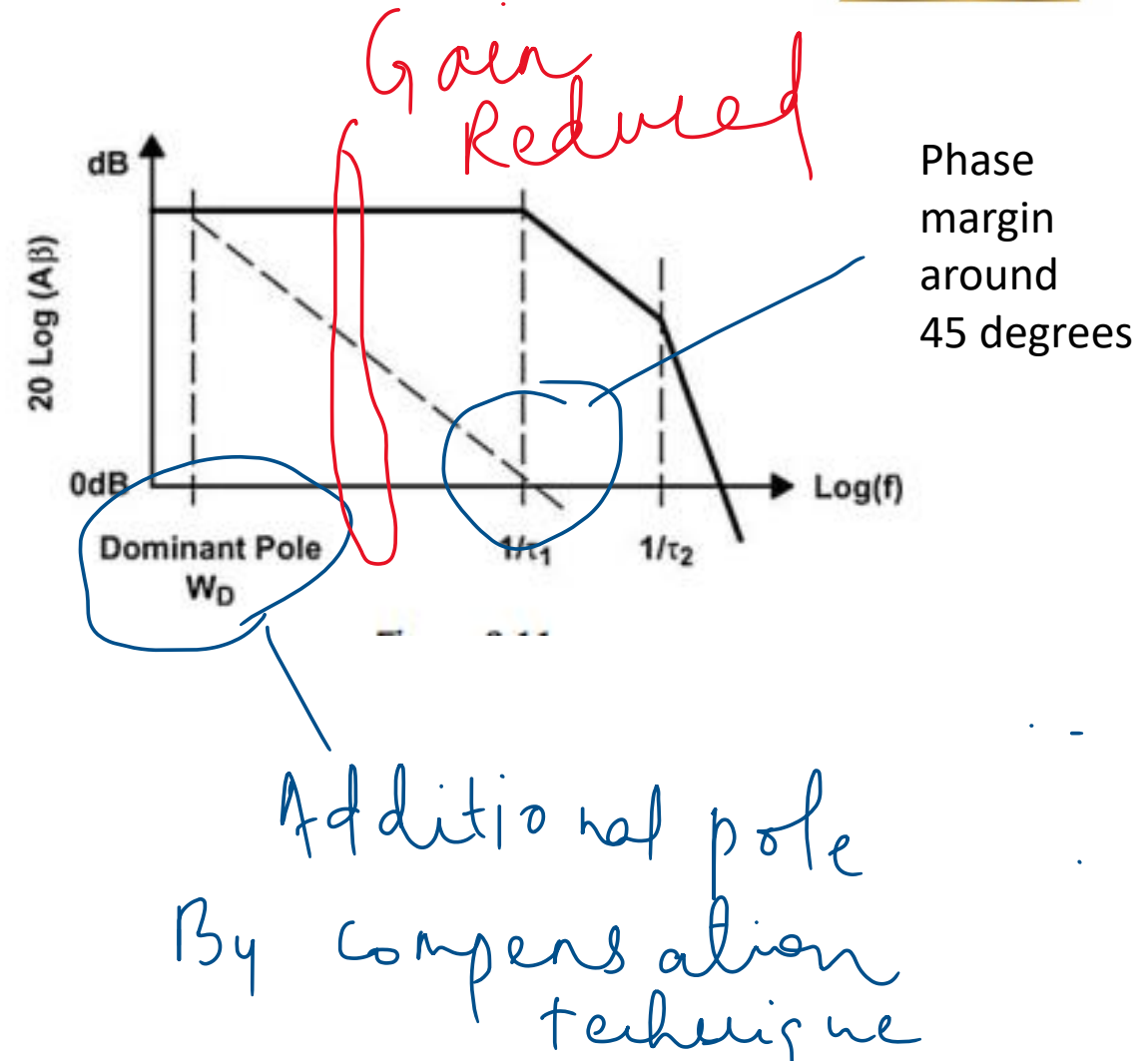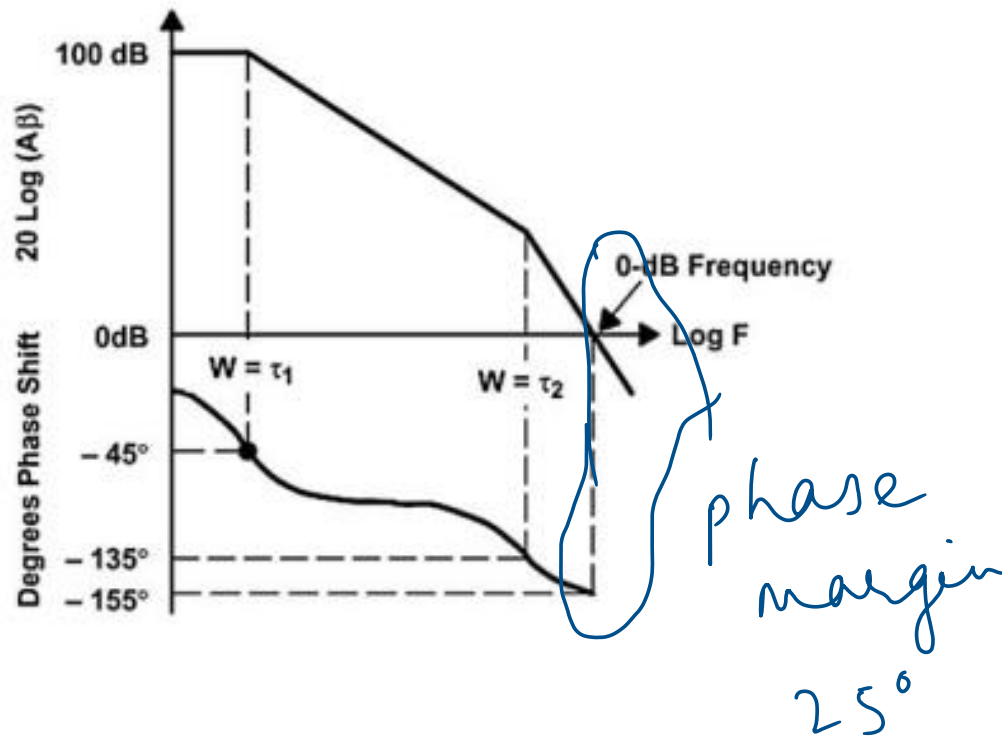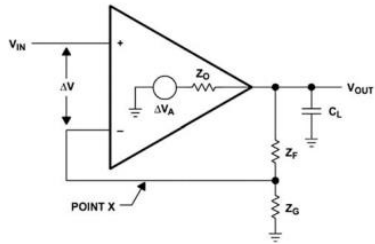

## Unit 2 Dominant pole compensation

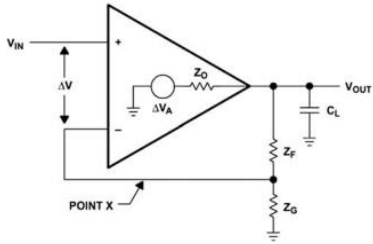

Loop gain  $A\beta = \frac{aZ_G}{Z_F + Z_G} \left( \frac{1}{Z_O C_L s + 1} \right)$

When  $Z_O \ll Z_F$

$$A\beta = \frac{aZ_G}{Z_G + Z_F}$$

Closed loop transfer function is given by

$$\frac{V_{OUT}}{V_{IN}} = \frac{a}{1 + \frac{aZ_G}{Z_G + Z_F}}$$

When  $a = \infty$

$$\frac{V_{OUT}}{V_{IN}} = \frac{Z_F + Z_G}{Z_G}$$

Which represents gain of non inverting amp

## Unit 2 Gain compensation


- Loop gain parameter and closed loop parameters are related

$$A\beta = \frac{aZ_G}{Z_G + Z_F}$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{a}{1 + \frac{aZ_G}{Z_G + Z_F}}$$

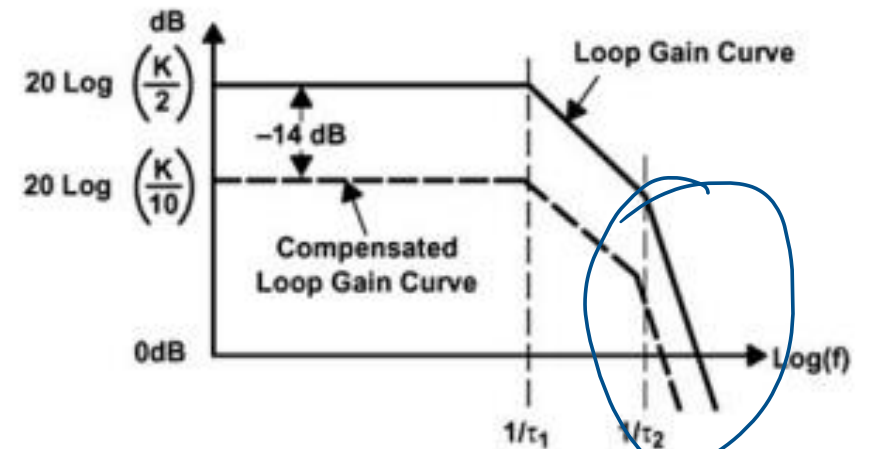- Example, Change non inverting amp gain from 2 to 10
- Loop gain will reduce by -14db

$$20 \text{ Log } \left( \frac{KZ_G}{Z_F + Z_G} \right)$$




*improved phase  
margin*


Improvement observation from the Bode plot

## Unit 2 Lead compensation


- C is because of parasitic capacitance

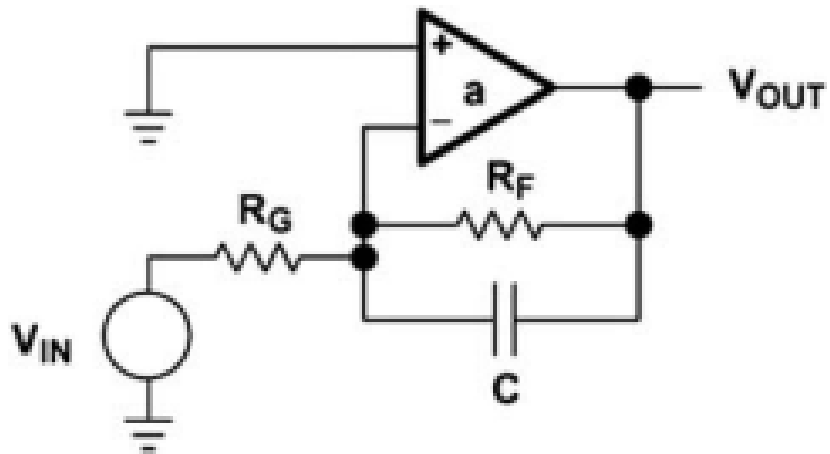

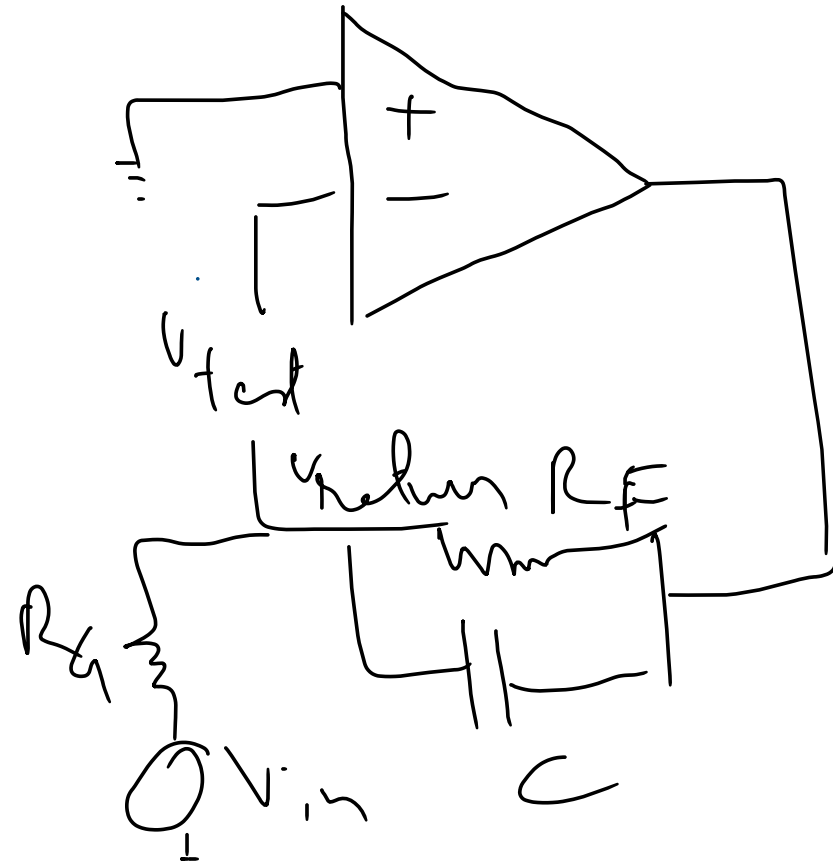- Break the loop for loop gain calculation



## Unit 2 Lead compensation

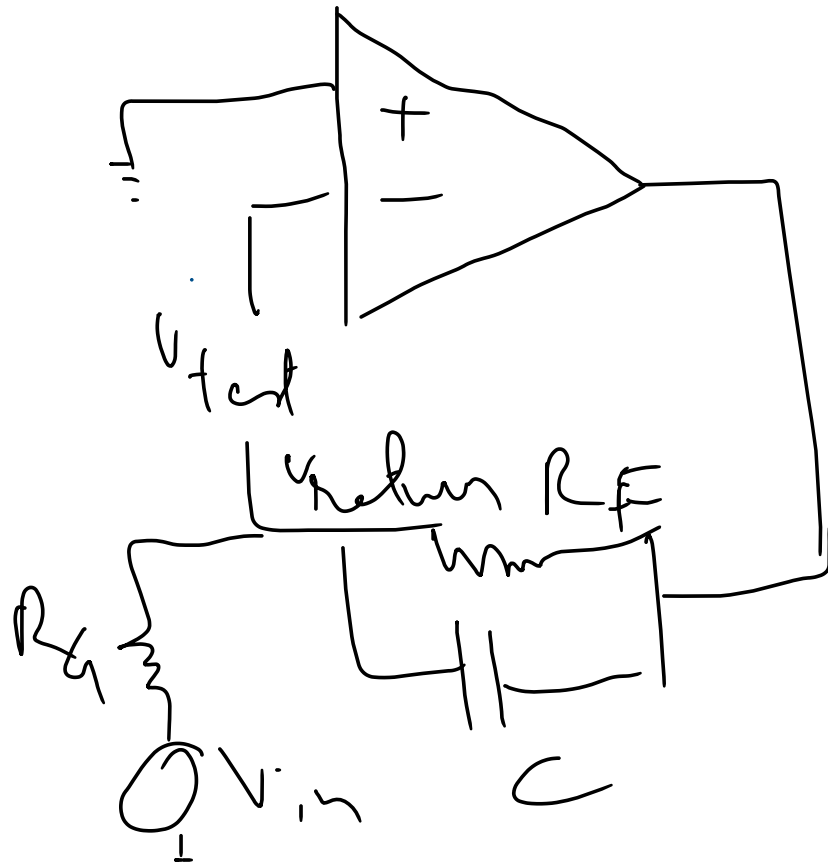

Contribution of open loop op amp



$$A\beta = \left( \frac{R_G}{R_G + R_F} \right) \left( \frac{R_F C s + 1}{R_G \parallel R_F C s + 1} \right) \left( \frac{K}{(s + \tau_1)(s + \tau_2)} \right)$$

$$\frac{V_{\text{return}}}{V_{\text{test}}} = \frac{R_G (s C R_F + 1)}{R_G (s C R_F + 1) + R_F}$$

## Unit 2 Lead compensation

$$A\beta = \left( \frac{R_G}{R_G + R_F} \right) \left( \frac{R_F C s + 1}{R_G \parallel R_F C s + 1} \right) \left( \frac{K}{(s + \tau_1)(s + \tau_2)} \right)$$


Zero introduced

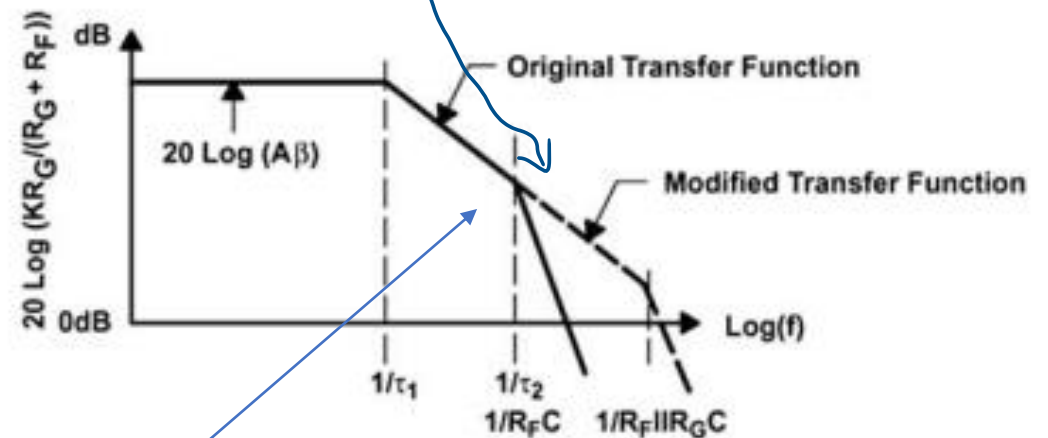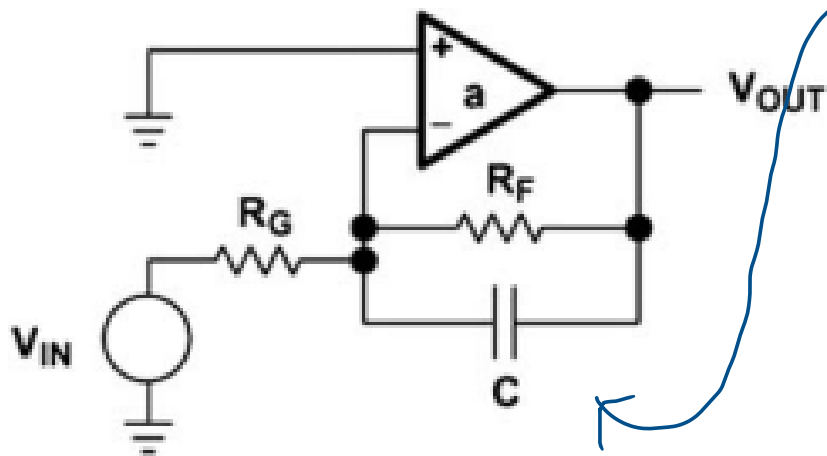

- Zero placed near pole 2
- $R_F$  has to be larger compared to  $R_G$  in parallel with  $R_F$



## Unit 3 Lead compensation

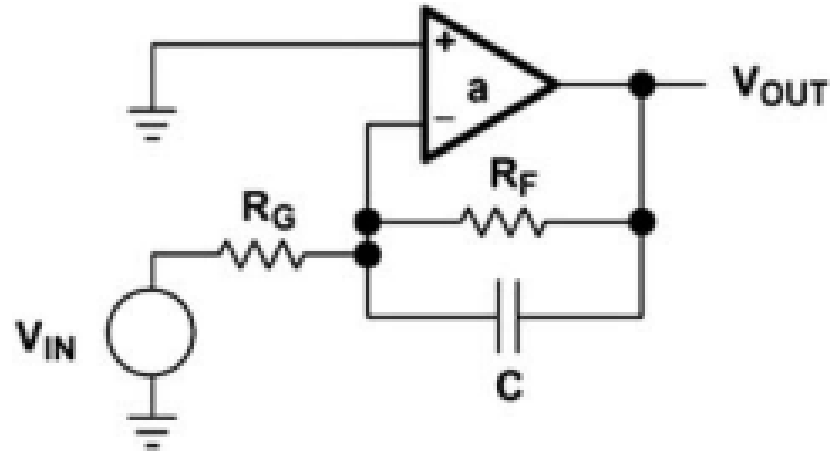

Transfer function of inverting amp is given by

$$\frac{V_{OUT}}{V_{IN}} = \frac{\frac{-aZ_F}{Z_G + Z_F}}{1 + \frac{aZ_G}{Z_G + Z_F}} \quad \text{-----10}$$

$$a = \frac{K}{(s + \tau_1)(s + \tau_2)} \quad \text{----11}$$

When **a** is infinity, transfer function can be seen as,

$$\frac{V_{OUT}}{V_{IN}} = -\frac{Z_F}{Z_{IN}} \quad Z_G$$



Substituting  $R_F \parallel C$  for  $Z_F$  and  $R_G$  for  $Z_G$  :

Transfer function is given by

$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_G} \left( \frac{1}{R_F C s + 1} \right) \quad \text{----12}$$

## Unit 2 Lead compensation


Behavior on bode plot for 10, 11, 12

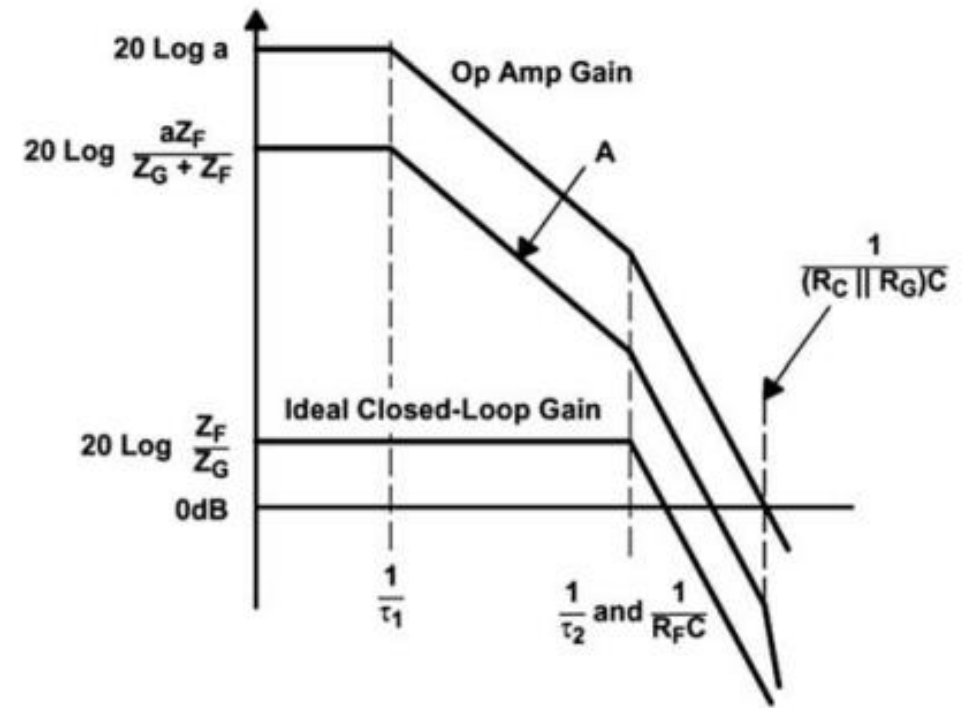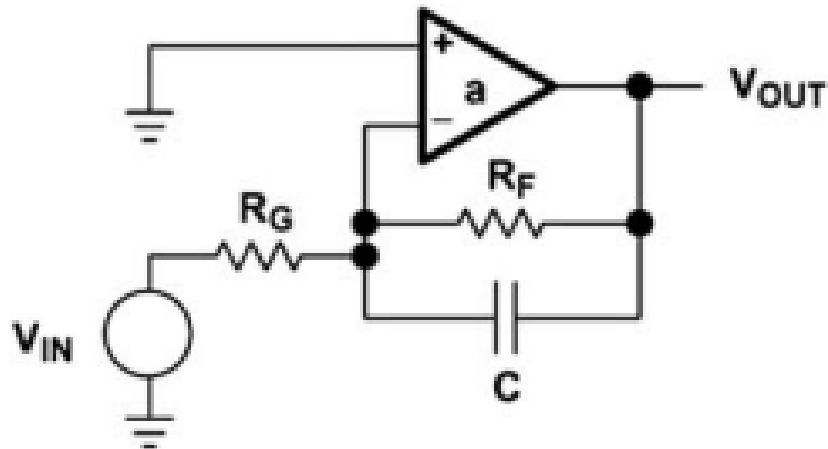

**Figure 8.15**  
Inverting op amp with lead compensation.
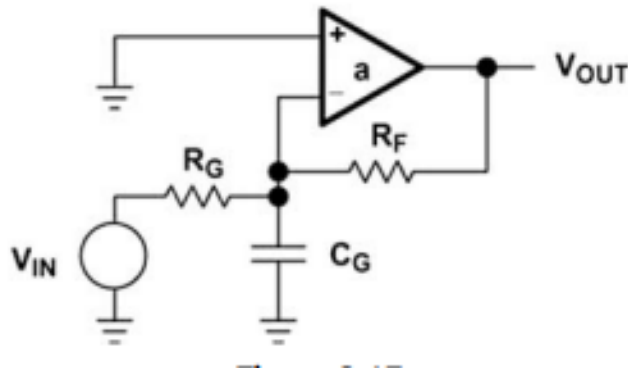
## Unit 2 Compensated attenuation

Stray capacitance is added due to PCB trace  
This circuit is unstable because of three poles




Loop gain

$$A\beta = \left( \frac{R_G}{R_G + R_F} \right) \left( \frac{1}{R_G \parallel R_F C s + 1} \right) \left( \frac{K}{(\tau_1 s + 1)(\tau_2 s + 1)} \right)$$
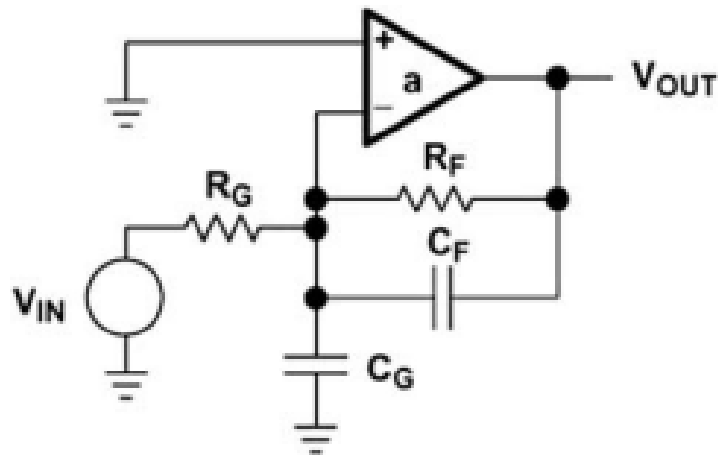
## Unit 2 Compensated attenuation

Compensation capacitor is added parallel to feedback resistor




Loop gain

$$A\beta = \left[ \frac{\frac{R_G}{R_G C_G s + 1}}{\frac{R_G}{R_G C_G s + 1} + \frac{R_F}{R_F C_F s + 1}} \right] \left( \frac{K}{(\tau_1 s + 1)(\tau_2 s + 1)} \right)$$

If  $R_G C_G = R_F C_F$

$$A\beta = \left[ \frac{R_G}{R_G + R_F} \right] \left( \frac{K}{(\tau_1 s + 1)(\tau_2 s + 1)} \right)$$


## Unit 2 Compensated attenuation

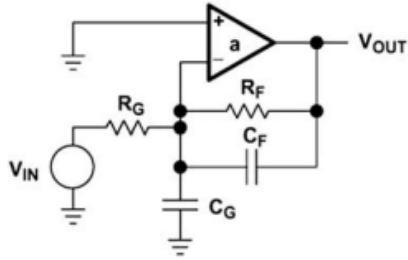

Compensation capacitor is added,  
acts like open loop gain two pole  
system

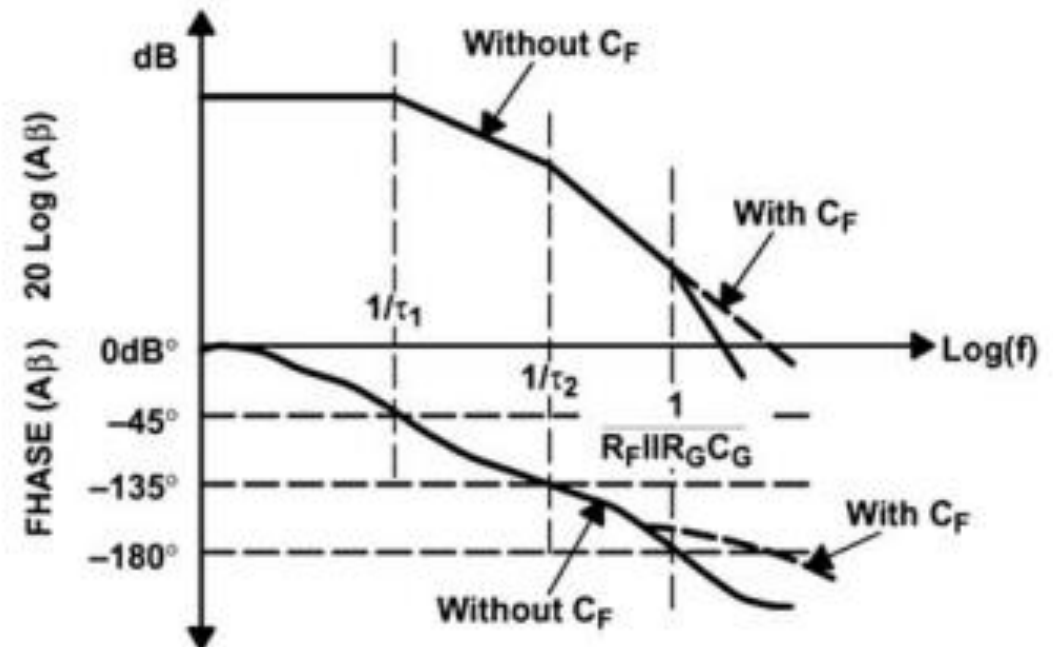
### Gain plot

$$A\beta = \left[ \frac{\frac{R_G}{R_G C_G s + 1}}{\frac{R_G}{R_G C_G s + 1} + \frac{R_F}{R_F C_F s + 1}} \right] \left( \frac{K}{(\tau_1 s + 1)(\tau_2 s + 1)} \right)$$


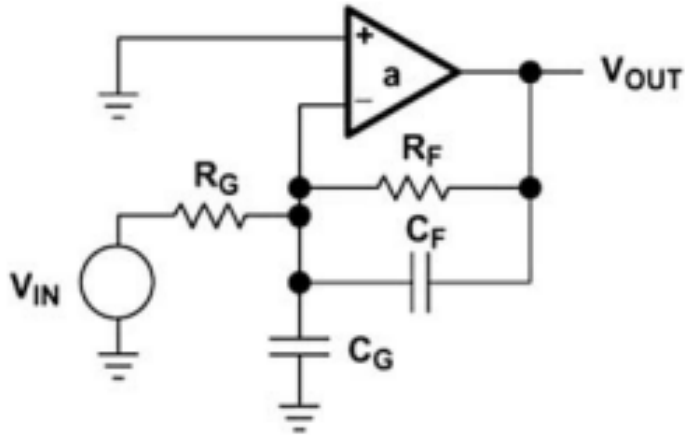
## Unit 2 Compensated attenuation

Closed loop gain of inverted amp does not change. Capacitor has not effect on gain




Closed loop gain

$$\frac{V_{OUT}}{V_{IN}} = \frac{\frac{R_F}{R_F C_F s + 1}}{\frac{R_G}{R_G C_G s + 1}}$$

$$\text{When } R_F C_F = R_G C_G \quad \frac{V_{OUT}}{V_{IN}} = - \left( \frac{R_F}{R_G} \right)$$
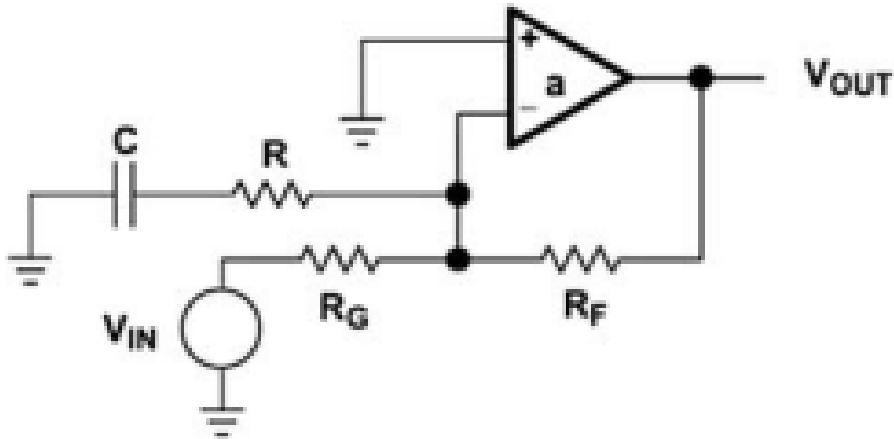
## Unit 2 Lead lag compensation

- R and C used for compensation
- Compensation circuit adds Pole and Zero




loop gain

$$A\beta = \frac{K}{(\tau_1 s + 1)(\tau_2 s + 1)} \frac{R_G}{R_G + R_F} \frac{RCs + 1}{\frac{(RR_G + RR_F + R_G R_F)}{(R_G + R_F)} Cs + 1}$$


## Unit 2 Lead lag compensation

### Gain plot

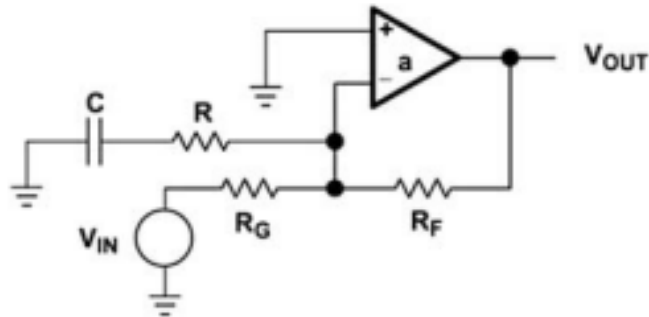

$$A\beta = \frac{K}{(\tau_1 s + 1)(\tau_2 s + 1)} \frac{R_G}{R_G + R_F} \frac{RCs + 1}{\frac{(RR_G + RR_F + R_F R_G)}{(R_G + R_F)} Cs + 1}$$


Zero

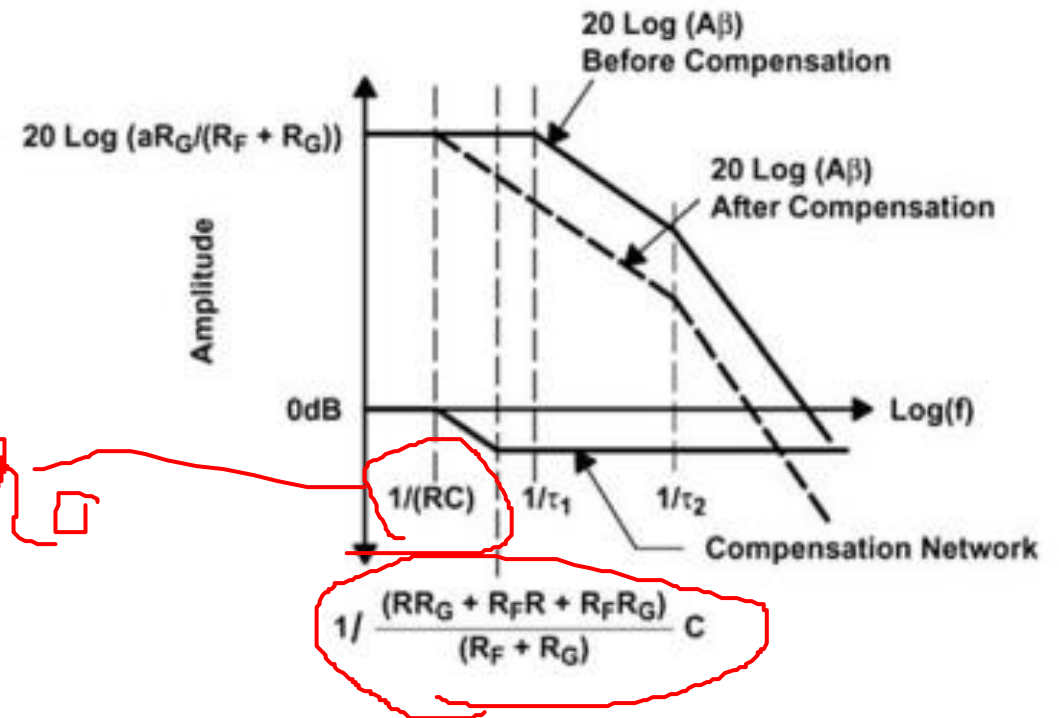



Pole



## Unit 2 Lead lag compensation

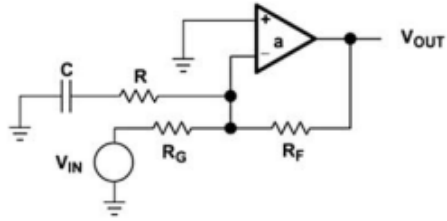


Ideal closed loop gain calculated

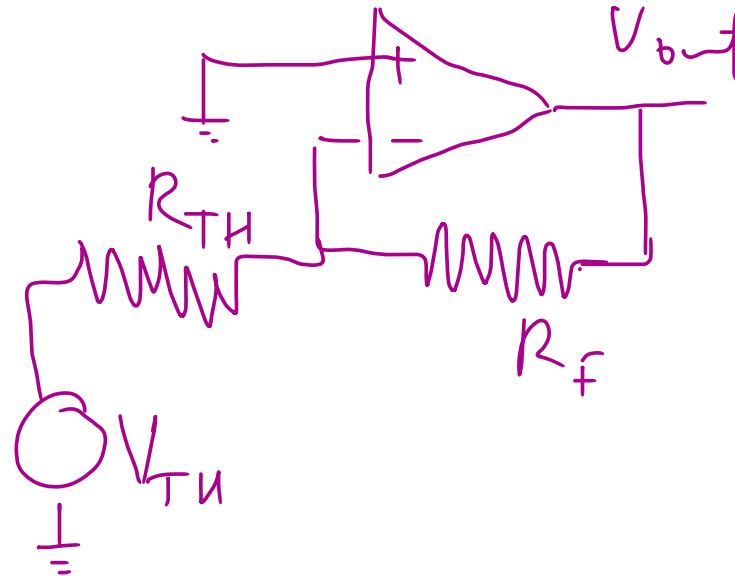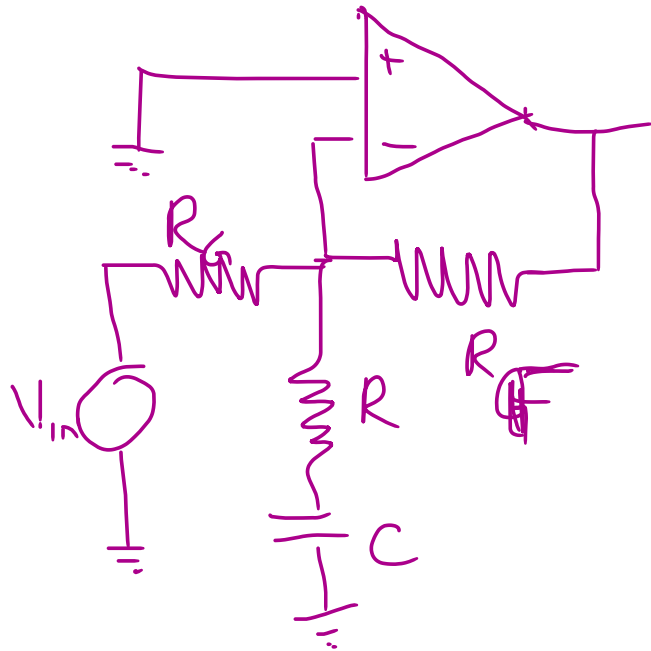

$$V_{TH} = V_{IN} \frac{R + \frac{1}{C_s}}{R + R_G + \frac{1}{C_s}}$$

$$R_{TH} \frac{R_G \left( R + \frac{1}{C_s} \right)}{R + R_G + \frac{1}{C_s}}$$

## Unit 2 Lead lag compensation

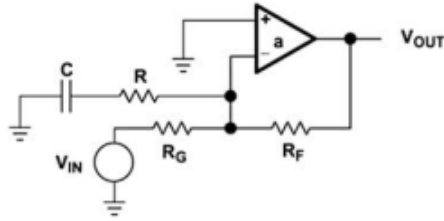


Ideal closed loop gain calculated

$$V_{OUT} = -V_{TH} \frac{R_F}{R_{TH}}$$

$$V_{TH} = V_{IN} \frac{R + \frac{1}{Cs}}{R + R_G + \frac{1}{Cs}}$$

Substitute  $V_{th}$  and  $R_{th}$

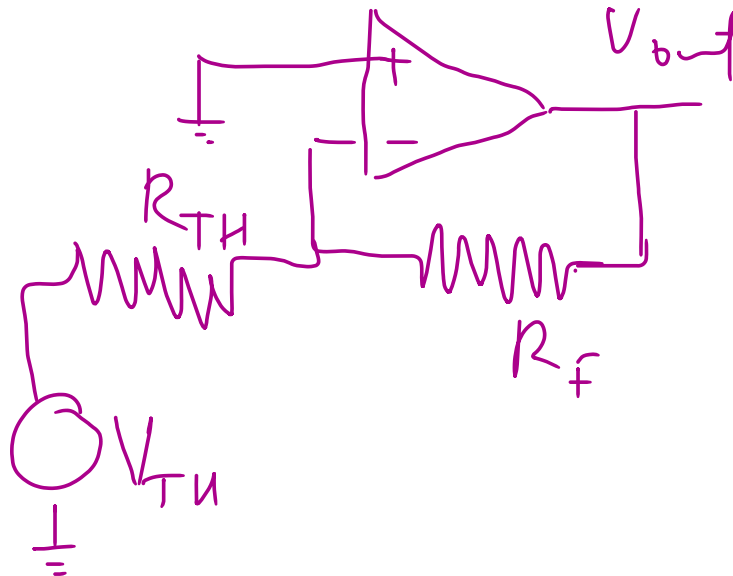


$$R_{TH} \frac{R_G \left( R + \frac{1}{Cs} \right)}{R + R_G + \frac{1}{Cs}}$$

$$-\frac{V_{OUT}}{V_{IN}} = \frac{R + \frac{1}{Cs}}{R + R_G + \frac{1}{Cs}} \frac{R_F}{R_G \left( R + \frac{1}{Cs} \right)} = \frac{R_F}{R_G}$$


gain remains same

## Unit 2 Lead lag compensation

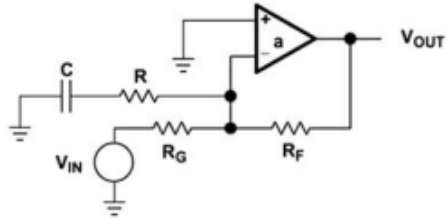

$$A\beta = \frac{K}{(\tau_1 s + 1)(\tau_2 s + 1)} \frac{R_G}{R_G + R_F} \frac{RCs + 1}{\frac{(RR_G + RR_F + R_G R_F)}{(R_G + R_F)} Cs + 1}$$
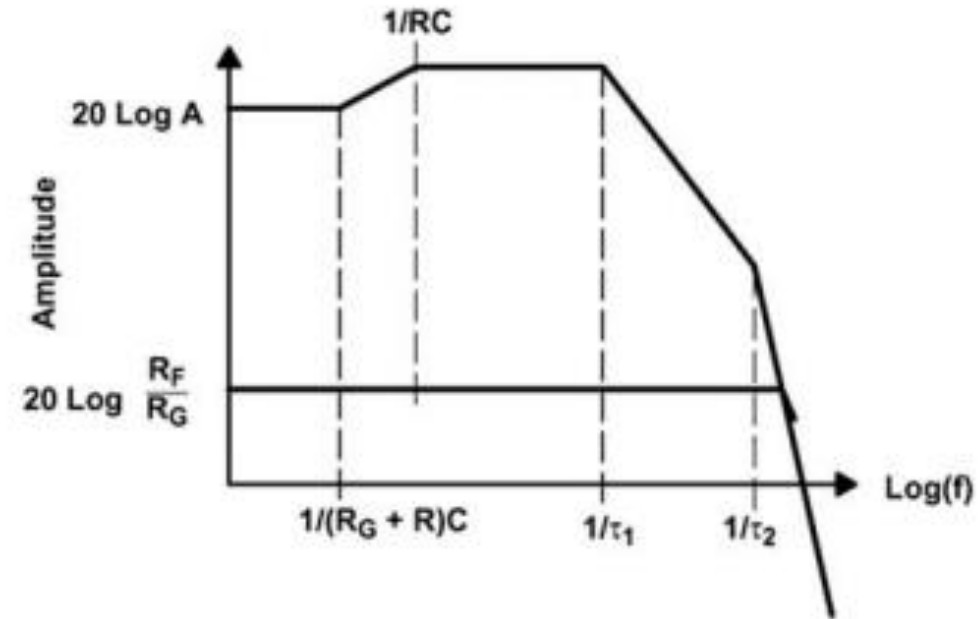
$$-\frac{V_{OUT}}{V_{IN}} = \frac{R_F}{R_G}$$



## Unit 3 Comparison of compensation schemes

Scheme	Advantages	Disadvantages
Internal compensation	No need for extra component	Under certain load capacitance, it is unstable
Dominant pole compensation	Suitable for high load capacitance	Load capacitance make op amp to ring
Gain compensation	Good in terms of stability	Gain reduces
Lead compensation	Increases bandwidth	Reduces closed loop gain
Compensated attenuator	Useful scheme when stray capacitance seen at inverting input	Needs matching two RC time constants
Lead lag compensation	Increased bandwidth	More external components

### **Textbook :**

Op Amp for Everyone : Bruce Carter and Ron Mancini Fifth  
Edition 2017



# THANK YOU

---

**Dr Shashidhar Tantry**

Electronics & Communication  
Engineering

**stantry@pes.edu**