

## MULTIPLE CHOICE QUESTIONS FOR LIC UNIT 1 & 2


1. Among these which is not characteristics of an ideal op amp

- Infinity Gain
- Infinity input resistance
- Zero output resistance
- Zero output current

2. Gain of voltage follower circuit is


- Unity
- Infinity
- Two
- Ten

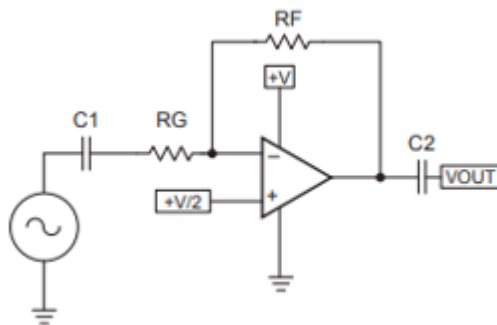3. Which statement is true for the below circuit?



- It is non inverting for DC and inverting for AC
  - It is non inverting for AC and inverting for DC
  - It is inverting for DC and inverting for AC
  - It is non inverting for DC and inverting for AC
4. Find out output voltage of an op amp, if  $V_1$  and  $V_2$  are two input voltages
- $V_{out} = A(V_1 - V_2)$
  - $V_{out} = A/(V_1 - V_2)$
  - $V_{out} = A(V_1 + V_2)$
  - $V_{out} = V_1 - V_2$

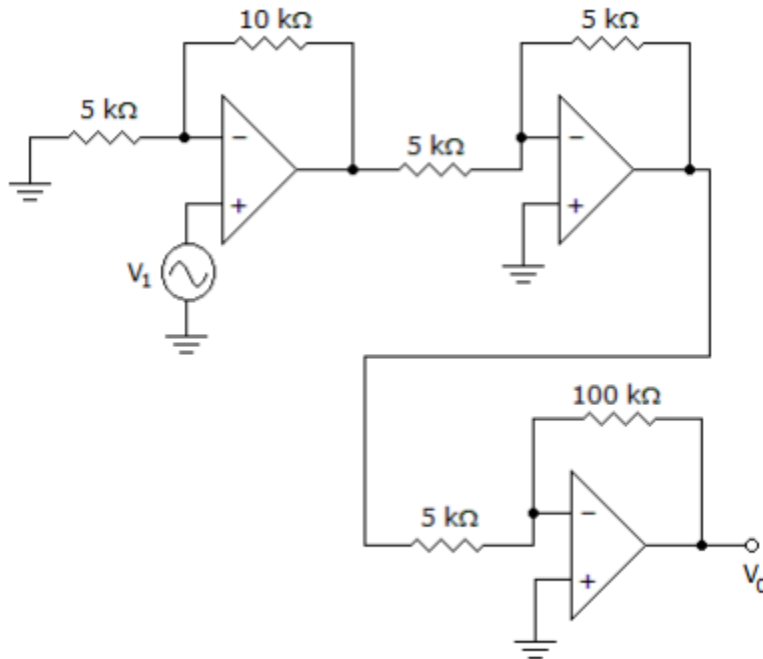5. Calculate the input voltage if the final output is 10.08 V.



- $-1.05\text{ V}$
- $0.525\text{ V}$
- $0.168\text{ V}$
- $4.2\text{ V}$

6. In which compensation technique, we do not use any additional resistor or capacitor?

- Lead compensation
- Gain compensation
- Lead lag compensation
- None of the above

7. Which statement is true with respect to phase margin calculations from Bode plot?

- We measure phase margin at 0db gain
- We measure phase margin at 0db gain and subtract it from 180 degrees

- We measure gain at 0db gain point
  - We measure phase margin at DC operating point
8. Which among them is not a AC parameter for an operation amplifier?
- CMRR
  - PSRR
  - Differential gain
  - Voltage offset
9. Which among these require input voltage at both inverting and non inverting terminals of an operation amplifier?
- Inverting attenuation with zero offset
  - Inverting attenuation with positive offset
  - Inverting attenuation with negative offset
  - Non inverting attenuation with negative offset
10. For the transfer function below, what is open loop gain?

$$\frac{V_{OUT}}{V_{IN}} = \frac{\frac{-aZ_F}{Z_G + Z_F}}{1 + \frac{aZ_G}{Z_G + Z_F}}$$

- a
- $-aZ_F/Z_G + Z_F$
- $1 + a$
- $1 + aZ_G/Z_G + Z_F$