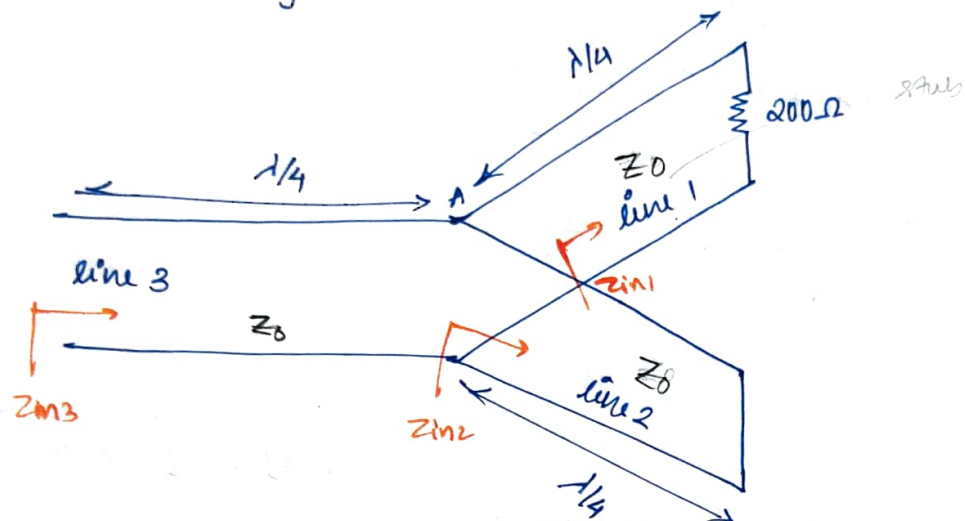


Q) Consider 3 lossless lines as shown in the figure.

If  $Z_0 = 50 \Omega$ , Calculate i)  $Z_{in}$  looking into line 1

ii)  $Z_{in}$  looking into line 2

iii)  $Z_{in}$  looking into line 3.



Sol.

i)  $Z_{in1} = \frac{Z_0^2}{200} = 12.5 \Omega$

ii)  $Z_{in2} = \frac{Z_0^2}{0} = \infty$

iii)  $Z_{in3} = \frac{Z_0^2}{Z}$


$Z = \frac{200}{(50)^2} + 0 \Omega$

$Z_{in1} \parallel Z_{in2} = \frac{12.5 \cdot \infty}{12.5 + \infty} = \frac{\infty (12.5)}{\infty (\frac{12.5}{\infty} + 1)}$

$= 12.5$

$Z_{in3} = \frac{(Z_0)^2}{12.5} = 200 \Omega$

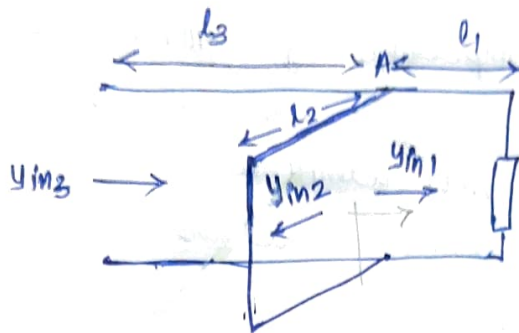2) A section of lossless transmission line is shunted across main line as shown in the figure. If  $l_1 = \frac{\lambda}{4}$ ,  $l_2 = \frac{\lambda}{8}$ ,  $l_3 = \frac{7\lambda}{8}$ . Find  $Y_{in1}$ ,  $Y_{in2}$  and  $Y_{in3}$  (admittances) if  $Z_0 = 100 \Omega$  and  $Z_L = 200 + j150 \Omega$



Sol.  $Z_{in1} = \frac{100^2}{250 \angle 36.86^\circ} = 40 \angle -36.86^\circ$

$l_1 = \frac{\lambda}{4}$

$Y_{in1} = \frac{250 \angle 36.86^\circ}{100^2} \neq \frac{200 + j150}{100^2}$

Refer Quarter wave transformer,

$= (20 + j15) mS$

$l_2 = \frac{\lambda}{8}$

for  $l_2$ , short  
ckt,  $Z_L = 0$

$Z_{in2} = jZ_0$

$\therefore Y_{in2} = \frac{1}{jZ_0}$

$l_3 = \frac{7\lambda}{8}$

$\therefore \beta l = \frac{7\pi}{4}$

$\tan \beta l = -1$

Check formula behind!

$Z_{in3} = Z_0 \left( \frac{Z_L - jZ_0}{Z_0 - jZ_L} \right)$

$= Z_0 \left( \frac{\frac{1}{Y_1 + Y_2} - jZ_0}{Z_0 - j \frac{1}{Y_1 + Y_2}} \right)$

$g = 6.4 + j5.2 mS$

(02)

$$Z = Z_{in1} \parallel Z_{in2}$$

3) An antenna with an impedance of  $40 + j30 \Omega$  is to be matched to a  $100 \Omega$  lossless line with shorted stub.

Determine i) Required stub admittance

ii) Distance between stub and antenna

iii) Stub length

iv) SWR on each segment.

SMITH  
CHART.

Sol. Calculate normalised load impedance, plot it on Smith chart.

$$Z_L = \frac{Z_L}{Z_0} = \frac{40 + j30}{100} = 0.4 + j0.3$$

→ Diagonal opp. to  $Z_L$  on  $S$ -circle, gives  $Y_L$  in chart.

$$Y_L = 1.6 - j1.2$$

→ Where  $S$ -circle intersects  $r=1$  circle

At 2 points A & B

What are values:

$$\text{At A: } 1 + j1.05 \rightarrow Y_1$$

$$\text{B: } 1 - j1.05 \rightarrow Y_2$$

i) Stub admittance required,

$$Y_S = \pm j1.05 \quad \text{normalised but}$$

So

$$Y_S = Y_S \times Y_0 / \frac{Y_S}{Z_0}$$

$$\text{for } Y_1: -j1.05$$

$$Y_2: +j1.05$$


ii) From  $y_L$ , dist. from  $y_L$  to stub at A & B

by 2 distances.

$$y_L \text{ to B: } 0.031$$

$$\frac{(x_2 - x_1)}{2}$$

$$0.337 - 0.3041$$

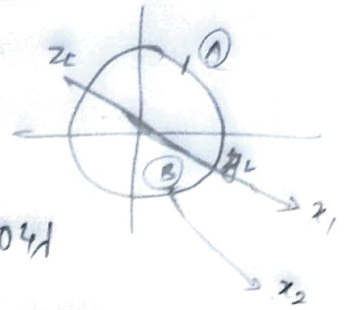

$$y_L \text{ to A: } @ A: 0.5 + 0.164 = 0.664$$

$$0.6641 - 0.3041(2)$$