

Voltage reflection coefficient.

— "ratio of reflected voltage to incident voltage"

Wave propagating in the z dirⁿ : $V_0^+ e^{-\gamma z}$ (INCIDENT WAVE)

In opp dirⁿ : $V_0^- e^{+\gamma z}$ (REFLECTED WAVE)

1) AT LOAD,
that's y
 z_L

$$\gamma_L = \frac{V_0^- e^{+\gamma z_L}}{V_0^+ e^{-\gamma z_L}} = \frac{V_0^-}{V_0^+} e^{2\gamma z_L}$$

using ③ & ④ for V_0^+ & V_0^-

$$\gamma_L = \frac{\cancel{V_0} (V_L - I_L Z_0)}{\cancel{V_0} (V_L + I_L Z_0)} \quad \div \text{ by } I_L$$

$$\boxed{\gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}}$$

① → When load is perfectly matched i.e. $Z_L = Z_0$
load is matched to characteristic impedance.
 $\boxed{\gamma_L = 0}$

In general, γ_L is a complex quantity (b/c of Z_0).

② → When load is short ckted, $\gamma_L = -1$ ($Z_L = 0$)

③ → When load is open ckted, $Z_L = \infty$, $\gamma_L = 1$

$$\boxed{0 \leq |\gamma_L| \leq 1}$$

for perfect mismatch

short ckt or open ckt!

that's y γz

2) AT ANY z ,

$$T(z) = \frac{V_0^- e^{\gamma z}}{V_0^+ e^{-\gamma z}}$$

$$= \frac{V_0^-}{V_0^+} \cdot e^{2\gamma z} = \gamma_L e^{-2\gamma l} e^{2\gamma z}$$

instead of using ③ & ④

Replace $z = l - l'$ from load also.

$$T(z) = \gamma_L e^{-2\gamma l'}$$

Q1) A 50Ω transmission line of length l is open circuited. If the input impedance is $-j62\Omega$, determine l in terms of λ .

Sol. $Z_{in} = 50\Omega - j62\Omega$; $Z_L = \infty$

$$Z_{in} = \frac{Z_0 [Z_L + Z_0 \tanh(\gamma l)]}{Z_0 + Z_L \tanh(\gamma l)}$$

$$\gamma = j\alpha = 0$$

$$\beta = \frac{2\pi}{\lambda}$$

Take out Z_L ;

$$= \frac{Z_0 \left(1 + \frac{Z_0}{Z_L} \tanh(\gamma l) \right)}{\frac{Z_0}{Z_L} + \tanh(\gamma l)}$$

$$\frac{Z_0}{Z_L} + \tanh(\gamma l)$$

$$Z_{in} = \frac{Z_0}{j + \tanh(\gamma l)}$$

$$Z_{in} = -j Z_0 \coth(\gamma l)$$

$$-j62 = -j50 \coth(\gamma l)$$

$$Z_{in} = -j Z_0 \cot(\beta l) \because \gamma = 0$$

$$-j62 = -j50 \cot(\beta l)$$

$$\tan \beta l = \frac{50}{62}$$

$$\tan^{-1} \left(\frac{50}{62} \right) = \beta l$$

$$\tan^{-1} \left(\frac{50}{62} \right) = 0.6786$$

$$= \beta l$$

$$0.6786 = \frac{2\pi}{\lambda} \cdot l$$

$$l = \frac{0.6786 \lambda}{2\pi}$$


Current reflection coefficient

- "ratio of reflected current to incident current". 9.11.23

- negative of voltage reflection coefficient


AT LOAD,
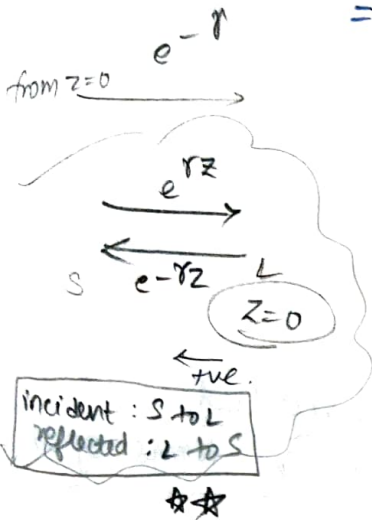
$$= \frac{I_0^- e^{+\gamma l}}{I_0^+ e^{-\gamma l}} = \frac{\frac{-V_0^-}{Z_0} e^{+\gamma l}}{\frac{V_0^+}{Z_0} e^{-\gamma l}} \quad \text{VOLT. R. COEFF.}$$



$$= -\Gamma_L$$

l' is the distance from the load.

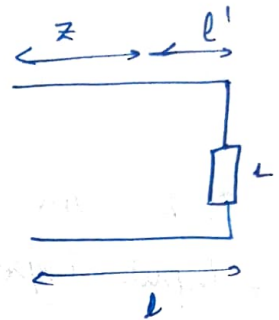

$$V(l') = V_L^+ e^{+\gamma l'} + V_L^- e^{-\gamma l'}$$

$$I(l') = I_L^+ e^{+\gamma l'} + I_L^- e^{-\gamma l'}$$

$$\Gamma(l') = \left(\frac{V_L^-}{V_L^+} \right) \frac{e^{-\gamma l'}}{e^{+\gamma l'}}$$

V_L^+ & V_L^- are the incident voltages at the load.

$$\Gamma(l') = \Gamma_L e^{-2\gamma l'}$$

⇒ Reflection coefficient at any z (from load end), (prev page)

$$\Gamma(z) = \Gamma_L e^{-2\gamma z}$$

$$= \Gamma_L e^{-2(\alpha + j\beta)z}$$

$$= \Gamma_L e^{-2\alpha z} e^{-j2\beta z}$$


WK, $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$; can be complex; so mag. & dirⁿ.

$$\Gamma(z) = |\Gamma_L| e^{j\theta_{\Gamma_L}} \cdot e^{-2\alpha z} \cdot e^{-j2\beta z}$$

contributes to magnitude

$$\Gamma(z) = |\Gamma_L| e^{-2\alpha z} \cdot e^{j(\theta_{\Gamma_L} - 2\beta z)}$$

V_L is a phasor, mag n dir

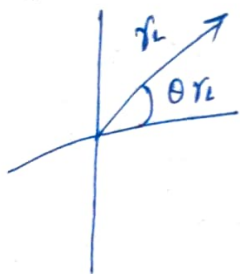

1) For general ~~lossless~~ line, (~~lossless~~)

As $z \rightarrow \infty$,

magnitudes \downarrow


phase \downarrow clockwise, spiralling (rotates)



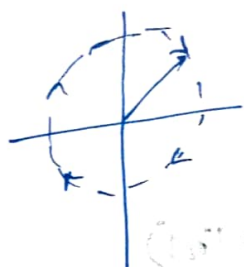2) For lossless line, ($\alpha = 0$)

As $z \rightarrow \infty$,

magnitude \downarrow of phasor remains same, (for all values of z)
angle rotates clockwise



$$\rightarrow V(z) = |V_L| e^{j(\theta_L - 2\beta z)}$$

For this phasor to complete one revolution, what will be the distance travelled? $2\beta z$ is the term deciding where it'll be there?

$$2\beta z_0 = 2\pi$$

$$\beta = \frac{2\pi}{\lambda}$$

$$2 \cdot \frac{2\pi}{\lambda} \cdot z_0 = 2\pi$$

$$z_0 = \frac{\lambda}{2}$$

1 complete revolution is equal to a distance $\frac{\lambda}{2}$.

(Important for Smith chart!)

\rightarrow standing wave: by ^{got} sketching sum of voltages of Inc & Ref. waves
It is "standing wave pattern" is obtained by plotting amplitude of resultant of voltages corresponding to incident and reflected waves. On a lossless line".

$\alpha = 0$

$$\cos \frac{V_0^-}{V_0^+} = \Gamma_L$$

$$V(z) = V_0 \sin(\omega t + \beta z) + V_0 \Gamma_L \sin(\omega t - \beta z)$$

$$= \underbrace{V_0 \sin(\omega t + \beta z)}_{\text{Incident}} + \underbrace{V_0 |\Gamma_L| \sin(\omega t - \beta z + \theta_L)}_{\text{Reflected}}$$

Incident

Reflected

→ for waveform:



bcos reflected has extra θ_r

arrows: direction

of rotation of

Incident & Reflected

Anticlockwise

$\sin(z)$

angle θ_{inc}

Clockwise

$\sin(-\beta z)$

angle θ_{ref}


Sketching sum of resultant (standing wave defn):

$$\rightarrow V(z) = V_0 \sin(\omega t + \beta z) + V_0 |\Gamma_L| \sin(\omega t - \beta z + \theta_r)$$

$$V_{max} = V_0 [1 + |\Gamma_L|]$$

$$V_{min} = V_0 [1 - |\Gamma_L|]$$

Corresponding to voltage.

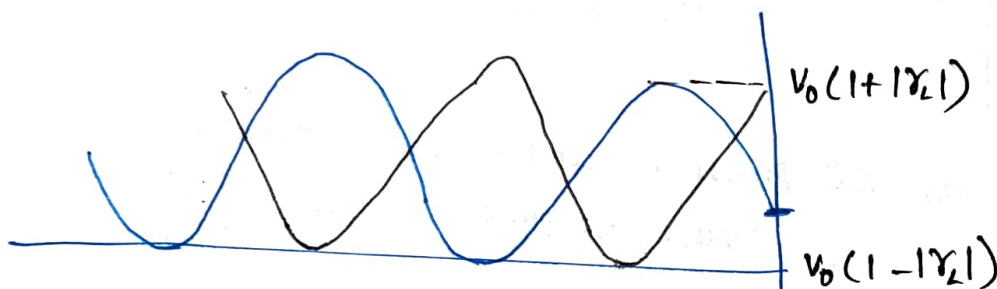

(■ - for current: bcos expⁿ for $I(z)$ there is -ve)
 $[I(z) = I_0^+ \sin(\omega t + \beta z) + I_0^- \sin(\omega t - \beta z + \theta)]$

→ V_{max} : when both in phase

V_{min} : when both out of phase

(Addⁿ of incld + refl.)

VSWR - voltage standing wave Ratio.

denoted as $\frac{S}{P}$ (our TS) (other TS)

- ratio of max^m voltage to min^m voltage.

$$S = \frac{V_{max}}{V_{min}} = \frac{V_0 [1 + |\Gamma_L|]}{V_0 [1 - |\Gamma_L|]}$$

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

; in terms of reflection coefficient

If $|r_L| = 0$, $S = 1$
 $|r_L| = 1$, $S = \infty$


1) Short circuited load $Z_L = 0$

$$\underline{r_L} = \frac{Z_L - Z_0}{Z_L + Z_0} = \underline{-1}$$

$$Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan(\beta L)}{Z_0 + jZ_L \tan(\beta L)} \right]$$

$$Z_{sc} = \boxed{Z_{in} = jZ_0 \tan(\beta L)}$$

→ Z_{sc} vs βL :

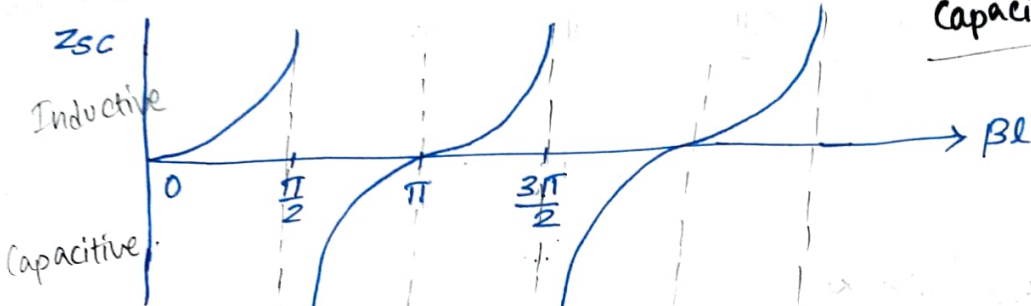

in terms of λ :

$\frac{\lambda}{4}$ $\frac{\lambda}{2}$


} All lossless
 inc. & refl. are out of phase:

If length of transmission line is varying from 0 to $\lambda/4$

$l \rightarrow 0 \text{ to } \frac{\lambda}{4}$; $Z = j0 \text{ to } j\infty$

$l \rightarrow \frac{\lambda}{4} \text{ to } \frac{\lambda}{2}$; $Z = -j\infty \text{ to } j0$

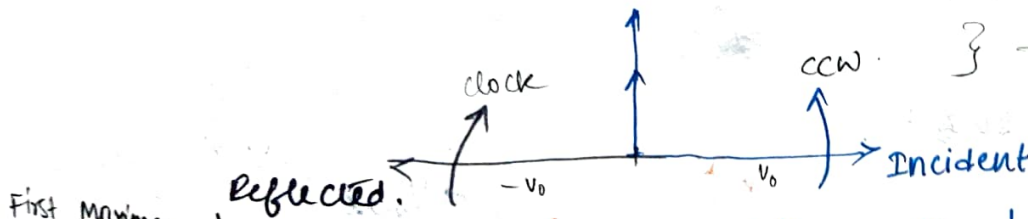Inductive reactance
 Capacitive reactance



First maxima = $\frac{\lambda}{4}$
 First minima = 0

Voltage standing wave

• VSWR; $\boxed{S = \infty}$

loss CR coeff:
 -ve of VRC:
 $r_L = 1$

Total phase
 $= \frac{\pi}{2} + \frac{\pi}{2} = \pi$
 when both travelled $\pi/2$ for maxm.

in terms of wavelength:
 $2\beta Z_0 = \pi$
 $2 \cdot \frac{2\pi}{\lambda} Z_0 = \pi$
 $\boxed{Z_0 = \frac{\lambda}{4}}$


2) Open circuited load: $Z_L = \infty$

$$\gamma_L = 1$$

$$Z_{oc} = Z_{in} = Z_0 \cdot \frac{Z_L \left[1 + j \frac{Z_0}{Z_L} \tan(\beta l) \right]}{\frac{Z_0}{Z_L} + j \tan(\beta l)}$$

$$Z_{oc} = Z_{in} = \frac{Z_0}{j \tan \beta l} = -j Z_0 \cot \beta l$$

Z_{oc} vs βl :

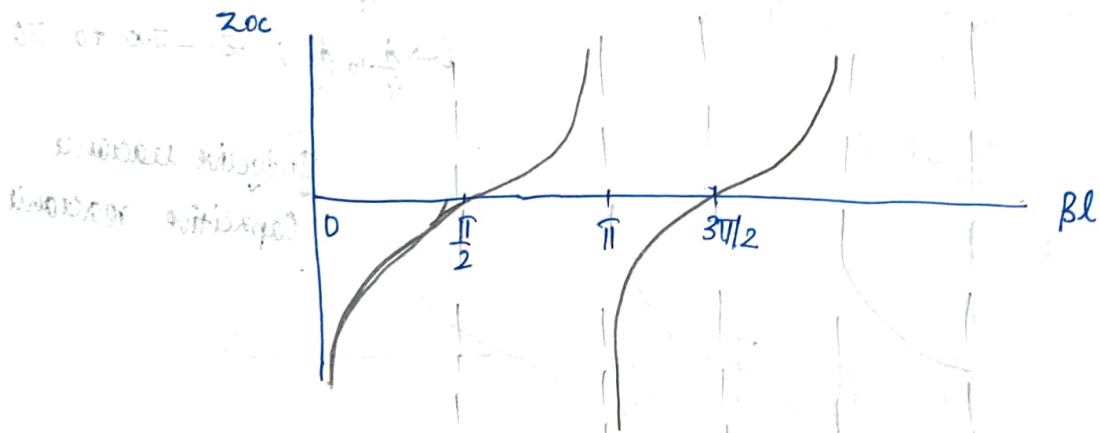


VSWR; $S = \infty$

• $\gamma_L = 1, S = \infty$

means if inc. wave \rightarrow dirⁿ, then refl. wave also same dirⁿ \rightarrow addⁿ. (starts at maxima)

Voltage SWR:

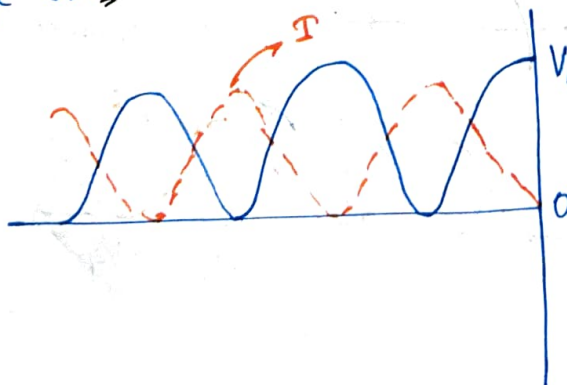

$$\begin{aligned} V_{max} &\Rightarrow V_0 (1 + |\gamma_L|) \\ &= V_0 (1 + 1) \\ &= \underline{\underline{2V_0}} \end{aligned}$$

3) Matched load:

$$\gamma_L = 0$$

$$Z_L = Z_0$$

→ Reflection coefficient;

so that means THERE'S NO REFLECTION.

∴ No standing wave pattern.

$$Z_{in} = Z_0$$

← Substitute in eqn.

Ideally preferred,

cos during reflection;

if there's loss of signal.

• VSWR;

$$S = 1$$

Average Power

$$P_{av} = V_{rms} I_{rms} \cos \theta$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$= \frac{1}{2} (V_m I_m \cos \theta)$$

$$P_{av} = \frac{1}{2} \operatorname{Re} \{ V_S(l) \cdot I_S^*(l) \} + \text{cos from load end.}$$

for a lossless

line;
($\alpha = 0$)

$$= \frac{1}{2} \operatorname{Re} \{ (V_0^+ e^{j\beta l} + \gamma_L V_0^+ e^{-j\beta l}) (I_0^+ e^{j\beta l} + \gamma_L I_0^+ e^{-j\beta l})^* \}$$

$$= \frac{1}{2} \operatorname{Re} \{ (V_0^+ e^{j\beta l} + \gamma_L V_0^+ e^{-j\beta l}) \left(\frac{V_0^+}{Z_0} e^{j\beta l} - \gamma_L \frac{V_0^+}{Z_0} e^{-j\beta l} \right)^* \}$$

For lossless
line,
 $Z_0 = \text{Real}$.

$$= \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \operatorname{Re} \{ (e^{j\beta l} + \gamma_L e^{-j\beta l}) (e^{j\beta l} - \gamma_L e^{-j\beta l})^* \}$$

$$= \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \operatorname{Re} \{ (e^{j\beta l} + \gamma_L e^{-j\beta l}) (e^{-j\beta l} - \gamma_L^* e^{j\beta l}) \}$$

$$= \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \operatorname{Re} \{ e^{j\beta l} (e^{-j\beta l} - \gamma_L^* e^{j\beta l}) + \gamma_L e^{-j\beta l} (e^{-j\beta l} - \gamma_L^* e^{j\beta l}) \}$$

$$= \frac{|V_0^+|^2}{2Z_0} \operatorname{Re} \{ 1 + \underbrace{\gamma_L e^{-j2\beta l}}_{\text{they are complex conjugates to each other.}} - \underbrace{\gamma_L^* e^{j2\beta l}}_{\text{they are complex conjugates to each other.}} - |\gamma_L|^2 \}$$

they are complex conjugates to each other.


$$\operatorname{Re} \{ a + jb - (a - jb) \} = 0$$

$$P_{av} = \frac{|V_0^+|^2}{2Z_0} [1 - |\gamma_L|^2]$$

$$P_t = P_i - P_r$$

→ Power dissipated by load / Avg. power / Total power.

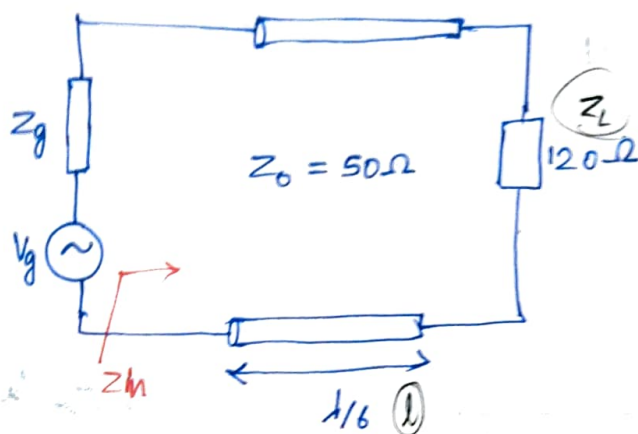Q. 1) A lossless transmission line is as shown in the figure.



Find Γ , VSWR and Z_{in} at the generator end.

Sol. i) $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{120 - 50}{120 + 50} = \frac{70}{170} = 0.411$

ii) VSWR, $S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = 2.39$

iii) Z_{in} , $Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right]$

$\Rightarrow \beta l = ?$


$\beta l = \frac{2\pi}{\lambda} \cdot l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{6} = \frac{\pi}{3}$

$Z_{in} = 50 \left[\frac{120 + j50 \tan(\pi/3)}{50 + j120 \tan(\pi/3)} \right] = 50 \left[\frac{120 + j50 \frac{\sqrt{3}}{1}}{50 + j120 \frac{\sqrt{3}}{1}} \right]$

$= \frac{6000 + j2500\sqrt{3}}{50 + j120\sqrt{3}} = \frac{7299.3 \angle 35.81^\circ}{213.77 \angle 76.47^\circ} = 34.61 \angle -40.66^\circ$


Casei
degree

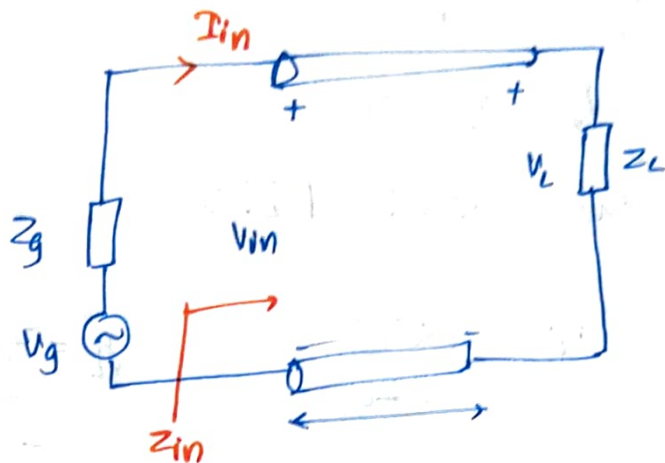- 2) A transmission line shown in the figure is 40m long and has $V_g = 15 \angle 0^\circ$ Vrms, $Z_0 = 30 + j60 \Omega$, $V_L = 5 \angle -48^\circ$ Vrms, $Z_g = 0$.
 If the line is matched to the load and $Z_g = 0$, calculate i) input impedance; Z_{in} ii) sending end current and voltage (I_{in} & V_{in}).



Sol. i) $Z_{in} = Z_0$
 $= 30 + j60 \Omega$

For matched load.

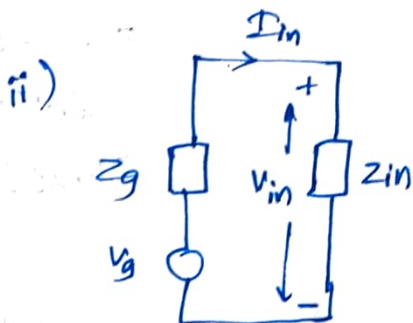

$\rightarrow I_{in}$ general (if Z_g was not zero)

$$V_{in} = V_g \cdot \frac{Z_{in}}{Z_{in} + Z_g}$$

here $Z_g = 0$

$$V_{in} = V_g$$

$$\rightarrow I_{in} = \frac{V_g}{Z_g + Z_{in}}$$

$$I_{in} = \frac{15 \angle 0^\circ}{67.08 \angle 63.43^\circ} = 0.223 \angle -63.43^\circ \text{ A}$$

3) A 50Ω lossless transmission line is terminated by a load impedance $50 - j75\Omega$. If the incident power is 100mW, find the power dissipated by the load.

Sol.

$$P_{av} = \frac{|V_0|^2}{2Z_0} [1 - |\Gamma_L|^2]$$

$$P_t = P_i - P_r$$

$$P_{av} = P_i (1 - |\Gamma_L|^2)$$

Incomp!

$$P_i = \frac{|V_0|^2}{2Z_0}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$= \frac{50 - j75 - 50}{50 - j75 + 50}$$

$$= \frac{-j75}{250 - j75}$$

$$= 75 \angle -90^\circ$$

$$261.007 \angle 16.69^\circ$$

$$= 0.28 \angle -73.31^\circ$$



20.11.23

$$\Rightarrow V(x) = V_0 e^{+\gamma x} + V_0 \Gamma_L e^{-\gamma x}$$

$$= V_0 (e^{\gamma x} + \Gamma_L e^{-\gamma x})$$

$$I(x) = I_0 e^{\gamma x} - I_0 \Gamma_L e^{-\gamma x}$$

3 || by inc + refl but -ve of VRC.

$$= \frac{V_0}{Z_0} (e^{\gamma x} - \Gamma_L e^{-\gamma x})$$

$$\rightarrow Z(x) = \frac{V(x)}{I(x)} = Z_0 \frac{(e^{\gamma x} + \Gamma_L e^{-\gamma x})}{(e^{\gamma x} - \Gamma_L e^{-\gamma x})}$$

Take $e^{\gamma x}$ out;

$$= Z_0 \frac{(1 + \Gamma_L e^{-2\gamma x})}{(1 - \Gamma_L e^{-2\gamma x})} = Z_0 \left(\frac{1 + \Gamma(x)}{1 - \Gamma(x)} \right)$$

capital gamma

$$\Gamma(x) = \Gamma_L e^{-2\gamma x}$$

$$= |\Gamma_L| e^{-2\alpha x} \angle \theta_{\Gamma_L} - 2\beta x$$

contributes to ampl.

Wherever there is voltage maximum, there is current minimum.

$$\rightarrow \underline{Z_{\max}} = \frac{V_{\max}}{I_{\min}}$$

$$= \frac{V_0 (1 + |\Gamma_L|)}{I_0 (1 - |\Gamma_L|)}$$

$$\boxed{Z_{\max} = Z_0 S}$$

Illy

$$\rightarrow \underline{Z_{\min}} = \frac{V_{\min}}{I_{\max}}$$

$$= \frac{V_0 (1 - |\Gamma_L|)}{I_0 (1 + |\Gamma_L|)}$$

$$\boxed{Z_{\min} = \frac{Z_0}{S}}$$

Q1) A 600Ω transmission line is 150 m long. It operates at 400 kHz with $\alpha = 2.4\text{ mnp/m}$ and $\beta = 0.0212\text{ rad/m}$ load impedance of $424.3\angle 45^\circ$. Find

i) length of the line in terms of λ .

* Refl. coeff @ load.

ii) Γ_L

* Refl. coeff from Z_L @ length l (So Src)

iii) $\Gamma(x)$ at $x=l$

iv) Z at $x=l$

Sol. Given, $Z_0 = 600\Omega$
 $l = 150\text{ m}$

$$Z_L = 424.3\angle 45^\circ = 300 + j300$$

$$\alpha = 2.4 \times 10^{-3}$$

$$\beta = 0.0212$$

$$f = 400\text{ kHz}$$

i) wk, $\beta = \frac{2\pi}{\lambda}$

$$0.0212 = \frac{2\pi}{\lambda} \text{ rad. Calc'}$$

$$\lambda = 296.37\text{ m}$$

$$x = 150\text{ m}$$

$$150\lambda = 296.37 \times l$$

$$\boxed{l = 0.506\lambda}$$

ii) $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{300 + j300 - 600}{300 + j300 + 600}$

$$= \frac{-300 + j300}{900 + j300} = \frac{424.26\angle 135^\circ}{948.68\angle 18.43^\circ}$$

$$\boxed{\Gamma_L = 0.447\angle 116.57^\circ}$$

θ_{Γ_L}

$$\text{iii)} \quad r(x) = |r_L| e^{-2\gamma x} \\ = |r_L| e^{-2\alpha x} \angle 0^\circ - 2\beta x$$

CALC:
Wimmerer B, rad.

$$\boxed{r(x) = 0.2175 \angle -247.}$$

$$\text{iv)} \quad z(x) = \frac{z_0 (e^{\gamma x} + r_L e^{-\gamma x})}{(e^{\gamma x} - r_L e^{-\gamma x})}$$

$$= z_0 \left(\frac{1 + r(x)}{1 - r(x)} \right)$$

$$= 600 \left(\frac{1 + 0.2175 \angle -247}{1 - 0.2175 \angle -247} \right)$$

$$= 600 \left(\frac{1 + (-0.081 + j0.2)}{1 - (-0.081 + j0.2)} \right)$$

$$= 600 \left(\frac{1 - 0.081 + j0.2}{1 + 0.081 - j0.2} \right) = 600 \left(\frac{0.919 + j0.2}{1.081 - j0.2} \right)$$

$$= 513.19 \angle 22.75.$$

SMITH CHART

→ Normalised impedance chart
Normalised admittance chart

Since many values of Z_L and Z_0 map to same Γ ,

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{\text{complex}}{\text{real}} = \Gamma_r + j\Gamma_i$$

Normalised impedance,

$$\bar{Z}_L = \frac{Z_L}{Z_0} = r + jx$$

From ①,

$$\Gamma = \frac{\bar{Z}_L - 1}{\bar{Z}_L + 1}$$

$$\Gamma(\bar{Z}_L + 1) = \bar{Z}_L - 1$$

$$\Gamma\bar{Z}_L + \Gamma - \bar{Z}_L + 1 = 0$$

$$\bar{Z}_L(1 - \Gamma) = 1 + \Gamma$$

$$\bar{Z}_L = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + \Gamma_r + j\Gamma_i}{1 - \Gamma_r - j\Gamma_i} \times \frac{(1 - \Gamma_r + j\Gamma_i)}{(1 - \Gamma_r + j\Gamma_i)}$$

$$(a - jb)(a + jb) = a^2 + b^2$$

Easy calcⁿ:

$$\frac{1 + j\Gamma_i - \Gamma_r}{1 + j\Gamma_i + \Gamma_r}$$

$$(a+b)(a-b) = a^2 - b^2$$

$$(a+b)(a-b) = a^2 - b^2$$

(\bar{Z}_L)

$$r + jx = \frac{1 - \Gamma_r^2 - \Gamma_i^2 + 2j\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

real Im.

i) Equating real parts

$$r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$r(1 - \Gamma_r)^2 + r\Gamma_i^2 = 1 - \Gamma_r^2 - \Gamma_i^2$$

$$r(1 - 2\Gamma_r + \Gamma_r^2) + r\Gamma_i^2 = 1 - \Gamma_r^2 - \Gamma_i^2$$

$$r - r\Gamma_r^2 + r\Gamma_i^2 = 1 - \Gamma_r^2 - \Gamma_i^2$$

$$\Gamma_r^2(x+1) - 2x\Gamma_r + \Gamma_i^2(x+1) = 1-x$$

$$\Gamma_r^2 - \frac{2x}{x+1}\Gamma_r + \Gamma_i^2 = \frac{1-x}{1+x}$$

Eqn. of circle w/ centre (a, b):

$$(x-a)^2 + (y-b)^2 = r^2$$

$$x = \Gamma_r$$

$$y = \Gamma_i$$

$$\left(\sqrt{r} - \frac{x}{x+1} \right)^2 + \sqrt{i}^2 = \frac{1-x}{1+x} + \frac{x^2}{(x+1)^2}$$

$$\left(\sqrt{r} - \frac{x}{x+1} \right)^2 + \sqrt{i}^2 = \left(\frac{1}{1+x} \right)^2$$

$$\text{center : } \left(\frac{x}{x+1}, 0 \right)$$

$$\text{Radius : } \left(\frac{1}{1+x} \right)$$

1) when $x=0$

$$\sqrt{r}^2 + \sqrt{i}^2 = 1$$

2) when $x = \frac{1}{2}$

$$\left(\sqrt{r} - \frac{1}{3} \right)^2 + \sqrt{i}^2 = \left(\frac{2}{3} \right)^2$$

W/ centre $\frac{1}{3}$, sketch a circle of radius $\frac{2}{3}$

3) when $x=1$


$$\left(\sqrt{r} - \frac{1}{2} \right)^2 + \sqrt{i}^2 = \left(\frac{1}{2} \right)^2$$

centre $\frac{1}{2}$, and radius $\frac{1}{2}$

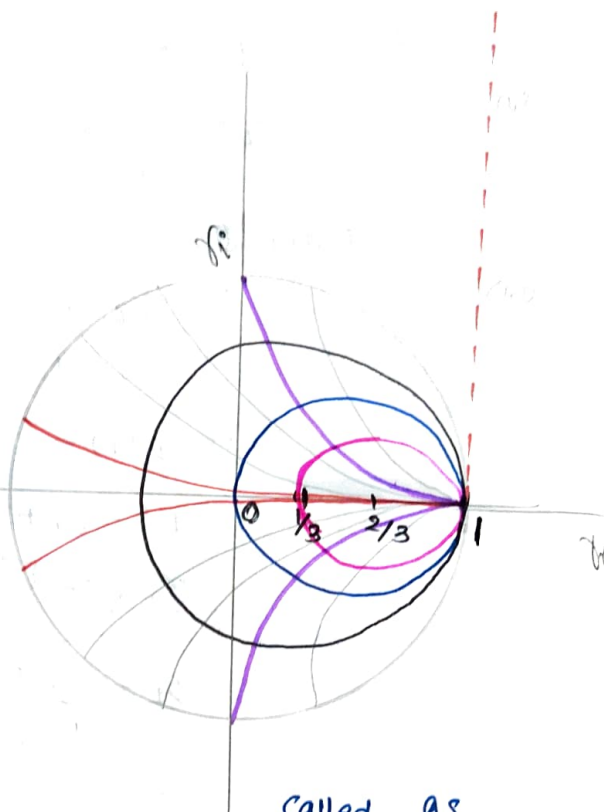4) when $x=2$

$$\left(\sqrt{r} - \frac{2}{3} \right)^2 + \sqrt{i}^2 = \left(\frac{1}{3} \right)^2$$

centre $\frac{2}{3}$, radius $\frac{1}{3}$



called as
"constant r -circle"
or resistance circles.

\Rightarrow When $r = \infty$,
smallest circle

That's why
 x is -ve (or)
+ve

x - can be cap / ind. reactance
but r - resistance
cannot be -ve.

ii) equating imaginary parts,

$$x = \frac{2r_i}{(1-r_r)^2 + r_i^2}$$

$$x = \frac{2r_i}{1 - 2r_r + r_r^2 + r_i^2}$$

$$\boxed{(r_r - 1)^2 + \left(r_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2}$$

1) when $x = 0$

$$(r_r - 1)^2 + (r_i - \infty)^2 = (\infty)^2$$

2) when $x = \frac{1}{2}$


$$(r_r - 1)^2 + (r_i - 2)^2 = 2^2$$

center: (1, 2)

Radius: 2

3) when $x = 1$

$$(r_r - 1)^2 + (r_i - 1)^2 = 1^2$$

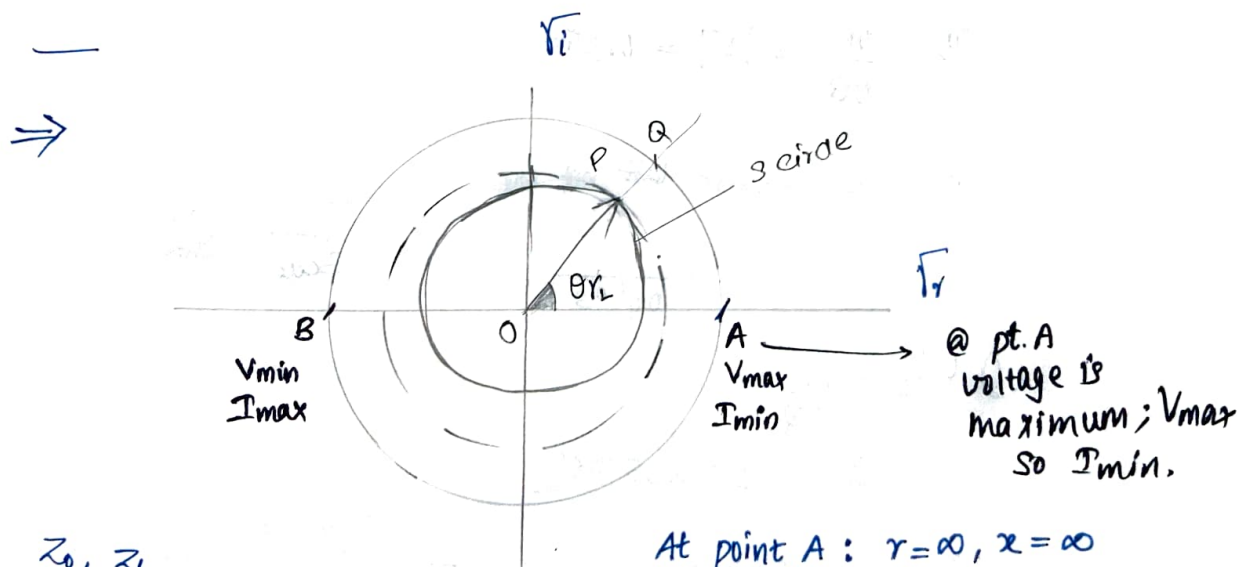

At point A: $r = \infty, x = \infty$

$$Z_L = \infty + j\infty$$

$$Z_L = \infty$$

open circuit.

Z_0, Z_L

$$Z_L = \frac{Z_L}{Z_0} = r + jx$$

normalised impedance.

114

At point B: $r = 0, x = 0$

$$Z_L = 0 + j0$$

$$Z_L = 0$$

Short circuit.

1) A lossless transmission line with $Z_0 = 50 \Omega$ is 30m long and operates at 2MHz. The line is terminated with a load $Z_L = (60 + j40) \Omega$. If $u = 0.6c$ on the line, find



- Γ using Smith chart.
- S
- Z_{in}

Sol. $Z_L = \frac{Z_L}{Z_0} = \frac{60 + j40}{50} = 1.2 + j0.8$

i) $OP = 2.7$
 $OQ = 7.7$ } from chart.

ii) $\frac{OP}{OQ} = |\Gamma| = 0.35$

iii) Bottom-most left but one.

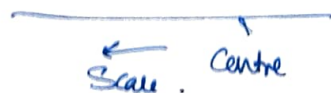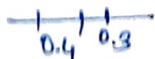

① $\Gamma_L = \frac{OP}{OQ}$

$\Gamma_L = 0.35 \angle 56^\circ$

iv) Draw circle w/ OP radius. = 2.1 = S ②

③ $\lambda = \frac{u}{f} = \frac{0.6c}{2M} = 90m$

For lossless,

one revolution = $\frac{\lambda}{2} = 360^\circ$; $\lambda = 720^\circ$
 $\frac{\lambda}{3} = 240^\circ$
 $90 \rightarrow \lambda$
 $36 \rightarrow \frac{\lambda}{3}$

$0.5\lambda = 720$

starting from P, clockwise (as expected), $56 + 240 = 184$
 extend 1.0 to 184.

→ Check where intersection.

we get $r = 0.48$
 $z = 0.04$

But this is normalised.

→ $Z_{in} = 0.48 + j0.04$

$Z_{in} = Z_0 Z_{in}$

$Z_{in} = 24 + j2$

21/11/23

2) A 70Ω lossless line has $S = 1.6$ and $\theta_r = 300^\circ$. If the line is 0.6λ long, obtain



1) T, Z_L, Z_{in}

2) The distance of first voltage minimum from the load. (r/r_{axis})

Sol. → From 1.0 as centre, draw a circle passing through 1.6 because $S = 1.6$

→ Draw a line joining the centre at 300° in Anticlockwise

dirn or 60° clockwise

→ Pt. of intersection of this line w/ S circle = Z_L

→ $(1.15, 0.5)$

∴ $Z_L = 1.15 - j0.5$

but we need Z_L ,

$$\rightarrow Z_L = Z_0 Z_L$$

$$= 70 (1.15 - j0.5)$$

$$\rightarrow \Gamma = \frac{OP}{OQ} = \frac{1.7}{7.6} = 0.22$$

① directly from
Ref. coeff below.
after getting OP

$$\gamma = 0.22 \angle 300^\circ$$

② Get OP, OQ from diag
& divide.

$$\rightarrow Z_{in} = ?$$

WR, one revolution; $360^\circ = \frac{\lambda}{2}$ in z

Method 1:

Given, $0.6\lambda = 1$

$$0.6 \times 720 = 432^\circ \rightarrow \text{from } 0.334 \text{ point}$$

$$432 - 360 = 72^\circ$$

$$Z_{in} = 0.68 - j0.25 \rightarrow \text{below}$$

$$Z_{in} = Z_0 Z_{in}$$

Method 2:


From 0.334, mark
0.6 λ

1 rev till 0.334 = 0.5.
then add + 0.1 λ to it

$$\text{So. } 0.334 + 0.1 = 0.434 \checkmark$$

$$2) 0.5 - 0.334 = 0.166$$

QUARTER WAVE TRANSFORMER

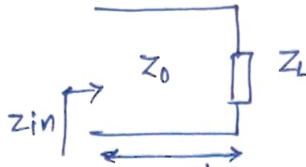

We want inp Impedance for this; $l = \frac{\lambda}{4}$ = length of transmission line

$$z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$$

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \pi/2$$

$$= Z_0 \left(\frac{Z_L + jZ_0 \tan \pi/2}{Z_0 + jZ_L \tan \pi/2} \right)$$

\div Nr & Dr by $\tan \pi/2$

$$= Z_0 \left(\frac{\frac{Z_L}{\tan \pi/2} + jZ_0}{\frac{Z_0}{\tan \pi/2} + jZ_L} \right)$$

$$Z_{in} = Z_0^2 \frac{1}{Z_L}$$


Input impedance for a quarter wave transformer.

→ Quarter wave matching.


23/11/23

We have transformer whose char. imp = Z_0

load imp = Z_L

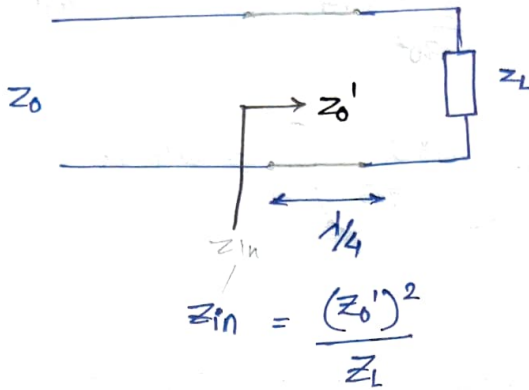

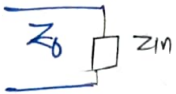$Z_0' =$ char. imp. of quarter wave transformer.




$$Z_{in} = \frac{(Z_0')^2}{Z_L} = Z_0$$

This condition should be satisfied for matching

→ At what frequency matching happens?
Freq. corresponding to $\frac{\lambda}{4}$.

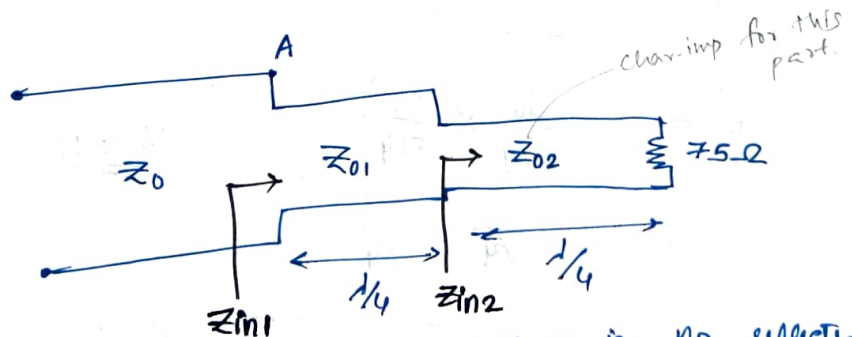Q1) Two $\frac{\lambda}{4}$ transformers in tandem are to connect a 50Ω line to a 75Ω load as shown in the figure.



Determine Z_{01} if $Z_{02} = 30\Omega$, and there is no reflected wave to the left of A.

Sol.

$$Z_{in2} = \frac{(Z_{02})^2}{75} = \frac{(30)^2}{75} \Omega$$

$$Z_{in1} = \frac{(Z_{01})^2}{Z_{in2}} = \cancel{70}$$

Since no reflection to left of A means has to be matched.


$$\frac{Z_{01}^2}{30^2} (75) = 50$$

$$\frac{Z_{01}}{Z_{in2}} = 1$$

$$Z_{01} = \left(\frac{50 \times 30^2}{75} \right)^{\frac{1}{2}} = 24.49$$

2) Two identical antennas with load impedance 74Ω are fed with 3 identical 50Ω quarter wave lossless transmission lines as shown in the figure.


each is Z_0 .

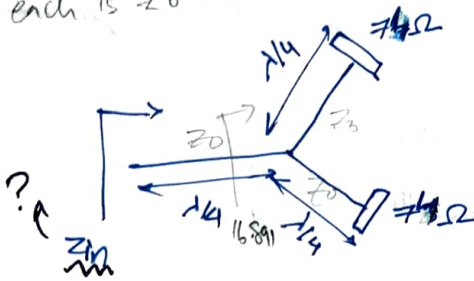

Acting as load even if not mentioned in question.

Calculate input impedance at the source.

Sol.

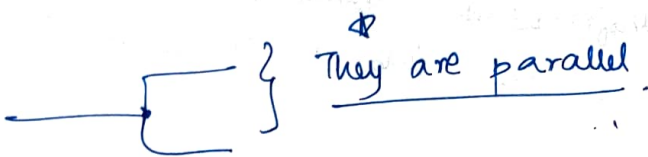

They are parallel.

$$Z_{in}' = \frac{\frac{50^2}{74} \times \frac{50^2}{74}}{\frac{50^2}{74} + \frac{50^2}{74}} = \underline{\underline{16.891}}$$

$$Z_{in} = \frac{50^2}{Z_{in}'(Z_0)} = \frac{50^2}{16.891} = \underline{\underline{148.007 \Omega}}$$

Maam's method :

$$Z_{in1} = Z_{in2} = \frac{(50)^2}{74} \Omega$$

Admittance $Y_{in1} = Y_{in2} = \frac{74}{(50)^2}$

$$Y = Y_{in1} + Y_{in2} = \frac{148}{(50)^2}$$


$$Z_{in} = \frac{50^2}{\frac{1}{Y}} = 148 \Omega$$

becos when in
||, easier
if admittance!

$$Z = \frac{1}{Y}$$

→ SINGLE STUB MATCHING

(using Smith chart.)

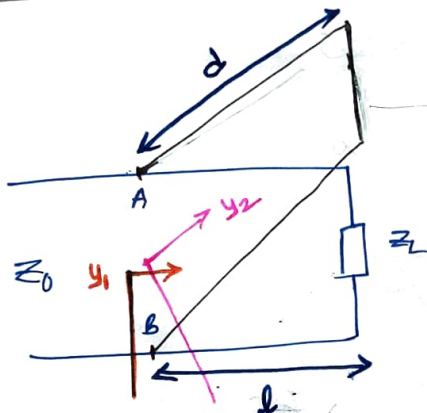

In Syllabus.
By using i) short ckt tho
ii) open ckt tho
(in || to main
transmission line)

Stub.

If matched,

$$\text{WK, } \left[\frac{Z_L}{Z_0} = 1 \right]$$

Normalised Impedance = 1,

so we can say admittance also = 1

why we took? cos
||, so easier.

$$Y_1 = 1 + jX$$

$$\therefore Y_2 = -jX$$

At AB admittance,

$$Y = Y_1 + Y_2 = 1 + jX - jX$$

$$\underline{Y = 1}$$

For matching, $Y = 1$ (only
real part)

Suppose Y_1 has jX

so Y_2 should have $-jX$


so that $Y = Y_1 + Y_2 = 1$

Q) Consider 3 lossless lines as shown in the figure.

If $Z_0 = 50 \Omega$, Calculate i) Z_{in} looking into line 1

ii) Z_{in} looking into line 2

iii) Z_{in} looking into line 3.

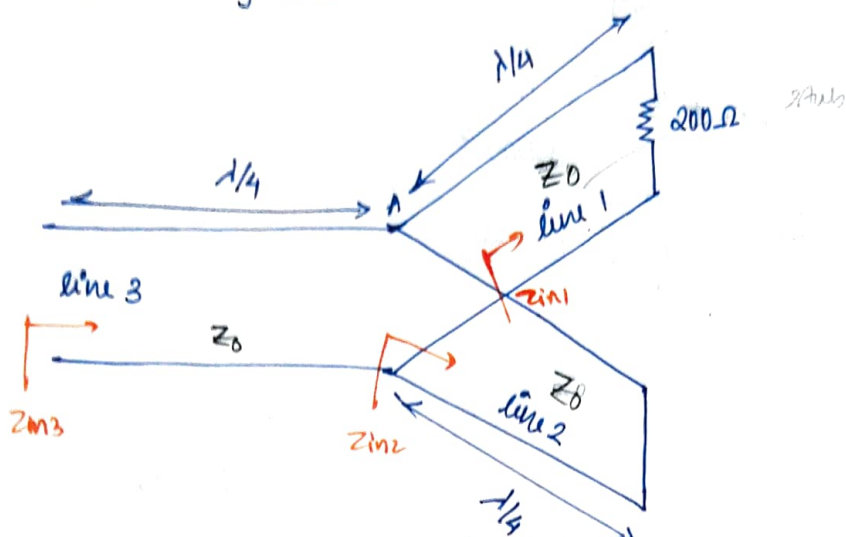

Sol.

i) $Z_{in1} = \frac{Z_0^2}{200} = 12.5 \Omega$

ii) $Z_{in2} = \frac{Z_0^2}{0} = \infty$

iii) $Z_{in3} = \frac{Z_0^2}{Z_L}$

At A,
 $Y = \frac{200}{(50)^2} + 0$

$Z_{in1} \parallel Z_{in2} = \frac{12.5 \cdot \infty}{12.5 + \infty} = \frac{\infty (12.5)}{\infty (\frac{12.5}{\infty} + 1)} = 12.5$

$Z_{in3} = \frac{(Z_0)^2}{12.5} = 200 \Omega$