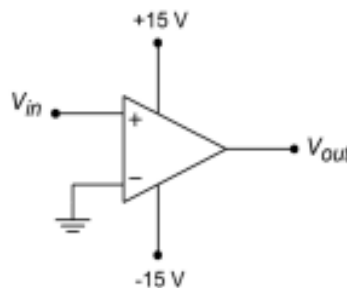



LINEAR INTEGRATED CIRCUITS QUESTION BANK

UNIT-1


- 1) List out features of ideal op amp.
- 2) Draw circuit diagram of inverting amplifier and write equation for its transfer function.
- 3) Draw circuit diagram of non inverting amplifier and write equation for its transfer function.
- 4) Write equation for output voltage in a summing amplifier.
- 5) Circuit diagram shown. What is output voltage for input voltage 0V, 1V and -2V.



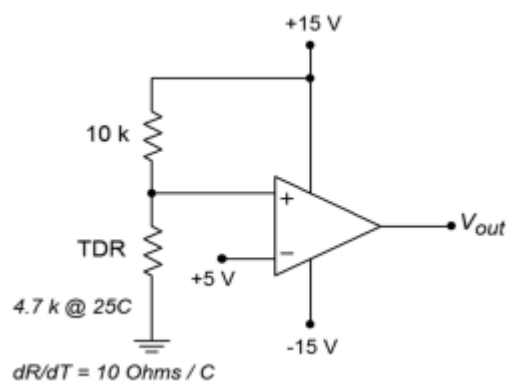- 6) What is the value of temperature dependent resistor at trip point? Refer circuit diagram shown below.



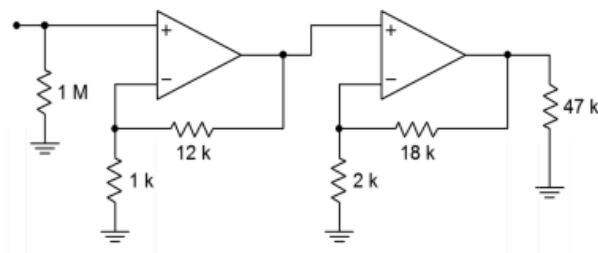- 7) For the circuit shown, what is the output voltage if input is -52dbV



- 8) Design an inverting amplifier with a gain of 14dB and input impedance of 10Kohm
- 9) Design a summing amplifier such that channel 1 has a gain of 10, channel 2 has a gain of 15 and channel 3 has a gain of 5. The minimum channel input impedance should be 1Kohm
- 10) For the circuit shown below, write equation for output voltage

