

# LINEAR INTEGRATED CIRCUITS

---

**Dr Shashidhar Tantry**

Electronics and Communication Engineering

## Unit 1 Adder (Summing Amplifier)

- Non-inverting input is grounded
- More than one input is connected to inverting input

$$V_{OUTN} = -\frac{R_F}{R_N}V_N$$

$$V_{OUT1} = -\frac{R_F}{R_1}V_1$$

$$V_{OUT2} = -\frac{R_F}{R_2}V_2$$

$$V_{OUT} = -\left(\frac{R_F}{R_1}V_1 + \frac{R_F}{R_2}V_2 + \frac{R_F}{R_N}V_N\right)$$

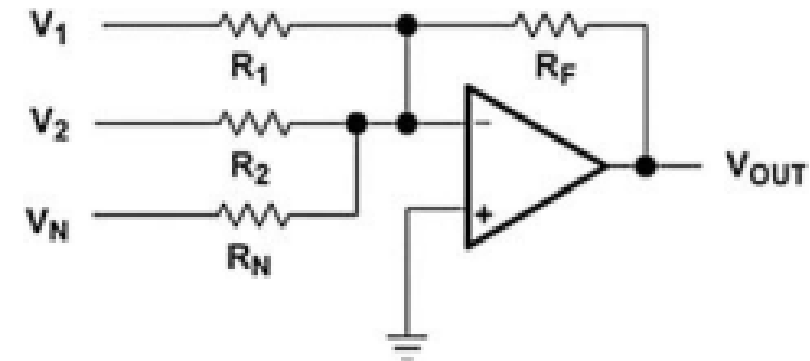


Figure 2.5

**Circuit is also called summing amplifier**

## Unit 1 Summing Amplifier

Design a circuit whose output is  $V_{out} = -2(3V_1 + 4V_2 + 2V_3)$

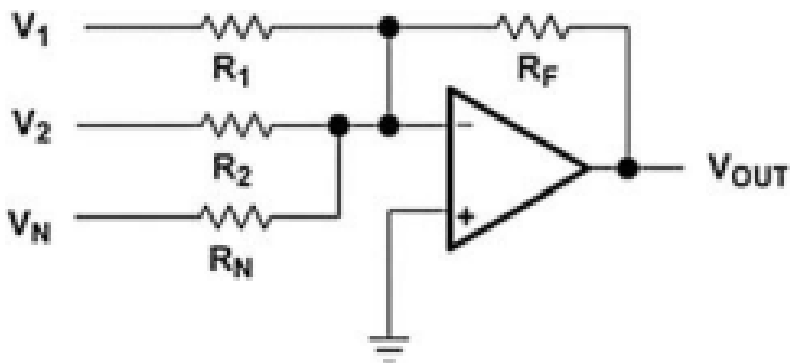


Figure 2.5

Answer is  
 $R_F = 10\text{Kohm}$  (Assume)  
 $R_1 = 1.6\text{Kohm}$   
 $R_2 = 1.25\text{Kohm}$   
 $R_3 = 2.5\text{Kohm}$

## Unit 1 Differential Amplifier

- Amplifies difference between two signals applied at the input
- Superposition theorem is used to calculate output

$$V_+ = V_1 \frac{R_2}{R_1 + R_2}$$

$$V_{OUT1} = V_+(G_+) = V_1 \frac{R_2}{R_1 + R_2} \left( \frac{R_3 + R_4}{R_3} \right)$$

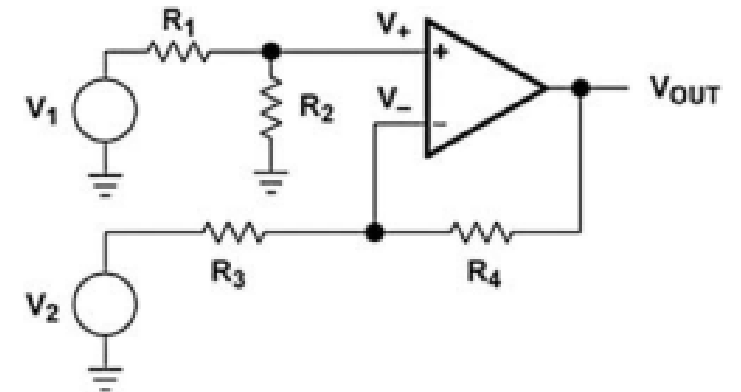


Figure 2.6

$$V_{OUT2} = V_2 \left( \frac{-R_4}{R_3} \right)$$

$$V_{OUT} = V_1 \frac{R_2}{R_1 + R_2} \left( \frac{R_3 + R_4}{R_3} \right) - V_2 \frac{R_4}{R_3}$$

When  $R_1 = R_3$  and  $R_2 = R_4$

$$V_{OUT} = (V_1 - V_2) \frac{R_4}{R_3}$$

## Unit 1 Differential amplifier

Design a simple difference amplifier with an input impedance of  $10\text{ k}\Omega$  per leg, and a voltage gain of 26 dB.

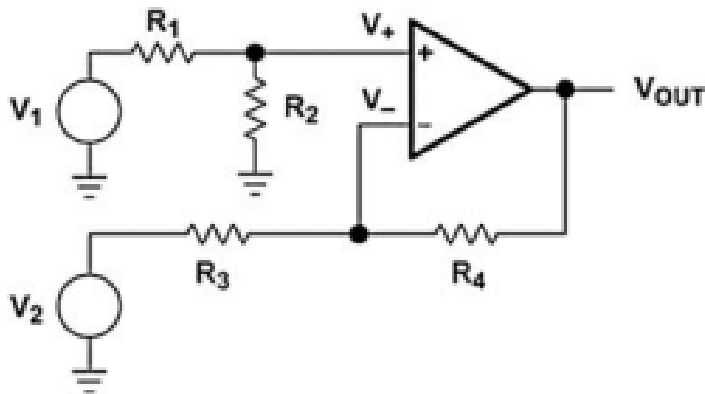


Figure 2.6

Answer is

$R_3 = 10\text{Kohm}$


$R_4 = 200\text{Kohm}$

$R_1 = 500\text{ohm}$


$R_2 = 9.5\text{Kohm}$
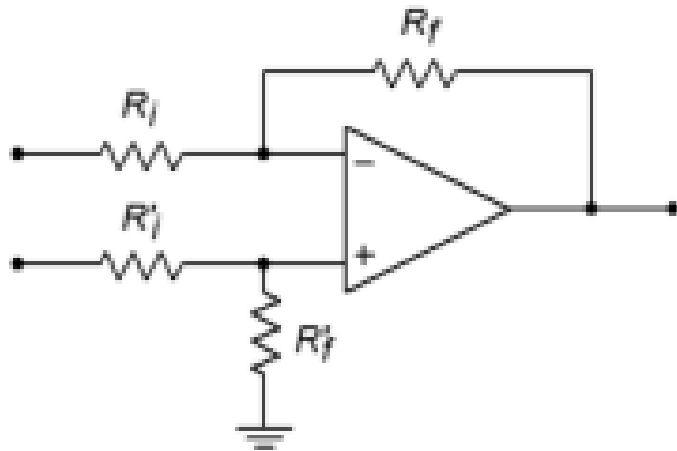
## Unit 1 Instrumentation amplifier

- Specialized op amp
- Offers very high input impedance
- Derived from **differential amp**




Buffer

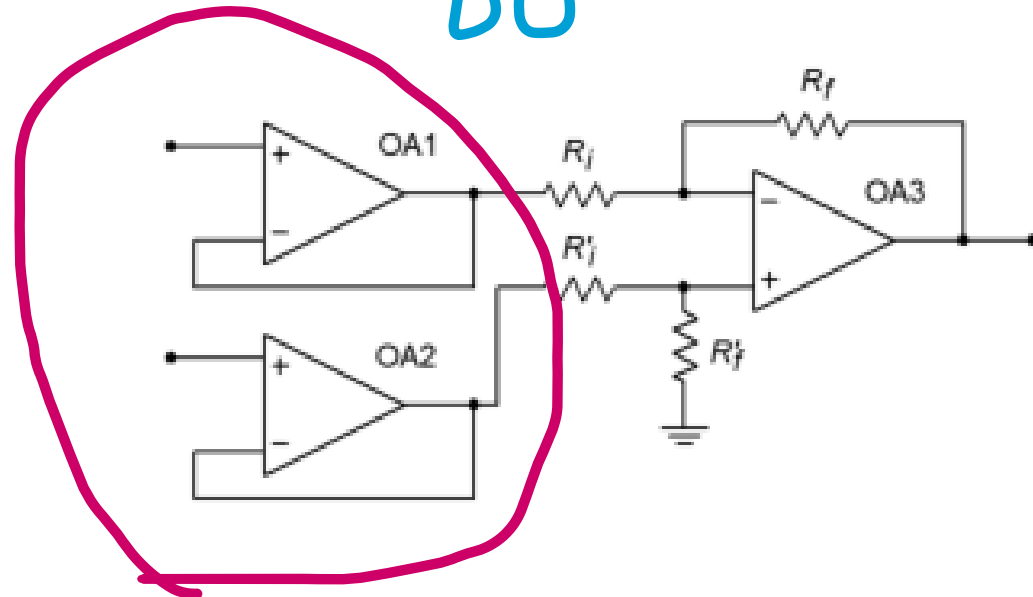

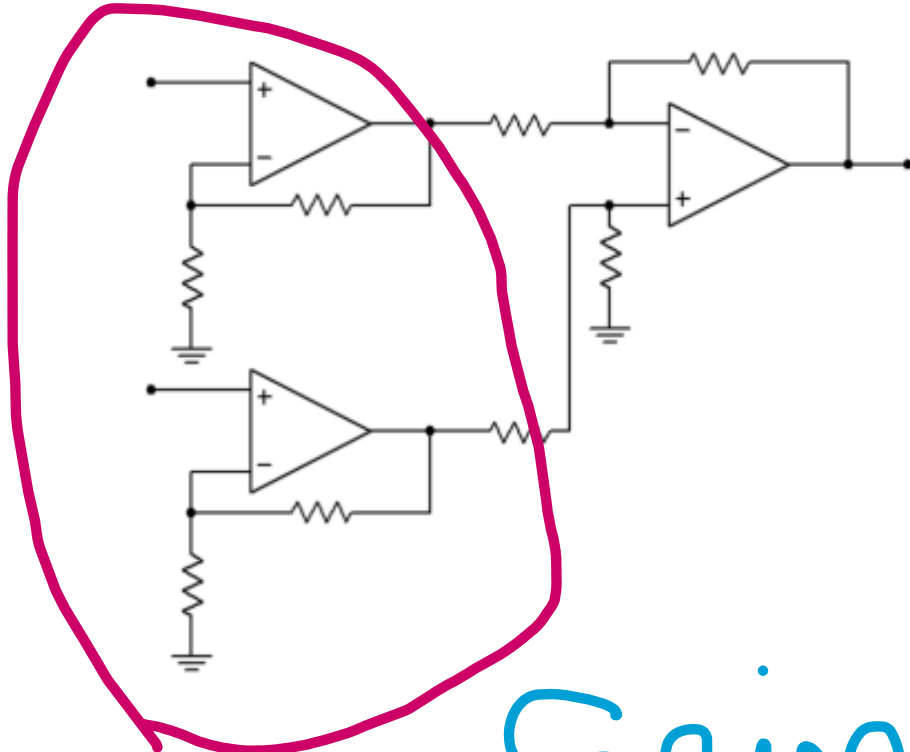
## Unit 1 Instrumentation amplifier

- Specialized op amp with higher precision
- Derived from differential amp



Gain

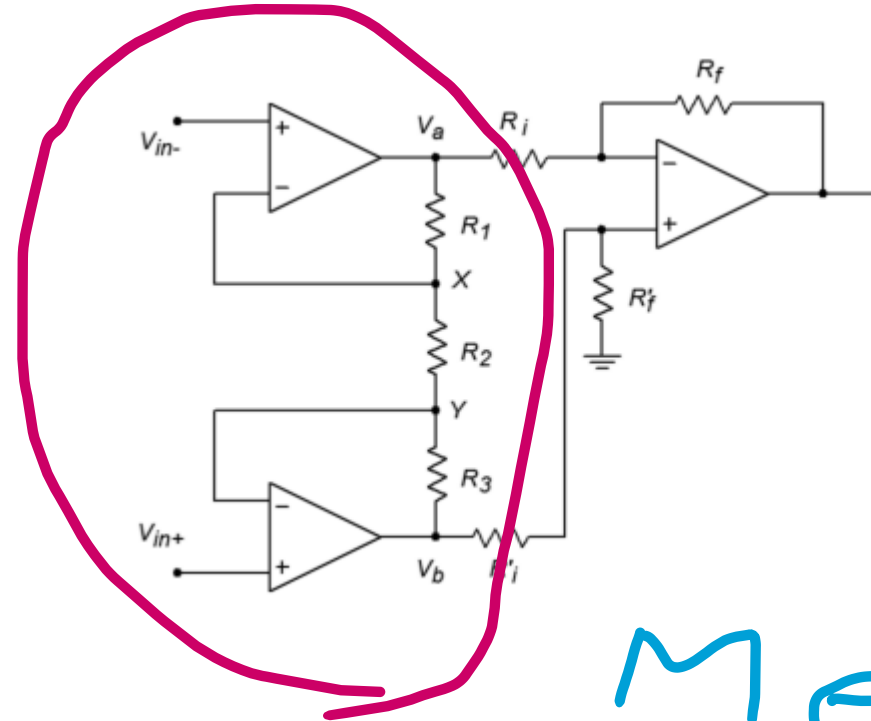

Merge

## Unit 1 Instrumentation amplifier Analysis

From Difference amp relation,

$$V_{out} = \frac{R_f}{R_i} (V_b - V_a)$$

From Ideal op amp relation,

$$V_x = V_{in-}$$

$$V_y = V_{in+}$$

The output voltage  $V_a$  must equal  $V_x$  plus the drop across  $R_f$ .

$$V_a = V_x + V_{Rf}$$

Voltage drop across  $R_1$  is given by,

$$V_{R1} = R_1 I_{R1}$$

$$V_{R1} = R_1 I_{R2}$$

Current  $I_{R2}$  is given by,

$$I_{R2} = \frac{V_x - V_y}{R_2}$$

Value of  $V_a$  is given by,

$$V_a = V_x + \frac{R_1 (V_x - V_y)}{R_2}$$



## Unit 1 Instrumentation amplifier Analysis

After substitution,

$$V_a = V_{in-} + \frac{R_1(V_{in-} - V_{in+})}{R_2}$$

$$V_a = V_{in-} + \frac{R_1}{R_2}(V_{in-} - V_{in+})$$

$$V_a = V_{in-} + V_{in-} \frac{R_1}{R_2} - V_{in+} \frac{R_1}{R_2}$$

$$V_a = V_{in-} \left(1 + \frac{R_1}{R_2}\right) - V_{in+} \frac{R_1}{R_2}$$

By a similar derivation, the equation for  $V_b$  is found

$$V_b = V_{in+} \left(1 + \frac{R_3}{R_2}\right) - V_{in-} \frac{R_3}{R_2}$$

For gain matching  $R_3$  is set equal to  $R_1$ .

And after substitution

$$V_{out} = \frac{R_f}{R_i} \left( \left( V_{in+} \left(1 + \frac{R_1}{R_2}\right) - V_{in-} \frac{R_1}{R_2} \right) - \left( V_{in-} \left(1 + \frac{R_1}{R_2}\right) - V_{in+} \frac{R_1}{R_2} \right) \right)$$

After combining terms,

$$V_{out} = \frac{R_f}{R_i} \left( (V_{in+} - V_{in-}) \left(1 + \frac{R_1}{R_2}\right) + (V_{in+} - V_{in-}) \frac{R_1}{R_2} \right)$$

$$V_{out} = (V_{in+} - V_{in-}) \left( \frac{R_f}{R_i} \right) \left( 1 + 2 \frac{R_1}{R_2} \right)$$



# THANK YOU

---

**Dr Shashidhar Tantry**

Electronics & Communication  
Engineering

**stantry@pes.edu**

